

Name: \_\_\_\_\_ Section: \_\_\_\_\_ Date: \_\_\_\_\_

## Worksheet - Exp 15: Ohm's Law

**Objective:** This experiment applies Ohm's Law to varying voltages, currents, and resistances in order to study the relationship. Students will become familiar with reading resistor color codes.

**Theory:**


Ohm's Law states that the current  $I$  that flows in a circuit is directly proportional to the voltage  $V$  across the circuit and inversely proportional to the resistance  $R$  of the circuit.

Knowing the value of any two of these variables in a circuit, one can solve for the third. In this lab, voltage and current will be manipulated in order to determine the equivalent resistance of a circuit.

$$I = \frac{V}{R}$$

1. A simple series circuit, like the one used in this experiment, is shown at the right. If the resistance of the circuit is  $11 \text{ k}\Omega$ , what voltage must be applied to achieve a current of  $16 \text{ mA}$ ? (3 pts)

$V =$  \_\_\_\_\_

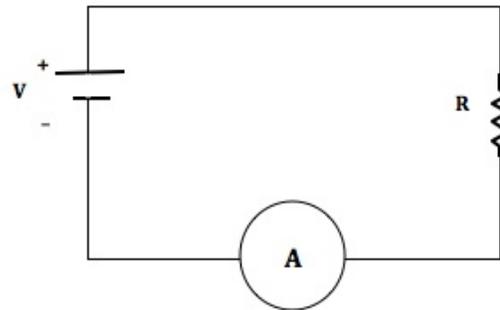

2. Consider the behavior of the above circuit when altered in the following manner. Voltage and resistance are both increased; the current in the circuit will be: (3 pts)
- Increased
  - Decreased
  - Unchanged
  - (not enough information)
3. Currents as low as  $0.07 \text{ amps}$  can be fatal when they pass through the human heart, but this semester's experiment will involve currents of several amps. To see why the experiment is safe, calculate the voltage required to produce such a current, assuming the human body has a resistance of about  $10,000 \Omega$ . (2 pts)

**Procedure**

**Part 1: Measures of Resistance**

4. Determine the nominal resistance for the three resistors: interpret the color codes according to the color code chart provided at the bottom of the page.
5. Measure the actual resistance of the three resistors using the ohmmeter and record them in the Table.
6. Do the measured resistances fall within the tolerance of the nominal resistance for each resistor? If not, what might cause their measured values to differ from those listed? (3 pts)
  
7. An ideal ammeter has no resistance; this ammeter does have a small resistance. Measure the resistance of the ammeter. (2 pts)

$R_A =$  \_\_\_\_\_

<u>Color</u>	<u>Number</u>	<u>Multiplier</u>
Black	0	10 <sup>0</sup>
Brown	1	10 <sup>1</sup>
Red	2	10 <sup>2</sup>
Orange	3	10 <sup>3</sup>
Yellow	4	10 <sup>4</sup>
Green	5	10 <sup>5</sup>
Blue	6	10 <sup>6</sup>
Violet	7	10 <sup>7</sup>
Grey	8	10 <sup>8</sup>
White	9	10 <sup>9</sup>
 <u>Tolerance</u>		
Gold	5%	
Silver	10%	
(No Band)	20%	

**Table 1**

**R<sub>1</sub>**

Color Code	_____   _____   _____   _____
Code Value	_____   _____   10 <sup>^</sup> _____ ± _____ %
Nominal Resistance	_____ ± _____ Ω
Measured Resistance	_____

(5 pts)

**R<sub>2</sub>**


Color Code	_____   _____   _____   _____
Code Value	_____   _____   10 <sup>^</sup> _____ ± _____ %
Nominal Resistance	_____ ± _____ Ω
Measured Resistance	_____

(5 pts)

**R<sub>3</sub>**

Color Code	_____   _____   _____   _____
Code Value	_____   _____   10 <sup>^</sup> _____ ± _____ %
Nominal Resistance	_____ ± _____ Ω
Measured Resistance	_____

(5 pts)

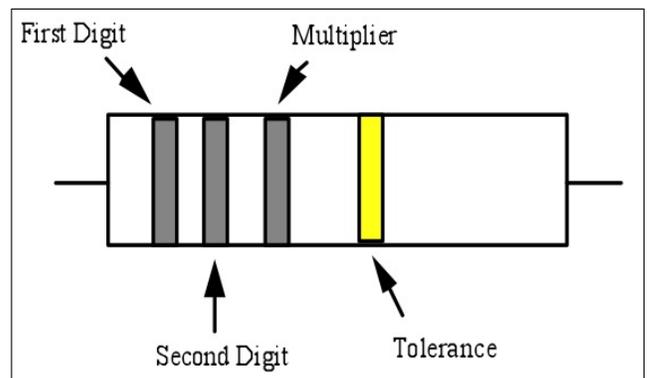

**Part 2: Ohm's Law Applied**

8. Build a simple series circuit using  $R_1$ , an ohmmeter, an ammeter, and a jumper.
9. Measure the equivalent resistance of the circuit using the ohmmeter and record this value in the table. Include units and uncertainty.
10. Is the equivalent resistance what we expect it to be – is it equal to the resistance of  $R_1$  plus the resistance of the ammeter? What would cause  $R_{eq}$  to be different than  $R_1 + R_A$ ? (4 pts)

11. Remove the ohmmeter and connect the unplugged power supply to the circuit. Connect a voltmeter to the circuit, across the power supply leads (in parallel).
12. Have your TA check your circuit. Plug in the power supply and turn it on.
13. Test Ohm's Law ( $V = IR$ ) by verifying that current increases linearly with applied voltage. Apply 1V, 2V, 3V, and 4V to the circuit. Measure current and voltage and record them in the table. Include units and uncertainty.
14. Repeat the *Ohm's Law Applied* procedure for  $R_2$  and  $R_3$ .

**Table 2**

<b>R<sub>1</sub> circuit</b>	
Equivalent Resistance: $R_{eq} =$ _____	
Voltage	Current
<b>R<sub>2</sub> circuit</b>	
Equivalent Resistance: $R_{eq} =$ _____	
Voltage	Current
<b>R<sub>3</sub> circuit</b>	
Equivalent Resistance: $R_{eq} =$ _____	
Voltage	Current

(18 pts)



**Part 4: Graphing**

19. Open your graphing software. Enter all of your voltage and current data from Tables 2 and 3 as four separate data sets (one for each resistor). Include the point (0,0) in each set.
20. Plot  $I$  vs.  $V$  for the three Ohmic resistors. Apply a linear fit to each one. (18 pts)
21. What does the slope of this graph represent? Consider Ohm's law and how it is represented on the graph by  $y = mx$ . (6 pts)

22. Calculate the resistance of each circuit using the slope of your  $I$  vs.  $V$  graphs. Compare these  $R_{graph}$  values to the measured  $R_{eq}$  values using the percent difference formula. (6 pts)

$$R_1 \text{ circuit: } R_{graph} = \underline{\hspace{2cm}} \quad \% \text{ Diff.} = \underline{\hspace{2cm}}$$

$$R_2 \text{ circuit: } R_{graph} = \underline{\hspace{2cm}} \quad \% \text{ Diff.} = \underline{\hspace{2cm}}$$

$$R_3 \text{ circuit: } R_{graph} = \underline{\hspace{2cm}} \quad \% \text{ Diff.} = \underline{\hspace{2cm}}$$

23. Plot a separate  $I$  vs.  $V$  graph for the light bulb. (5 pts)
24. Does the slope of this graph change at different voltages, or does it remain constant? What does this tell you about the resistance of the light bulb? (5 pts)

25. Print a copy of both graphs and submit them with your worksheet.