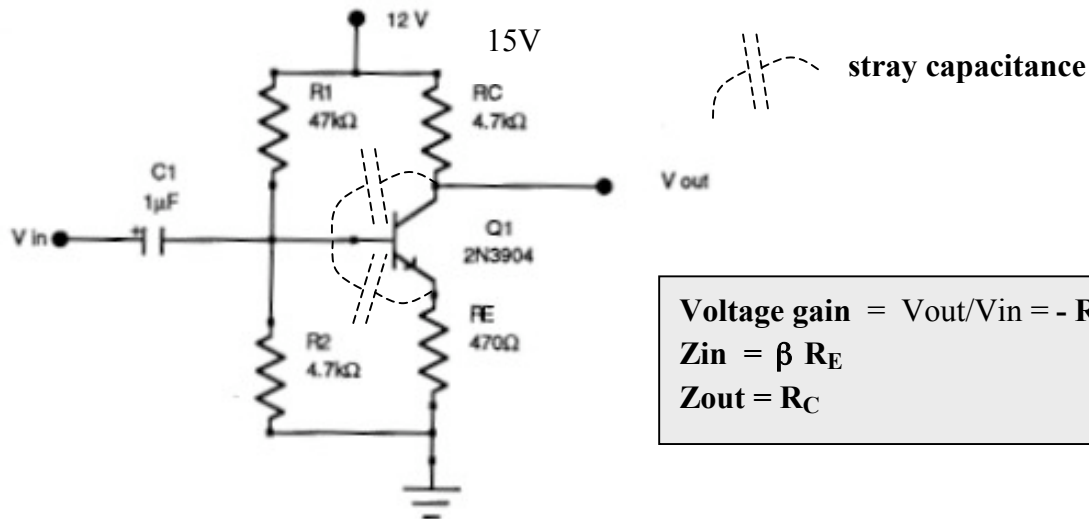


COMMON EMITTER AMPLIFIER

The transistor can be used as a voltage amplifier. The gain will be temperature dependent, and certain distortions will be encountered. More suitable amplifiers in which combinations of transistors called OP-AMPS , operational amplifiers, are more practical devices. But it will be instructive to build a simple transistor amplifier.



- The input signal is AC coupled to the amplifier. The input capacitor blocks the DC.
- The output impedance is selected to be $R_C = 4700\Omega$.
- We choose the voltage drop across V_C to be half the supply voltage $V_C = 15V/2 = 7.5V$.
- The current then is $I_C = 15V - V_C / R_C = 7.5 / 4.7K = 1.6mA$
- For a gain of 10 then $R_E = R_C / 10 = 470\Omega$
- To set the base voltage divider note that $V_E = I_E R_E = I_C R_E = (1.6mA)(470\Omega) = 0.75V$
- $V_B = 0.75V + 0.6V = 1.35V$
- $\beta R_E \gg R_2$ to limit the power supply current through the base.
 $R_2 = 10 R_E = 4700\Omega$
- $I_2 = V_B / R_2 = 1.35V / 4700\Omega = 0.29mA$ $I_B = I_C / \beta = 8\mu A$
- $I_1 = I_2 + I_B = 0.30mA$
- $R_1 = (15V - V_B) / I_1 = 13.6V / 0.30e-3A = 45k\Omega$ (Use 47 kΩ)

hfe

Measure the $\beta = h_{fe}$ of your transistor with the DMM.

$\beta =$ _____

GAIN

Construct the circuit and drive it with at the smallest voltage available on your sweep generator (~500mv). Vary the frequency from 10 Hz to 1MHz in decades of ten. Record and plot the output voltage gain. Record the relative phase eg. -180° .

Gain vs Frequency

gain	20						
	15						
	10						
	5						
	0						
		10	100	1K	10K	100k	1M frequency Hz
phase							

Question#1- Is the voltage gain and phase what you expected from theory of the common emitter amplifier? Explain.

Question#2- What is the input and output impedance of your amplifier?

Question#3- Explain any frequency dependence of the voltage gain.

Question#4- Is it possible to modify the circuit to give a gain of 1000. Explain.