

Digital Circuitry

Flip-Flops

LEDs - Seven Segment Decoder

Binary Counters

Multiplexing


Shift Registers

Adder

One Shot

Flip-Flop

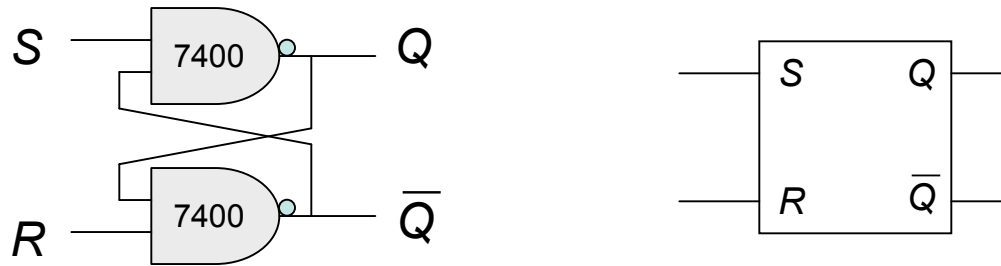
- In a number of digital applications one needs a device whose outputs Q_1, Q_2 states go hi and low as the input states changes.
- Since $S/R=1/0$ and $S/R=0/0$ leave $Q=1$ we have a bounceless switch!



<i>Set</i>	<i>Reset</i>	Q	\bar{Q}
0	0	NC	NC
1	0	1	0
0	1	0	1
1	1	?	?

RST Flip-Flop (Latch)

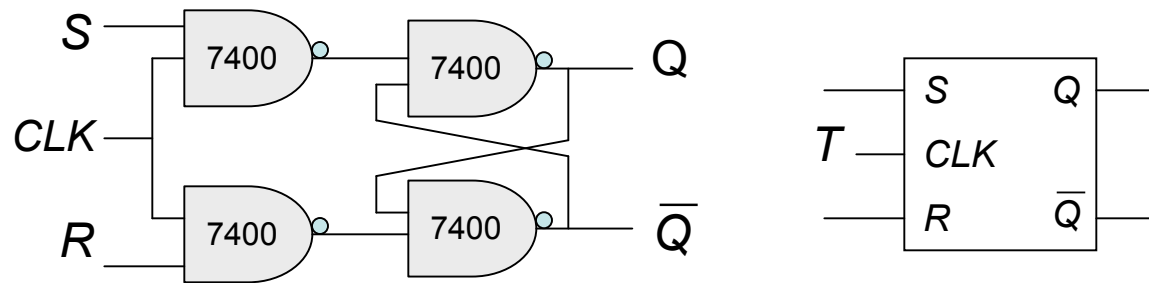
- In a clocked RST-FF the state is only allowed to change if the clock is high.
- The clock signal thus *latches* (locks) the output state.




		CLK=1		CLK=0	
Set	Reset	Q	\bar{Q}	Q	\bar{Q}
0	0	NC	NC	NC	NC
1	0	1	0	NC	NC
0	1	0	1	NC	NC
1	1	?	?	NC	NC

Data and Toggle Flip-Flops

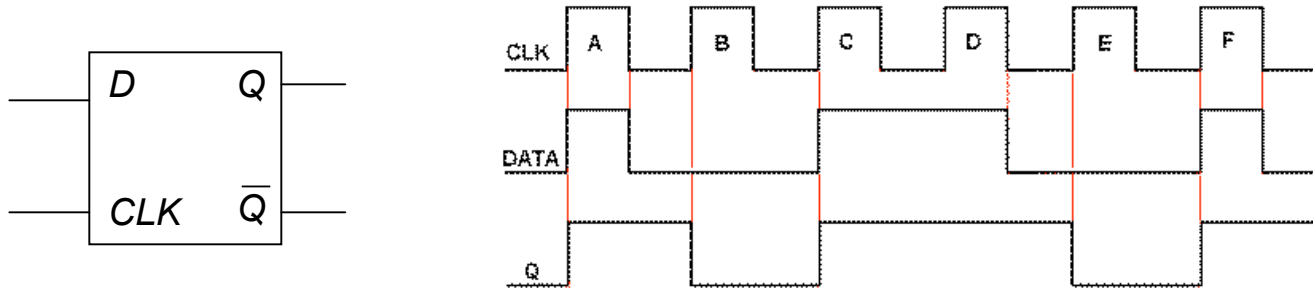- A D flip-flop (DFF) avoids the indeterminate states (NR).
- When the CLK=hi Q is set to D (0 or 1)
- When CLK = low Q unchanged




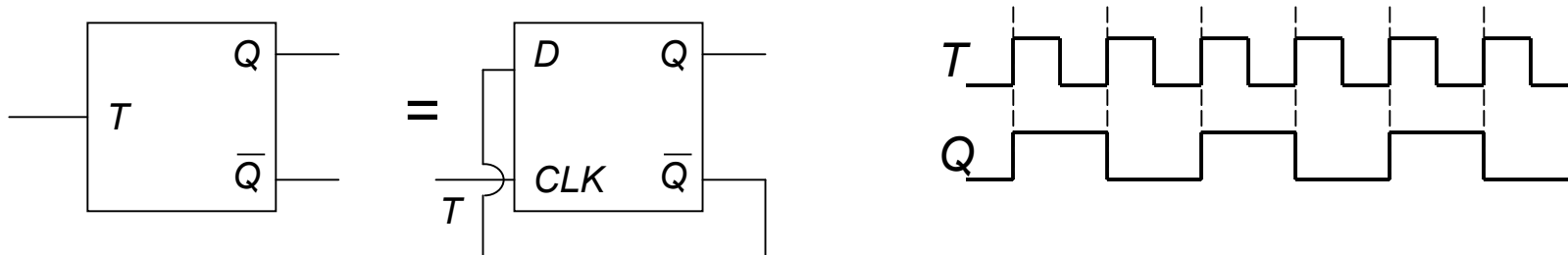- A Toggle flip-flop (TFF) flips state upon a T=1 pulse.
- When T=1 $Q=0 \rightarrow Q=1$ or $Q=1 \rightarrow Q=0$
- When T=0 No Change



JK Flip-Flops

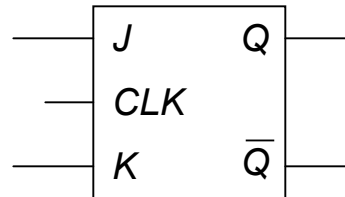- The J-K flip-flop can be wired to behave as most other types of flip-flop.
- It incorporates the functionality of the previous FFs.



- CLK=LO NC
- CLK=HIGH

If J is high and K is low, Q will set. ($Q=1$)

If K is high and J is low, Q will reset ($Q=0$)

If J and K are both low, Q will not change. (NC)

If J and K are both high, the output toggles on the clock pulse.

BCD to 7-Segment Decoder


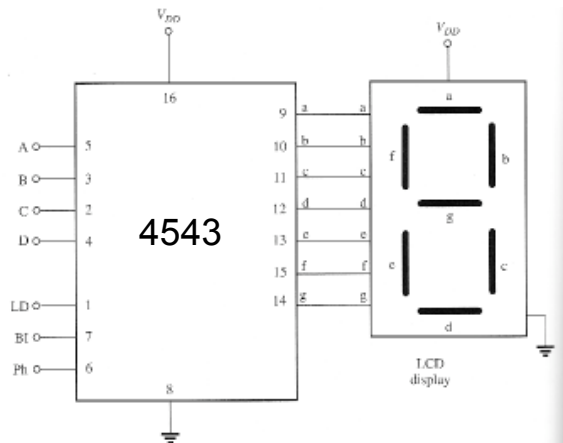


FIGURE 12.14 BCD-to-seven-segment latch/decoder/driver for LCD display.

- BCD #'s are decoded to turn on digit forming LEDs



BCD inputs				segment outputs							display
D	C	B	A	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	1	0	0	0	0	1
0	0	1	0	1	1	0	1	1	0	1	2
0	0	1	1	1	1	1	1	0	0	1	3
0	1	0	0	0	1	1	0	0	1	1	4
0	1	0	1	1	0	1	1	0	1	1	5
0	1	1	0	0	0	1	1	1	1	1	6
0	1	1	1	1	1	1	0	0	0	0	7
1	0	0	0	1	1	1	1	1	1	1	8
1	0	0	1	1	1	1	0	0	1	1	9

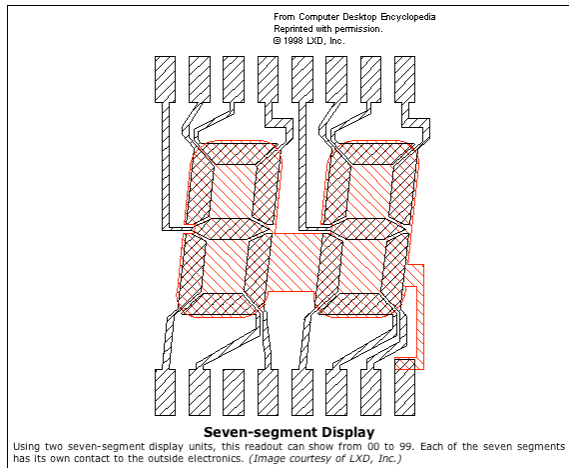


- Two 7-segment displays.

Ripple Counter

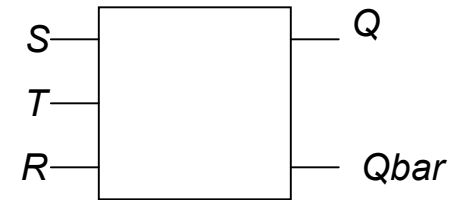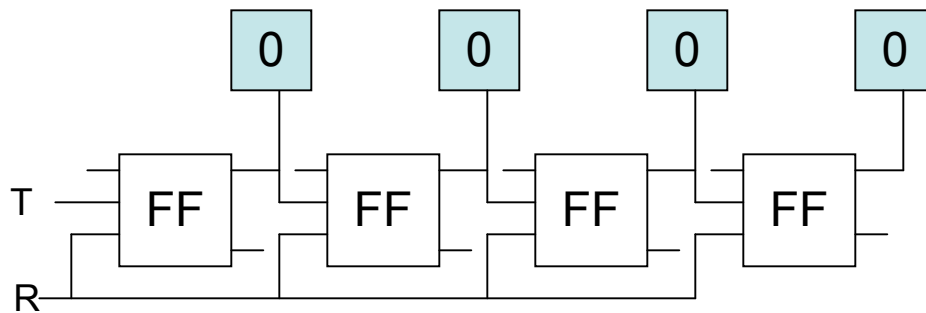- A ripple counter uses RST flip-flops to perform binary counting.
- The Q of each FF toggles the next in the chain.
- Initially a reset $R=1$ is issued setting all flip-flops to $Q=0$.
- The *true* RST FF changes on a down transition.



Ripple Counter

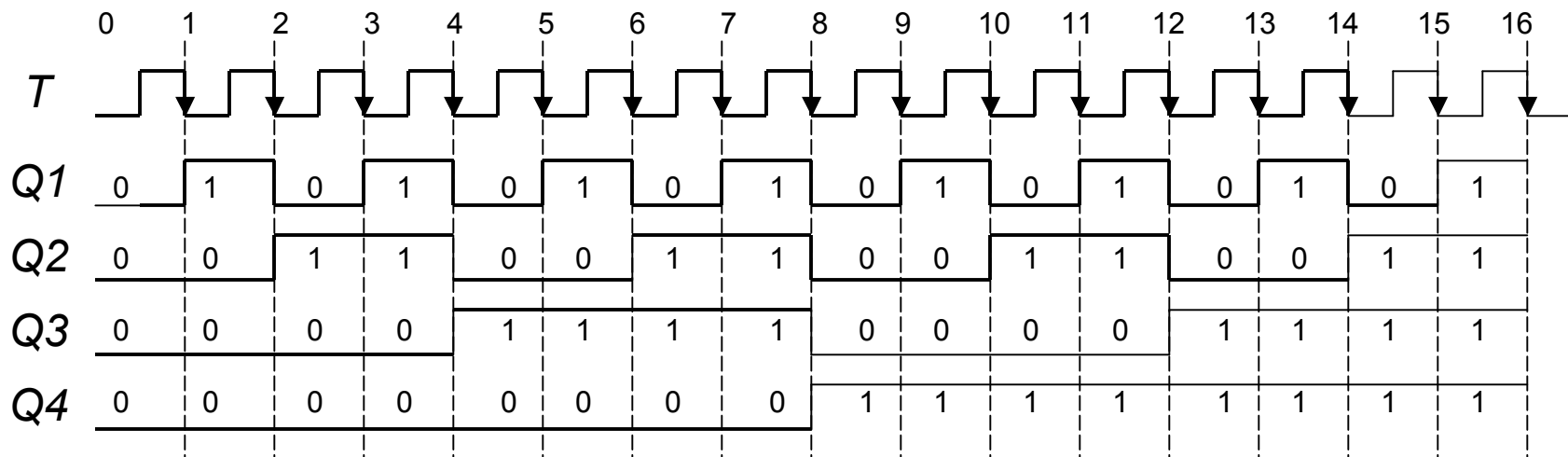

Multiplexer

- A multiplexer allows any of a number of inputs states to be translated to an output state.
- A decimal input could be multiplexed to a binary output.
- A number of analogue inputs can be translated to a digital out.
- 16 digital inputs can be multiplexed to 4 outputs, thus a reduction in the number of cables.

Shift Register

- An register holds n bits of digital information to be used in further operations, usually constructed with a series of flip-flops.
- The bits in a *serial-shift register* can be shifted to the right or left in n clock cycles.
- The bits in a *parallel shift register* can be simultaneously shifted in or out in one clock cycle.

One Shot

- It is often needed that a digital pulse be created when an input signal makes a transition from low to high state. - *monostable multivibrator* (one-shot).
- The pulse duration can be controlled by an RC time constant. $\Delta T \sim RC$
- When signal A transitions above $B=0$, the Q output goes high for ΔT .

