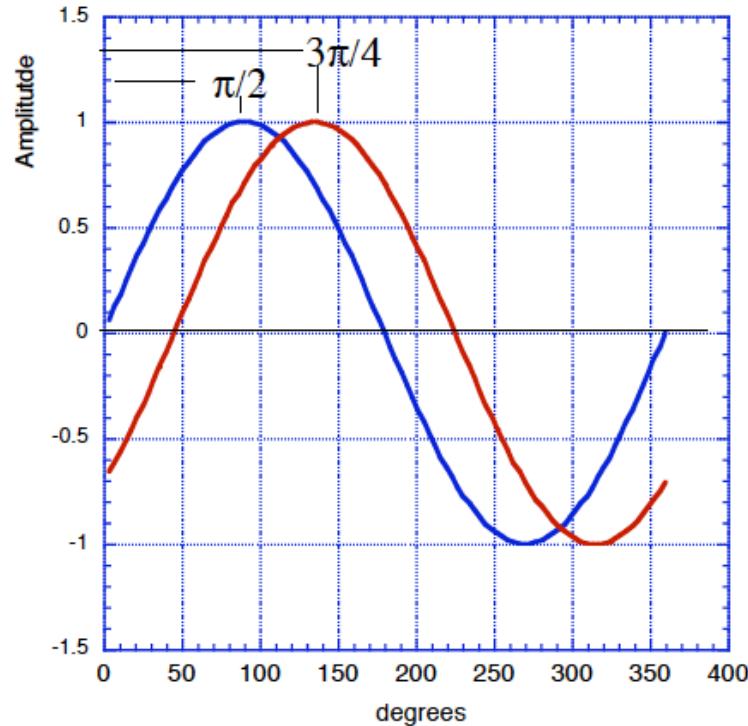


## Chapter 3 Alternating Current Circuits I

- AC Voltage and Current - Phasors
- RMS Voltage and Current
- Reactance and Impedance
- High Pass and Low Pass filters
- RLC Resonance Circuits


# Waves and Phasors



$$y(t) = A \cos(\omega t - \phi)$$

$\omega = 2\pi f$  where  $f = 1/T$

Phasor

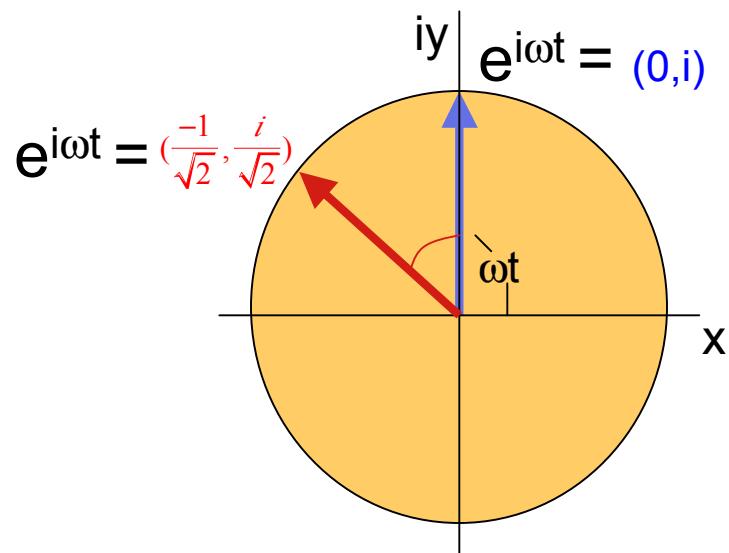

$$z = (x, iy) = |z|e^{i\pi/2} = (\cos(\pi/2), i \sin(\pi/2)) = (0, i)$$




$$z = (x, iy) = |z|e^{i\pi/4} = (\cos(3\pi/4), i \sin(3\pi/4)) = \left(\frac{-1}{\sqrt{2}}, \frac{i}{\sqrt{2}}\right)$$

## Phase Lag in an AC Circuit

In a general AC circuit (RLC) we have to consider that the voltage and current may be out of phase due to the circuit elements.

$$V(t) = V_0 \sin(\omega t) \sim V_0 e^{i\omega t}$$
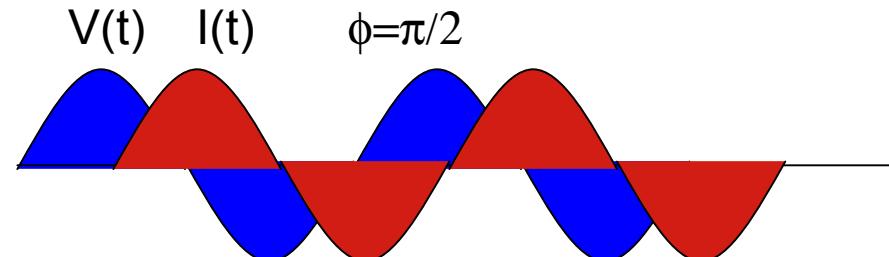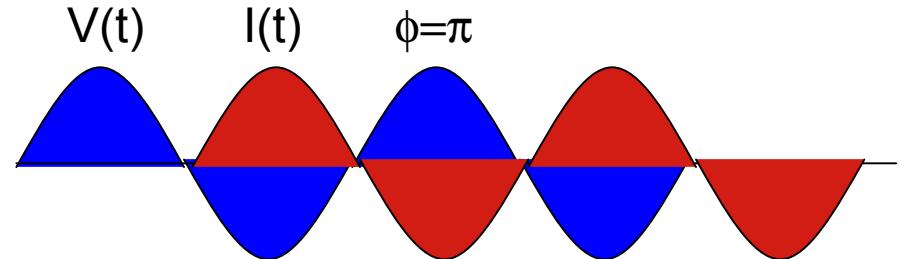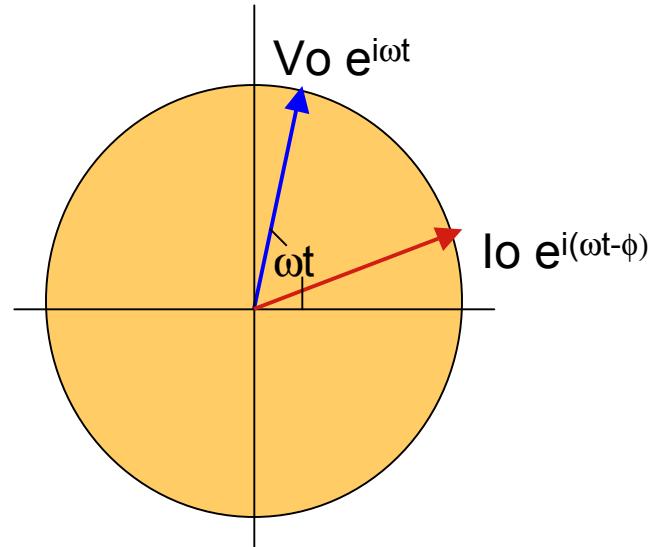
$$I(t) = I_0 \sin(\omega t - \phi) \sim I_0 e^{i(\omega t - \phi)}$$



## Average and RMS Voltage, Current, Power

$$V_{AVG} = \frac{1}{T} \int_0^T V(t) dt \quad I_{AVG} = \frac{1}{T} \int_0^T I(t) dt \quad P_{AVG} = \frac{1}{T} \int_0^T I(t)V(t) dt$$

$$(V_{RMS})^2 = \frac{1}{T} \int_0^T |V(t)|^2 dt = \frac{V_0^2}{T} \int_0^T \sin^2(\omega t) dt = \frac{Vo^2}{T} \int_0^T \frac{1 + \cos(2\omega t)}{2} dt = \frac{Vo^2}{2} + \frac{Vo^2}{2T} \frac{1}{2\omega} \cos(2\omega t) \Big|_0^T$$

$$(V_{RMS})^2 = \frac{Vo^2}{2} + \frac{Vo^2}{2T} \frac{1}{2\omega} (\cos(2\omega T) - 1) = \frac{Vo^2}{2} + \frac{Vo^2}{2T} \underbrace{\frac{1}{2\omega} \left( \cos(2\omega \frac{2\pi}{\omega}) - 1 \right)}_{=0} = \boxed{V_{RMS} = \frac{Vo}{\sqrt{2}}}$$

$$(I_{RMS})^2 = \frac{1}{T} \int_0^T |I(t)|^2 dt = \frac{Io^2}{2} \quad \boxed{I_{RMS} = \frac{Io}{\sqrt{2}}}$$

$$(P_{RMS})^2 = \frac{1}{T} \int_0^T |I(t)V(t)|^2 dt = \frac{I_0 V_0}{T} \int_0^T \sin^2(\omega t + \varphi) \sin^2(\omega t) dt$$

# Reactance, Impedance, and Phasors

Consider the general RLC circuit with  $V(t) = V_0 e^{j\omega t}$ ,  $I(t) = I_0 e^{j(\omega t - \phi)}$ :

$$V(t) = L \frac{dI}{dt} + IR + \frac{1}{C} \int I(t) dt$$

$$V(t) = I(t) \underbrace{\left( i\omega L + R + \frac{1}{i\omega C} \right)}_{\text{Reactance or Complex Impedance}} \quad \text{Ohm's Law Complex (AC) Form}$$

In any AC Circuit the Resistive, Capacitive, and Inductive elements can be replaced by their Complex Impedances!

$$Z_R = R = X_L$$

Resistive Reactance

$$1 = e^{+i \cdot 0}$$

$$\phi = 0$$

$$Z_L = i(\omega L) = +i X_L$$

Inductive Reactance

$$+i = e^{+i \pi/2}$$

$$\phi = +\pi/2$$

$$Z_C = \frac{1}{i} \left( \frac{1}{\omega C} \right) = -i X_C$$

Capacitive Reactance


$$-i = e^{-i \pi/2}$$

$$\phi = -\pi/2$$

# Magnitude and Phase

The total Resistance can be written as  $Z = R + i\left(\omega L - \frac{1}{\omega C}\right)$

corresponding to a complex number

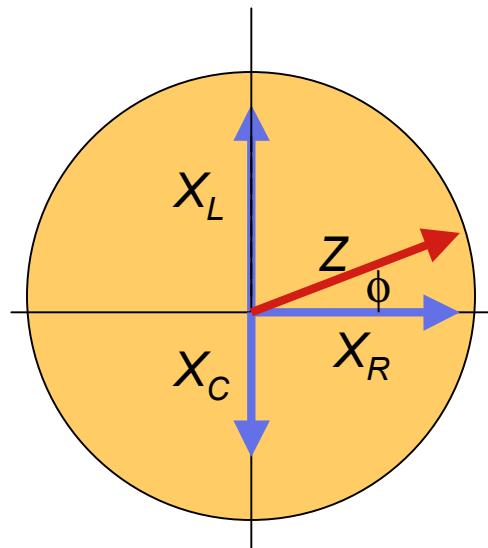

The magnitude (length) of  $Z$  is




$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

The phase angle between  $X_R$  and  $Z$

$$\phi_Z = \tan^{-1}(y/x) = \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$\cos(\phi) = \frac{R}{|Z|}$$

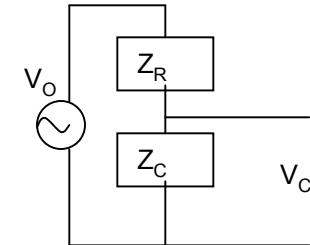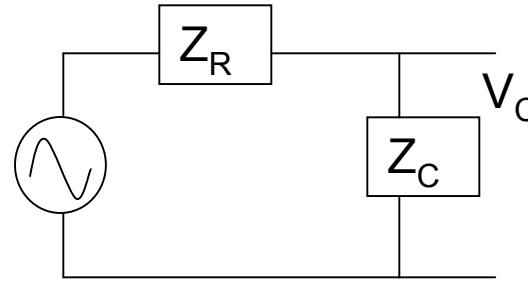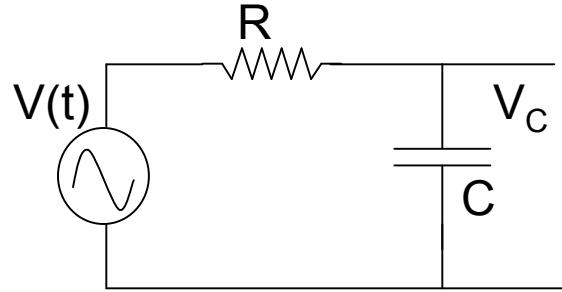
## Simple RC Circuit - Low pass Filter (1)



What is the output voltage  $V$  and phase  $\theta$  looking across the capacitor?

$$V_c = \frac{Z_c}{Z_r + Z_c} V_o e^{i\omega t} = \frac{-i/\omega C}{R - i/\omega C} V_o e^{i\omega t} \leftarrow \text{voltage divider eq} \quad \text{gain} = |V_c / V_o|$$

$$|V_c| = \sqrt{V_c V_c^*} = \sqrt{\frac{(-i/\omega C)(+i/\omega C)}{(R - i/\omega C)(R + i/\omega C)}} V_o = \frac{1/\omega C}{\sqrt{R^2 + (1/\omega C)^2}} V_o = \frac{1/\omega RC}{\sqrt{1 + (1/\omega RC)^2}} V_o$$

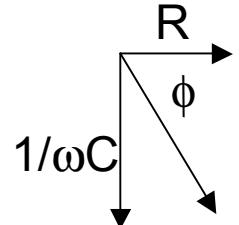

$$\text{Phase : } V_c = \overbrace{\left( \frac{-i/\omega C}{R - i/\omega C} \right)}^{=Z} \overbrace{\left( \frac{1}{R + i/\omega C} \right)}^{=1} = \overbrace{\left( \frac{X}{R^2 + (1/\omega C)^2} \right)}^{=1/\omega^2 C^2} - i \overbrace{\left( \frac{Y}{R^2 + (1/\omega C)^2} \right)}^{=R/\omega C}$$

$$\phi_c = \tan^{-1} \left( \frac{Y}{X} \right) = \tan^{-1} \left( \frac{-R/\omega C}{1/\omega^2 C^2} \right) = \tan^{-1} (-\omega RC) = \cot^{-1} \left( \frac{-1}{\omega RC} \right) = \tan^{-1} \left( \frac{1}{\omega RC} \right) - \pi/2$$

$$\text{At } \omega = 1/RC \quad \phi_c = \tan^{-1}(1) - \pi/2 = \pi/4 - \pi/2 = -\pi/4$$

## Simple RC Circuit - Low pass Filter (2)

Break Frequency occurs when  $\omega_{break} = \frac{1}{RC} \Rightarrow |V_C| = \frac{1}{\sqrt{2}} V_o = 0.707 V_o$

$$|V_C| = \frac{1}{\sqrt{1 + (\omega RC)^2}} V_o \quad f_{break} = \underbrace{\frac{1}{2\pi RC}}_{\text{break frequency}}$$

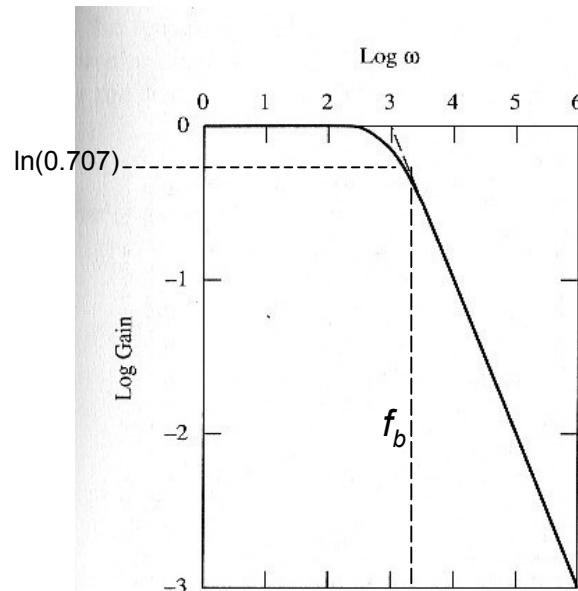


FIGURE 3.9A Gain versus frequency for the circuit of Figure 3.8 (low pass).


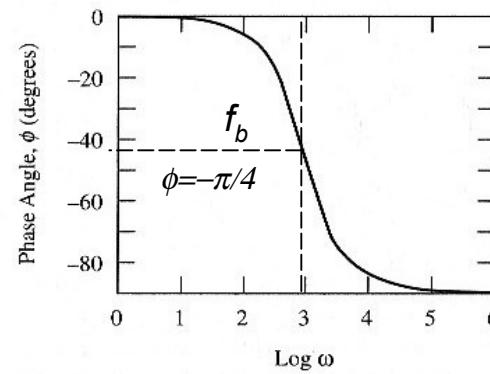
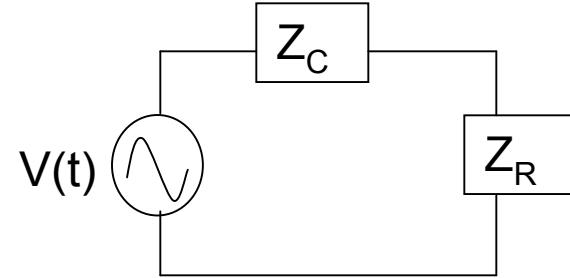


FIGURE 3.9B Phase angle versus frequency for the circuit of Figure 3.8 (low pass).

## Simple RC Circuit - High Pass Filter

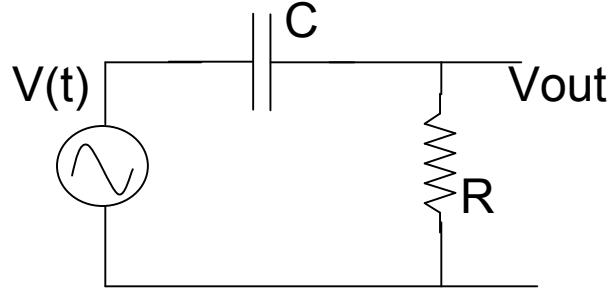

What is the output voltage  $V_R$  and phase  $\phi_R$  looking across the resistor?


$$V_R = \left( \frac{Z_R}{Z_R + Z_C} \right) V_O e^{j\omega t} = \frac{R}{(R - j/\omega C)} V_O e^{j\omega t}$$

$$|V_R| = \sqrt{V_R V_R^*} = \sqrt{\frac{R^2}{(R - j/\omega C)(R + j/\omega C)}} V_O = \frac{R}{\sqrt{R^2 + (1/\omega C)^2}} V_O = \frac{\omega R C}{\sqrt{1 + (\omega R C)^2}} V_O$$

$$gain = V_R / V_O = \frac{\omega R C}{\sqrt{1 + (\omega R C)^2}}$$

$$Phase : V_R = \left( \frac{R^2}{R^2 + (1/\omega C)^2} \right) + j \left( \frac{R/\omega C}{R^2 + (1/\omega C)^2} \right) \Rightarrow \phi_R = \tan^{-1} \left( \frac{Y}{X} \right) = \tan^{-1} \left( \frac{1}{\omega R C} \right)$$
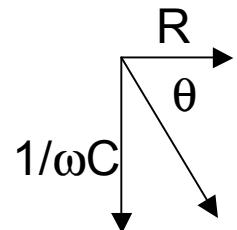
$$At \quad \omega = 1/RC \quad \phi_R = \tan^{-1}(1) = \pi/4$$




## Simple RC Circuit - High Pass Filter (2)


$$|V_R| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} V_o$$

$$f_{break} = \underbrace{\frac{1}{2\pi RC}}_{break frequency}$$
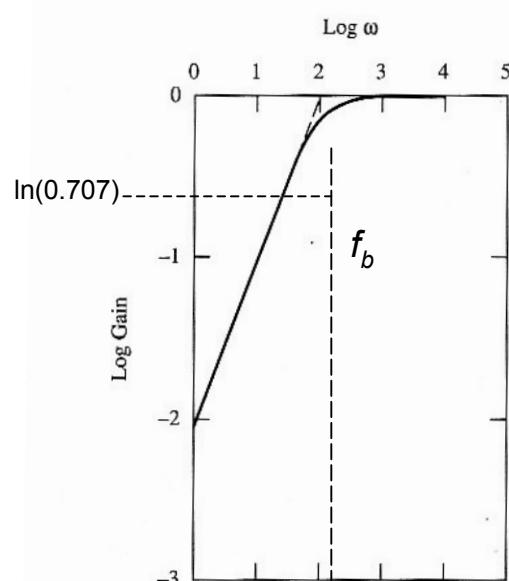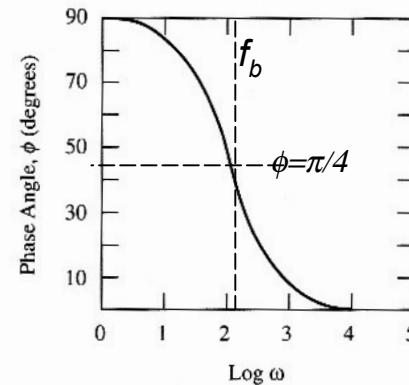
$$|V_R| = \frac{1}{\sqrt{2}} V_o = 0.707 V_o$$



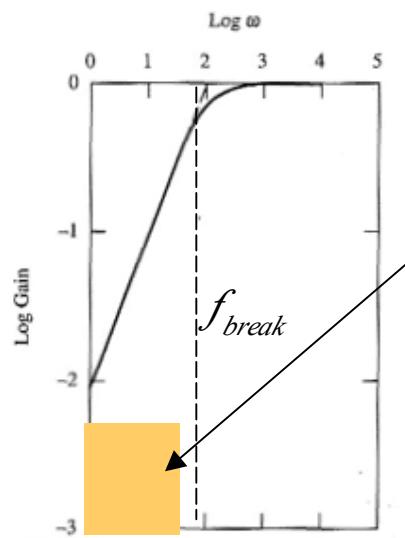


**FIGURE 3.11A** Gain versus frequency for the circuit of Figure 3.10 (high pass).

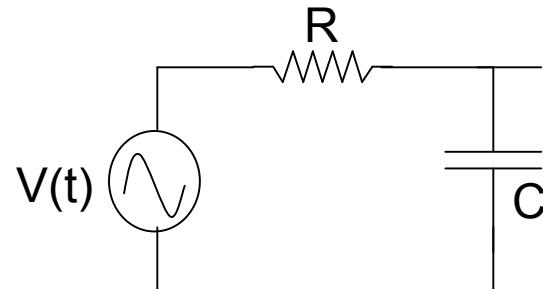

**FIGURE 3.11B** Phase angle versus frequency for the circuit of Figure 3.10 (high pass).


# Differentiator and Integrator Connection

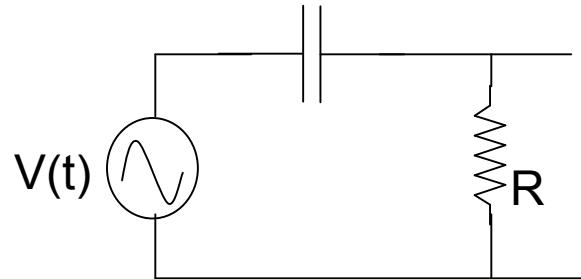

**FIGURE 3.11A** Gain versus frequency for the circuit of Figure 3.10 (high pass).

$$V_R = \underbrace{R dq / dt}_{\text{differentiator}}$$

$RC \ll T$   
 $1/T \ll 1/RC$   
 $f \ll 1/RC$   
 $f < f_{break}$

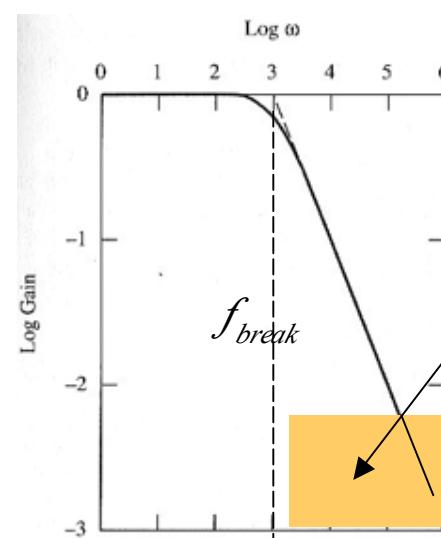



**FIGURE 3.9A** Gain versus frequency for the circuit of Figure 3.8 (low pass).

$$V_C = \underbrace{\frac{1}{C} \int i dt}_{\text{integrator}}$$

$RC >> T$   
 $1/T >> 1/RC$   
 $f >> 1/RC$   
 $f > f_{break}$

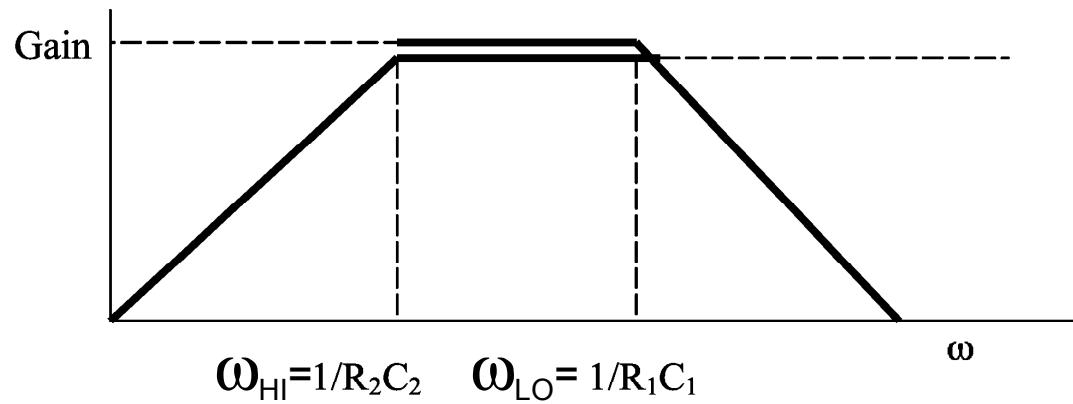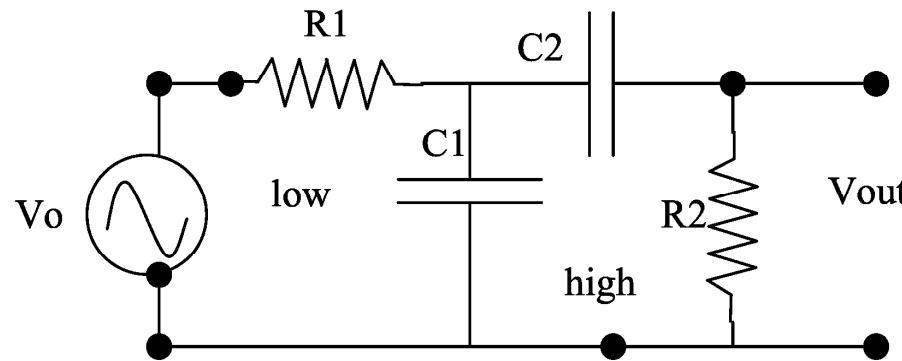
## Band Pass or Notch Filter

Band Pass Filter - Combination of Low and High Pass



# RLC Circuit

## RLC Circuit

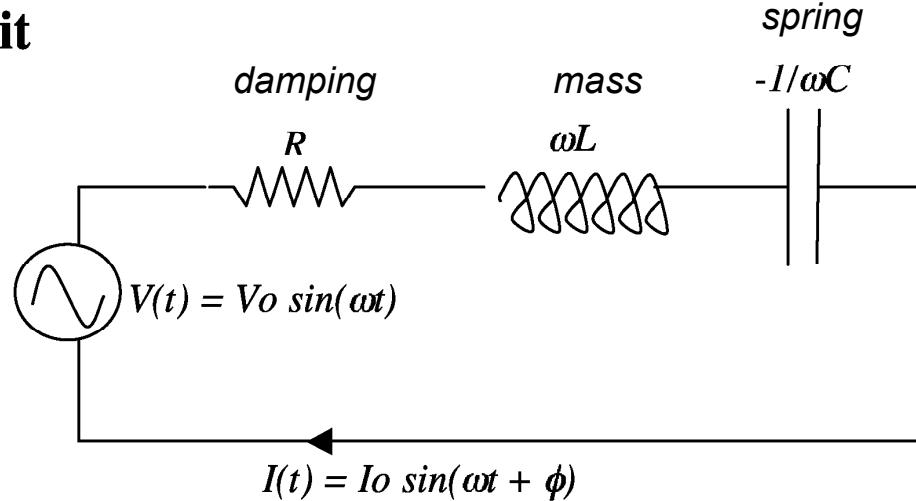

$$Z = R + i(\omega L - 1/\omega C)$$

$$|Z| = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

$$I(t) = V(t)/|Z|$$

$$|I(t)| = V(t) / \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

$$V_R = I(t) R = V(t) R / |Z|$$

$$\phi = \tan^{-1} \{(\omega L - 1/\omega C)/R\}$$

$$V_L = I(t) e^{+i\pi/2} \{(\omega L) / |Z|\}$$

$$V_C = I(t) e^{-i\pi/2} \{(1/\omega C) / |Z|\}$$


# Resonance Condition and Q-factor

$$|I(t)| = V(t) / \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

When  $\omega_0 L = 1/\omega_0 C$  the current flowing in the circuit and Gain reach a maximum.  $\rightarrow \omega_0^2 = 1/LC$


$$f_0 = 1/2\pi \sqrt{LC}$$

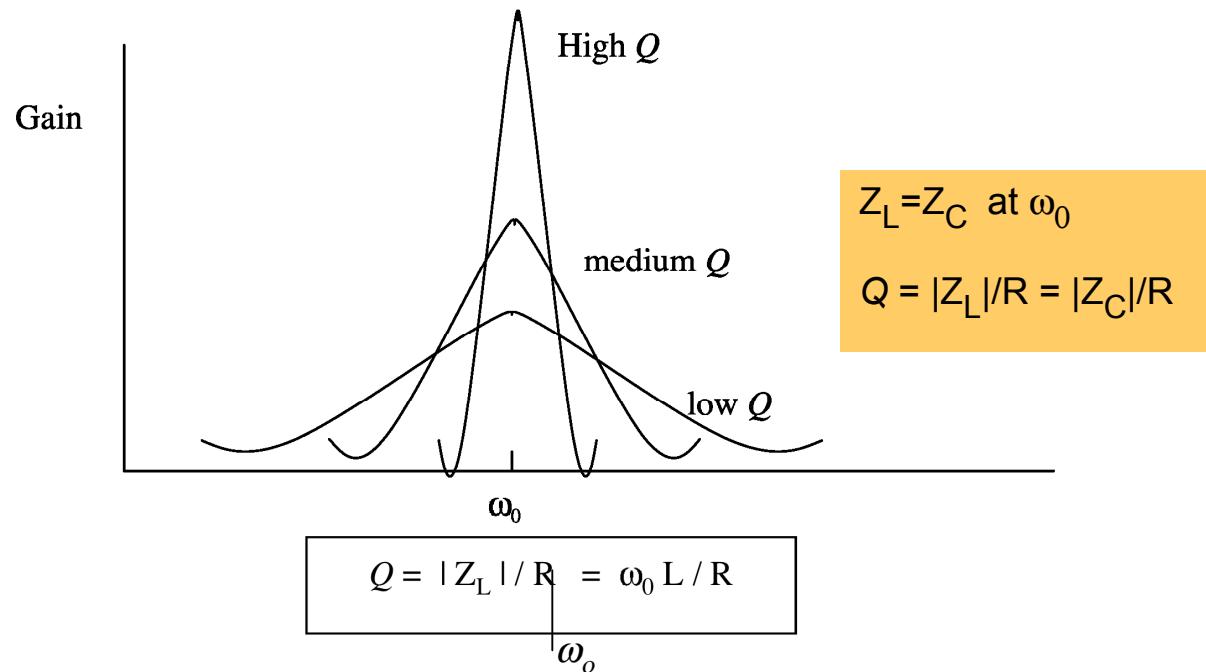The  $Q$ -factor of the circuit is defined as the  $Q \sim G_{peak}/\Delta G \sim (maxAmplitude)/(Width at half max)$



# Power in AC Circuits

## Power in AC Circuits

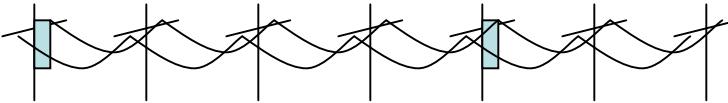

$$P(t) = I(t) V(t)$$

*Instantaneous Power*

$$P_{AVG} = 1/T \int_0^T I(t)V(t)dt$$

*Average Power*

$$= I_o V_o / T \int_0^T \sin(\omega t) \sin(\omega t - \phi) dt$$

$$= 1/2 I_o V_o \cos(\phi) = I_o / \sqrt{2} V_o / \sqrt{2} \cos(\phi) = I_{RMS} V_{RMS} \cos(\phi)$$

$$P_{AVG} = I_o / \sqrt{2} V_o / \sqrt{2} \cos(\phi)$$

$$\cos(\phi) = R / \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

*RLC Circuit*

Maximum power transfer to the circuit occurs when  $\cos(\phi) = 1$  or at resonance  $\rightarrow \omega_0 L = 1/\omega_0 C$

If the load is strongly inductive (motors, compressors, etc ) then capacitors are added to the circuit the by power companies to create a more favorable power transfer.

# Decibel Scale

## DECIBEL SCALE

When measuring power gain and voltage gain in an amplifier or circuit we often use the decibel scale.

### Power

$$P_{db} = 10 \log(P_{out}/P_{in})$$

### Voltage

$$V_{db} = 20 \log_{10}(V_{out}/V_{in}) = 20 \log_{10}(\text{gain})$$

### **Sound Power**

- Near total silence - 0 dB
- A whisper - 15 dB
- Normal conversation - 60 dB
- A lawnmower - 90 dB
- A car horn - 110 dB
- A rock concert or a jet engine - 120 dB
- A gunshot or firecracker - 140 dB

### V<sub>db</sub> at the Break Frequency

At the breaking frequency the gain  $V_{out}/V_{in}$  drops by a factor of  $1/\sqrt{2}$ . This is called the -3 dB point. Can you justify this remark?