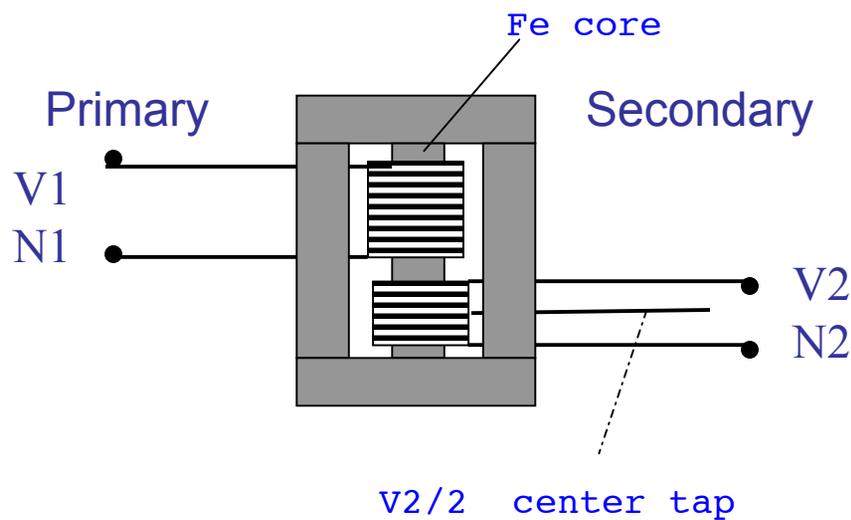


# Chapter 4 - AC Circuits II

- Transformers and Impedance Matching
- Transmission Lines
- Fourier Waveforms

## • Transformers- VAC



$V1/V2 = N1/N2$  *voltage ratio = winding ratio*

$I1 V1 = I2 V2$  *conservation of energy*

$I1/I2 = V2/V1 = N2/N1$

$V=I Z$  *Ohms AC Law*

$Z1/Z2 = (V1/I1) / (V2/I2) = (I2/I1)(V1/V2)$

$Z1/Z2 = (N1/N2)^2$  *Impedance Matching*

Transformer core enhances performance

$$L \sim \mu_{Fe}(\omega) \mu_o \times L_{air}$$

# Impedance matching - theory

$$P = I V = I^2 R = [V/(r+R)]^2 R$$

*Maximum power is delivered at what value of R?*


$$dP/dR = -2V^2R(r+R)^{-3} + V^2/(r+R)^{-2} = 0$$

$$-2V^2R(r+R)^{-3} + V^2/(r+R)^{-2} = 0$$


$$R/(r+R) = 1/2$$

$$R = 1/2r + 1/2R \rightarrow R = r !$$

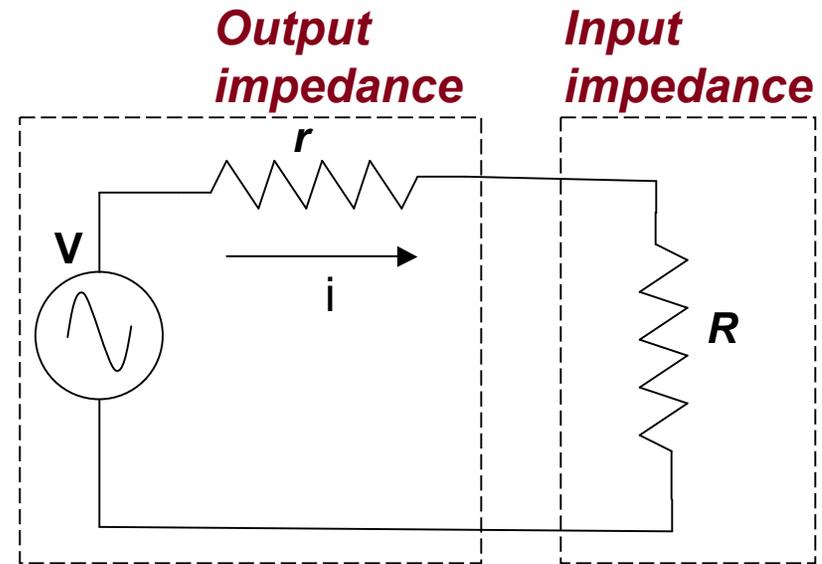*Maximum power is transferred when Output impedance matches Input impedance!*



# Impedance matching - w transformer

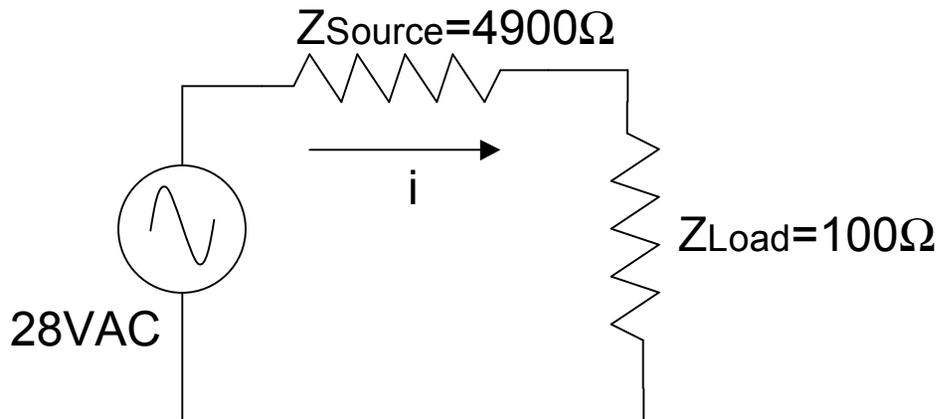


## Without Transformer

$$i = 28/(4900+100) = 5.6\text{mA}$$

$$V_L = (100/5000)28\text{V} = 0.56\text{V}$$

$$P_L = i V_L = 3.1 \text{ mW}$$

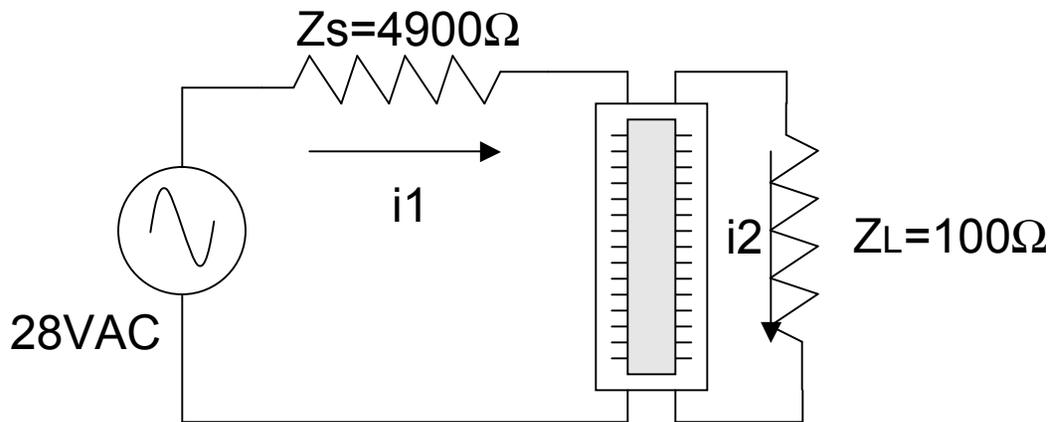

## With Transformer

$$Z_1/Z_2 = (N_1/N_2)^2$$

$$N_1/N_2 = \text{sqrt}(4900/100)=7$$

$$V_2 = (1/7)V_1 = (1/7) 28 = 4\text{V}$$


$$I_2 = 4\text{V}/100\Omega = .040\text{A}$$

$$P_2 = (.040\text{A})4\text{V} = 160\text{mW} !$$

$$I_1 = i_2(N_2/N_1)=.0057\text{A}$$

$$P_1 = (.0057\text{A})28\text{V} = 160\text{mW}$$


# Transmission Lines

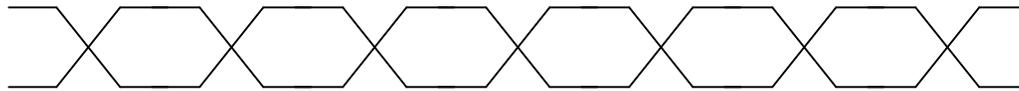

Twisted pair  
( $Z \sim 100\Omega$ )



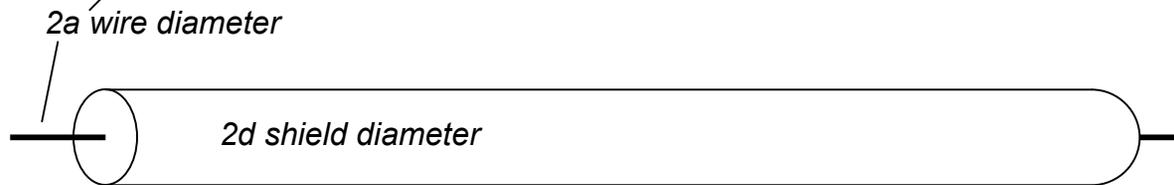Parallel conductor  
( $Z \sim 90\Omega$ )




CoAxial  
( $Z \sim 50-100\Omega$ )

$$Z_{parallel} = \left( \frac{\mu\mu_o}{\pi^2\epsilon\epsilon_o} \right)^{1/2} \ln\left( \frac{2d}{a} \right)$$

$$Z_{coax} = \left( \frac{\mu\mu_o}{\pi^2\epsilon\epsilon_o} \right)^{1/2} \ln\left( \frac{b}{a} \right)$$

<http://www.eeweb.com/toolbox/wire-over-plane-inductance/>

# Transmission Lines

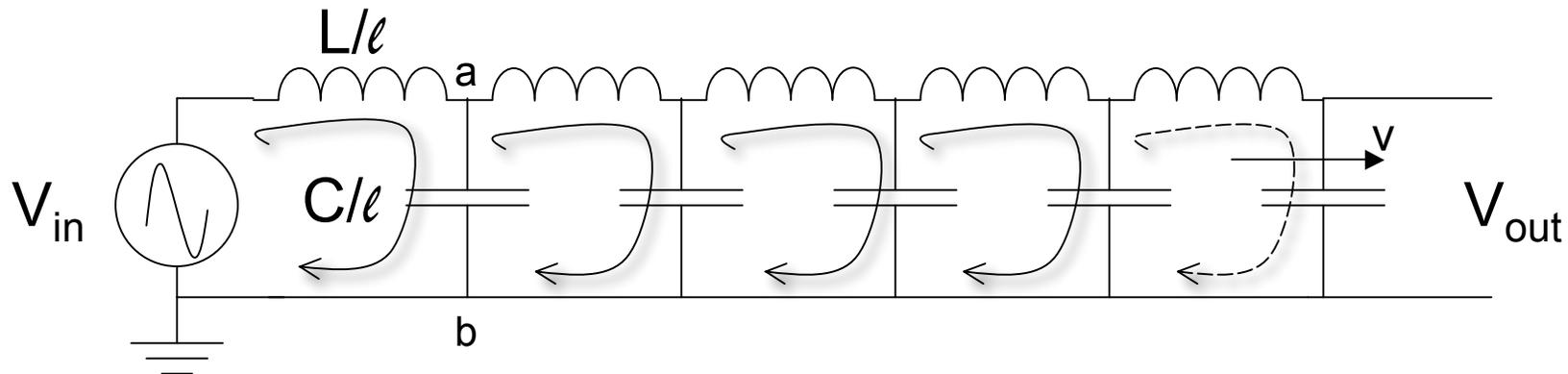

- We often use a cable or transmission line to transfer AC signals.


- The cable can be modeled as a series  $L=L/l$  and parallel  $C=C/l$  to ground. Sometimes a series  $R=R/l$  is also included.

$$V_{ab} = \frac{1/\omega C}{\sqrt{(1/\omega C)^2 + (\omega L)^2}} V_{in} = \frac{1}{\sqrt{1 + (\omega^2 LC)^2}} V_{in} \quad V_{out} = \left( \frac{1}{\sqrt{1 + (\omega^2 LC)^2}} \right)^N V_{in}$$

- Since  $V_{ab} \sim 1$  for low frequencies ( $\omega \rightarrow 0$ ) generally signal propagation is only a concern at higher frequency.

- Resistance of the line will attenuate the signal at all frequencies!

# Transmission Line Theory(1)

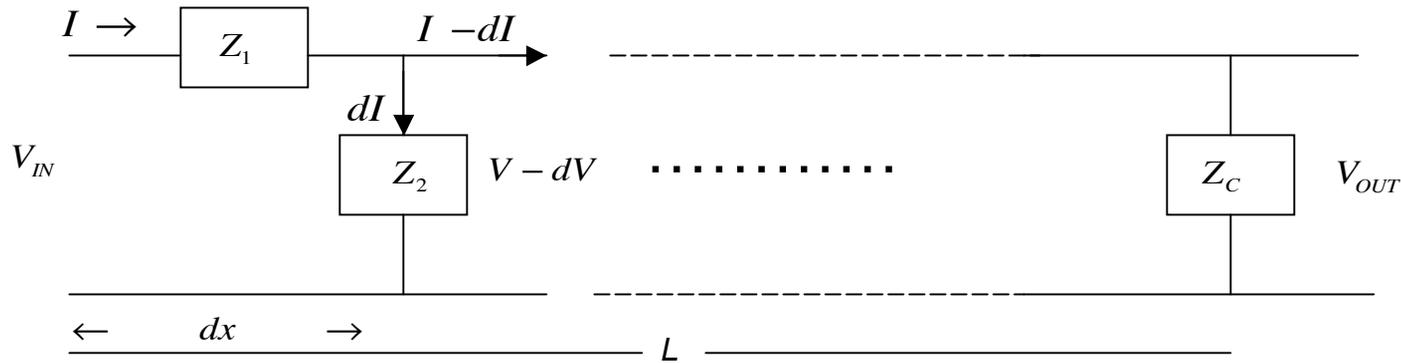

$$1) \quad dV/dx = -I Z_1 \quad \rightarrow \quad \frac{d^2V}{dx^2} = -Z_1 \frac{dI}{dx} = \frac{Z_1}{Z_2} V \quad \rightarrow \quad \underline{V(x) = A e^{-\sqrt{Z_1/Z_2}x} + B e^{+\sqrt{Z_1/Z_2}x}}$$

$$2) \quad dI/dx = -\frac{V}{Z_2} \quad \rightarrow \quad \frac{d^2I}{dx^2} = -Z_1 \frac{dV}{dx} = \frac{Z_1}{Z_2} I \quad \rightarrow \quad \underline{I(x) = C e^{-\sqrt{Z_1/Z_2}x} - D e^{+\sqrt{Z_1/Z_2}x}}$$

By using 1)  $I = \frac{1}{Z_1} \frac{dV}{dx} \rightarrow \underline{I(x) = \frac{1}{\sqrt{Z_1 Z_2}} (A e^{-\sqrt{Z_1/Z_2}x} - B e^{+\sqrt{Z_1/Z_2}x})}$  where  $\underline{Z_C = \sqrt{Z_1 Z_2}}$  characteristic impedance

$$\begin{aligned} Z_1 &= R_1 / \ell + i\omega L / \ell \\ Z_2 &= R_2 / \ell + i\omega (C / \ell) \end{aligned}$$

3) Assume we terminate the transmission at  $x = L$  line with  $Z_C$ .

$$V(L) = A e^{-\sqrt{Z_1/Z_2}L} + B e^{+\sqrt{Z_1/Z_2}L} \quad \text{and} \quad I(L) = \frac{1}{Z_C} (A e^{-\sqrt{Z_1/Z_2}L} - B e^{+\sqrt{Z_1/Z_2}L})$$

$$Z(L) = \frac{V(L)}{I(L)} = Z_C \quad \rightarrow \quad B = 0$$

$$4) \quad V(0) = V_{IN} \quad \rightarrow \quad \underline{V(x) = V_{IN} e^{-\sqrt{Z_1/Z_2}x} \quad \text{and} \quad I(x) = \frac{V_{IN}}{Z_C} e^{-\sqrt{Z_1/Z_2}x}}$$

$$\begin{aligned} \text{Input Impedance} &= Z_C \text{ independent of } L! \\ \underline{Z_{IN} = \frac{V(0)}{I(0)} = Z_C} \end{aligned}$$

## Transmission Line Theory(2)



- The characteristic impedance of a transmission line is


$$Z_{\text{Characteristic}} = Z_C = \sqrt{Z_1 Z_2}$$

- The input impedance of a transmission line is independent of  $L$  terminated if terminated in characteristic impedance is  $Z_C$ .

- The signal speed of propagation

$$v = 1 / \sqrt{L'C'} = c / \sqrt{\mu\epsilon} = c / n$$

# Speed of Signal Propagation

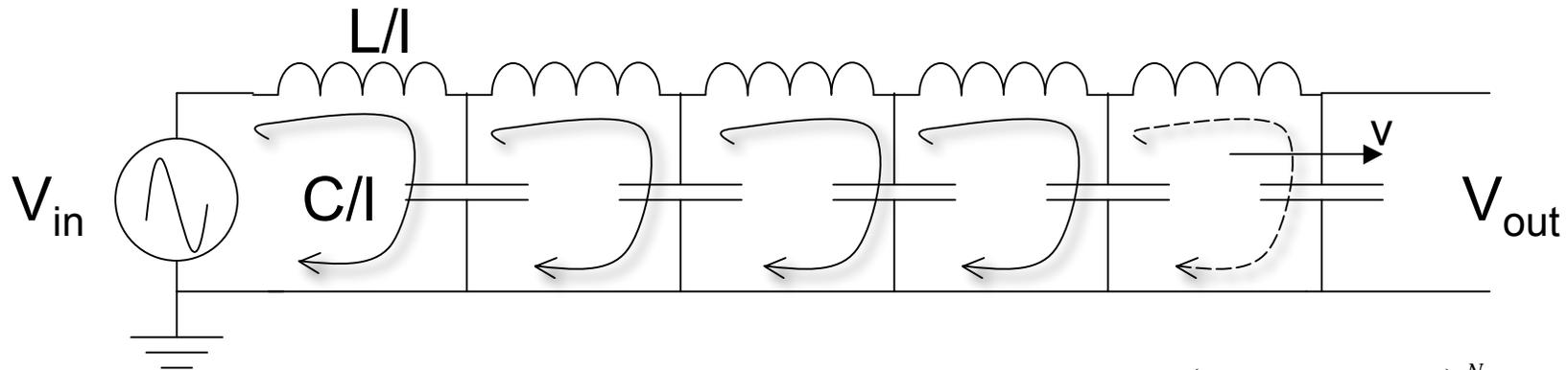

$$V_{ab} = \frac{1/\omega C}{\sqrt{(1/\omega C)^2 + (\omega L)^2}} V_{in} = \frac{1}{\sqrt{1 + (\omega^2 LC)^2}} V_{in} \quad V_{out} = \left( \frac{1}{\sqrt{1 + (\omega^2 LC)^2}} \right)^N V_{in}$$

The LC circuit rings when  $\omega^2 LC = 1$  or  $\omega = 1/\sqrt{LC}$


This is the optimum condition for signal transport.

Using the ringing period as  $T = \sqrt{LC}$

$$\omega = 1/\sqrt{LC} \Rightarrow 1/v = \overbrace{\sqrt{LC}}^T / l = \sqrt{(L/l)(C/l)}$$

$$v = 1/\sqrt{L'C'} = c/\sqrt{\mu\epsilon} = c/n$$

# Reflection Coefficient

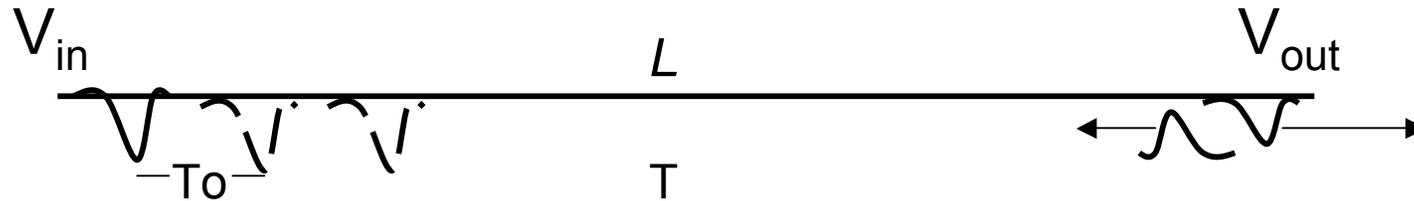

$$f = 1/T_0 = \text{signal frequency}$$

If a transmission line of characteristic impedance  $Z_c$  is terminated with impedance  $Z \neq Z_c$  a reflected signal will develop!

$$K = A/A_0 = [(Z - Z_c)/(Z + Z_c)] \quad \text{reflection coef} \quad (\text{If } Z = Z_0 \text{ then no reflection!})$$

If  $T \sim 2(L/v) = \text{transit time for } 2L \text{ reflection}$  then signal cancellation likely.

If  $T \ll T_0$  then no termination necessary.

If  $T \sim T_0$  then cancellation or distortion and termination necessary.


***Will a 100 MHz signal traveling down a 2 m RG58/U 50Ω cable need termination?***

***$T_0 = 10 \text{ ns}$      $T = [2(2\text{m})/2 \times 10^8 \text{ m/s}] = 20 \text{ ns}$  :    Yes cable should be terminated in 50Ω!***
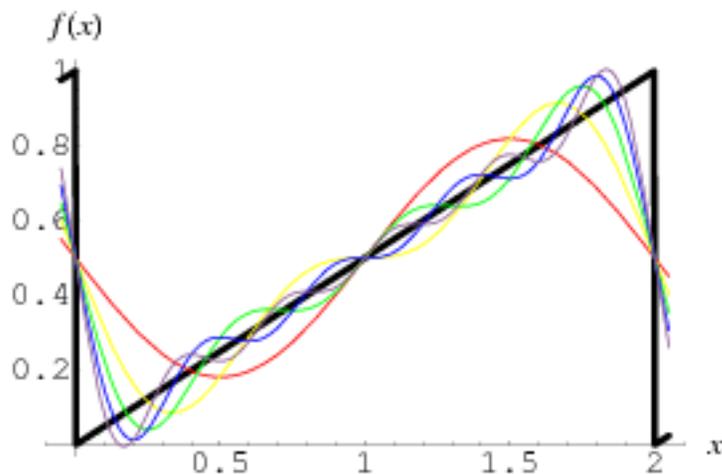
# Complex Signal and Fourier Decomposition

$$V(t) = \underbrace{\frac{A_0}{2}}_{DC} + \underbrace{\sum A_n \sin(2n\pi t / T) + \sum B_n \cos(2n\pi t / T)}_{AC} \quad \omega_n = 2n\pi f$$


*Fourier – Any waveform  $V(t)$  can be decomposed in to sine and cosine waves.*



*Sawtooth Wave*

$$A_n = \frac{1}{n\pi} \quad n = 1, 3, 5, \dots \text{ odd}$$

$$B_n = 0$$

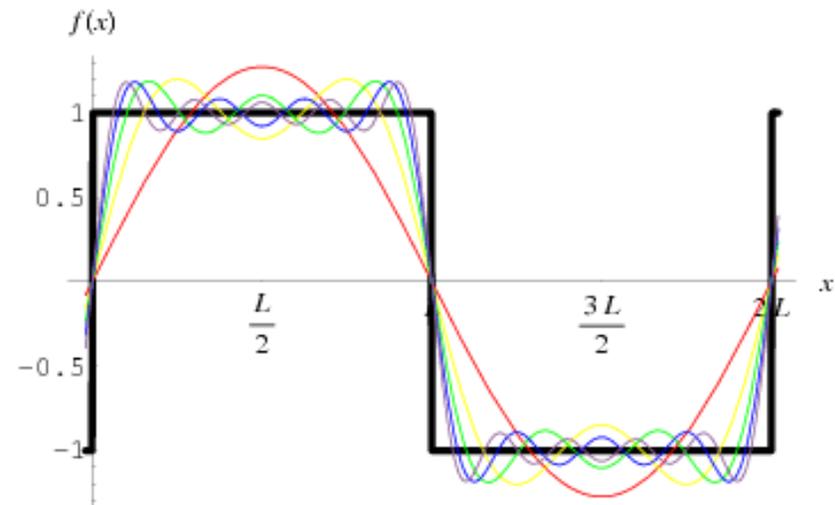


*Square Wave*

$$A_n = \frac{4}{n\pi} \quad n = 1, 3, 5, \dots \text{ odd}$$

$$B_n = 0$$
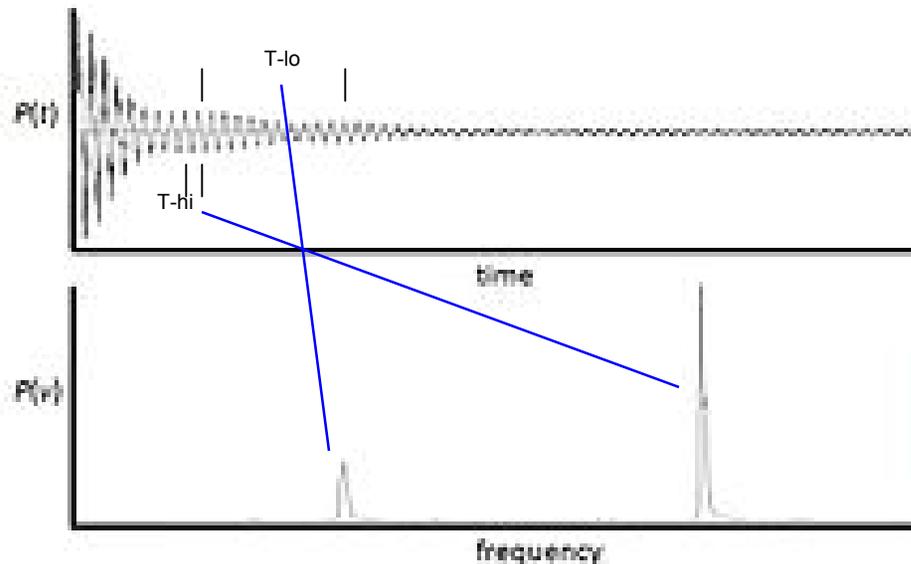
# Fourier Decomposition- FFT

- Fast Fourier Transform (FFT) is an algorithm to compute a discrete Fourier transform. This signal  $P(t)$  is decomposed into a high frequency and low frequency  $P(v)$ .



- Noise and signal can be separated in the frequency domain