
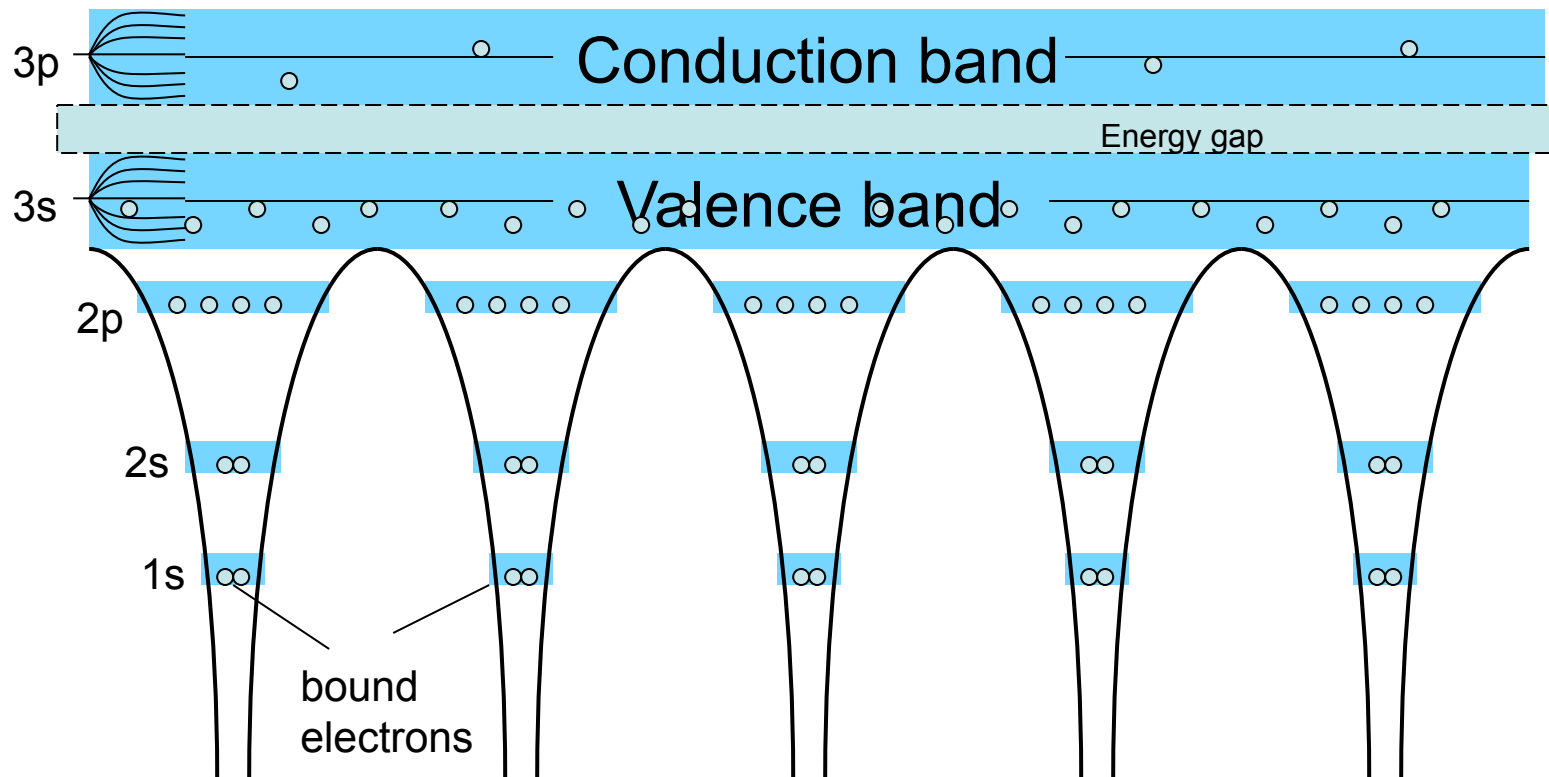


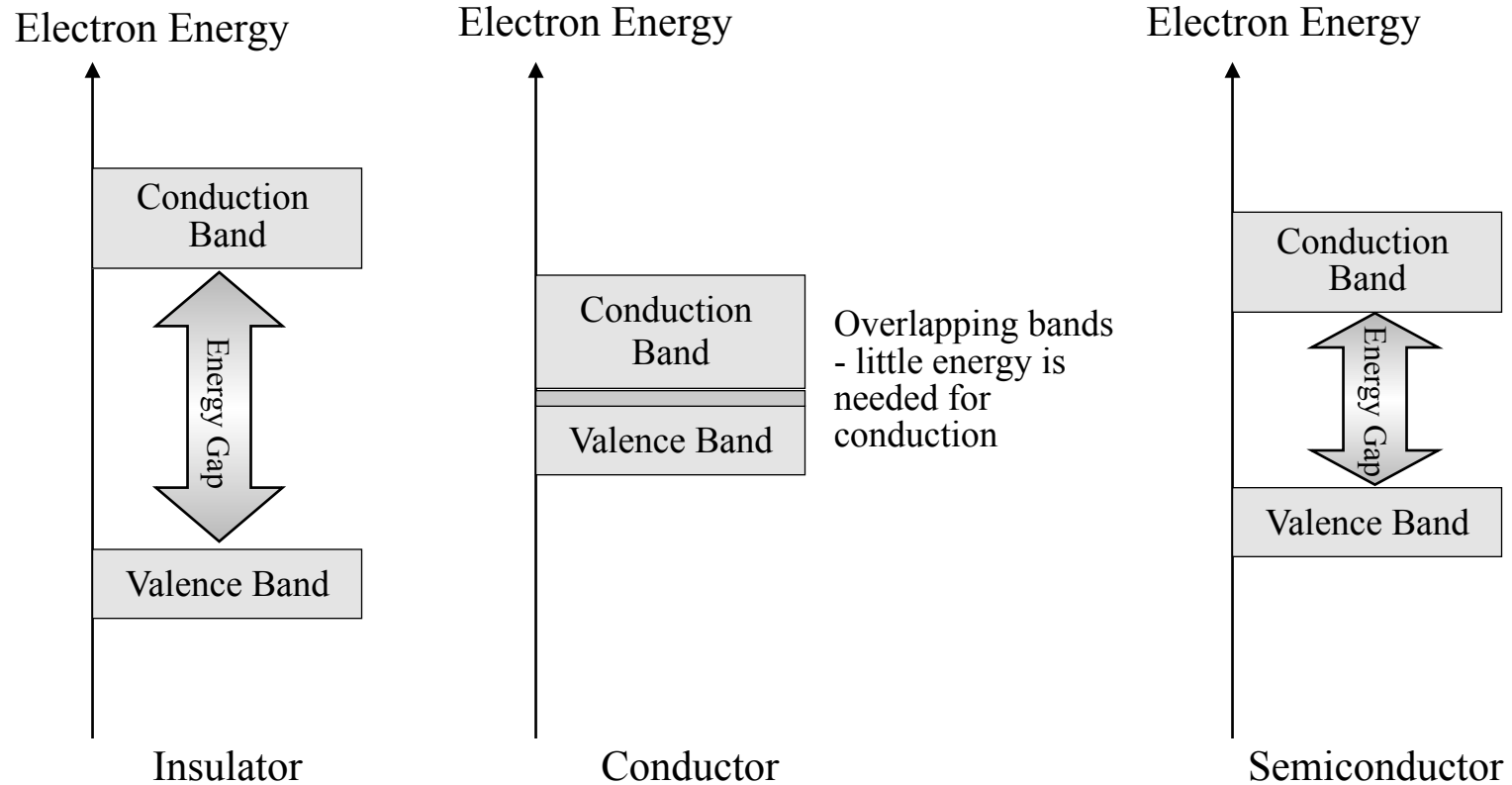Chapter-5: Introduction to Semi-Conductors and Diode Circuits



When atoms form a crystalline structure (metals, semiconductors,) the valence electrons loose their attraction to a local atom and form an band of ~equivalent charges- **valence band**. The **conduction band** lies within or above the valence band.

Energy Bands




IA										VIIIA									
1 1.008 H Hydroge										2 4.002 6 He Heliu									
IIA										IIIA IVA VA VIA VIIA									
3 6.939 Li Lithiu										4 9.01 2 Be Berylliu									
Transition Metals										5 10.81 B Boron									
11 22.98 9 Na Sodiu										12 24.312 Mg Magnesium									
IIIB IVB VB VIB VIIB VIIIB IB IIB										6 12.01 1 C Carbon									
19 39.10 2 K Potassiu										20 40.08 Ca Calcium									
21 44.95 6 Sc Scandium										22 47.90 Ti Titaniu									
23 50.94 2 V Vanadium										24 51.99 6 Cr Chromiu									
25 54.93 8 Mn Manganese										26 55.84 7 Fe Iron									
27 58.93 3 Co Cobalt										28 58.71 Ni Nickel									
29 63.54 Cu Coppe										30 65.37 Zn Zinc									
31 69.72 Ga Galliu										32 72.59 Ge Germaniu									
33 74.92 As Arseni										34 78.96 Se Seleniu									
35 79.90 9 Br Bromin										36 83.80 Kr Krypton									
37 85.47 Rb Rubidiu										38 87.62 Sr Strontium									
39 88.90 5 Y Yttrium										40 91.22 Zr Zirconium									
41 92.90 6 Nb Niobium										42 95.94 Mo Molybde-num									
43 99 Tc Technitium										44 101.0 7 Ru Ruthenium									
45 102.91 Rh Rhodiu										46 106.4 Pd Palladium									
47 107.8 7 Ag Silver										48 112.4 Cd Cadmium									
49 114.8 2 In Indium										50 118.6 9 Sn Tin									
51 121.7 5 Sb Antimony										52 127.6 0 Te Tellurium									
53 126.90 4 I Iodine										54 131.3 0 Xe Xenon									
55 132.90 Cs Cesium										56 137.34 Ba Barium									
57 138.91 La Lanthanum										58 140.91 Ce Cerium									
59 140.91 Pr Praseodym										60 140.91 Nd Neodym									
61 140.91 Pm Promethium										62 140.91 Sm Samarium									
63 140.91 Eu Europium										64 140.91 Gd Gadolinium									
65 140.91 Tb Terbium										66 140.91 Dy Dysprosium									
67 140.91 Ho Holmium										68 140.91 Er Erbium									
69 140.91 Tm Thulium										70 140.91 Yb Ytterbium									
71 140.91 Lu Lutetium										72 140.91 Hf Hafniu									
73 180.95 Ta Tantalum										74 183.85 W Tungsten									
75 186.2 Re Rhenium										76 190.2 Os Osmium									
77 192.2 Ir Iridium										78 195.09 Pt Platinum									
79 196.967 Au Gold										80 200.59 Hg Mercury									
81 204.37 Tl Thallium										82 207.19 Pb Lead									
83 208.98 Bi Bismuth										84 210 Po Poloniu									
85 210 At Astatine										86 222 Rn Radon									
87 223 Fr Francium										88 226 Ra Radium									
89 227 Ac Actiniu										90 227 Th Thorium									
91 227 Pa Protactiniu										92 227 U Uranium									
93 227 Np Neptunium										94 227 Pu Plutonium									
95 227 Am Americium										96 227 Cm Curium									
97 227 Bk Berkelium										98 227 Cf Californium									
99 227 Es Einsteinium										100 227 Fm Fermium									
101 227 Md Mendelevium										102 227 No Nobelium									
103 227 Lr Lawrencium										104 227 Rf Rutherfordium									
105 227 Ha Hassium										106 227 Sg Seaborgium									
107 227 Uns										108 227 Uno									
109 227 Une										110 227 Uun									
Nonmetals										Metalloids									

Group IVA Elemental Semiconductors


Carbon	C	6	<ul style="list-style-type: none"> •Very Expensive diamond •Band Gap Large: 6V •Difficult to produce without high contamination
Silicon	Si	14	<ul style="list-style-type: none"> •Cheap •Ultra High Purity •Oxide is amazingly perfect for IC applications
Germanium	Ge	32	<ul style="list-style-type: none"> •High Mobility (good) •High Purity Material (good) •Oxide is porous to water/hydrogen (disasterous!)
Tin	Sn	50	<ul style="list-style-type: none"> •Only “White Tin” is semiconductor •Converts to metallic form under moderate heat
Lead	Pb	82	<ul style="list-style-type: none"> •Only “White Lead” is semiconductor •Converts to metallic form under moderate heat

Covalent Bonding of Pure Silicon

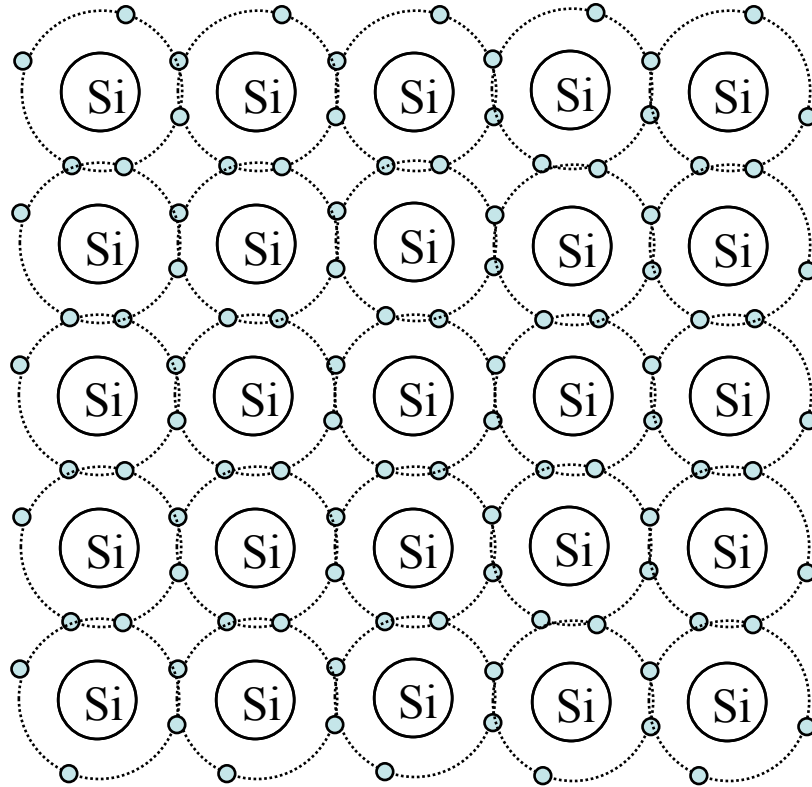


Silicon atoms share valence electrons
to form insulator-like bonds.

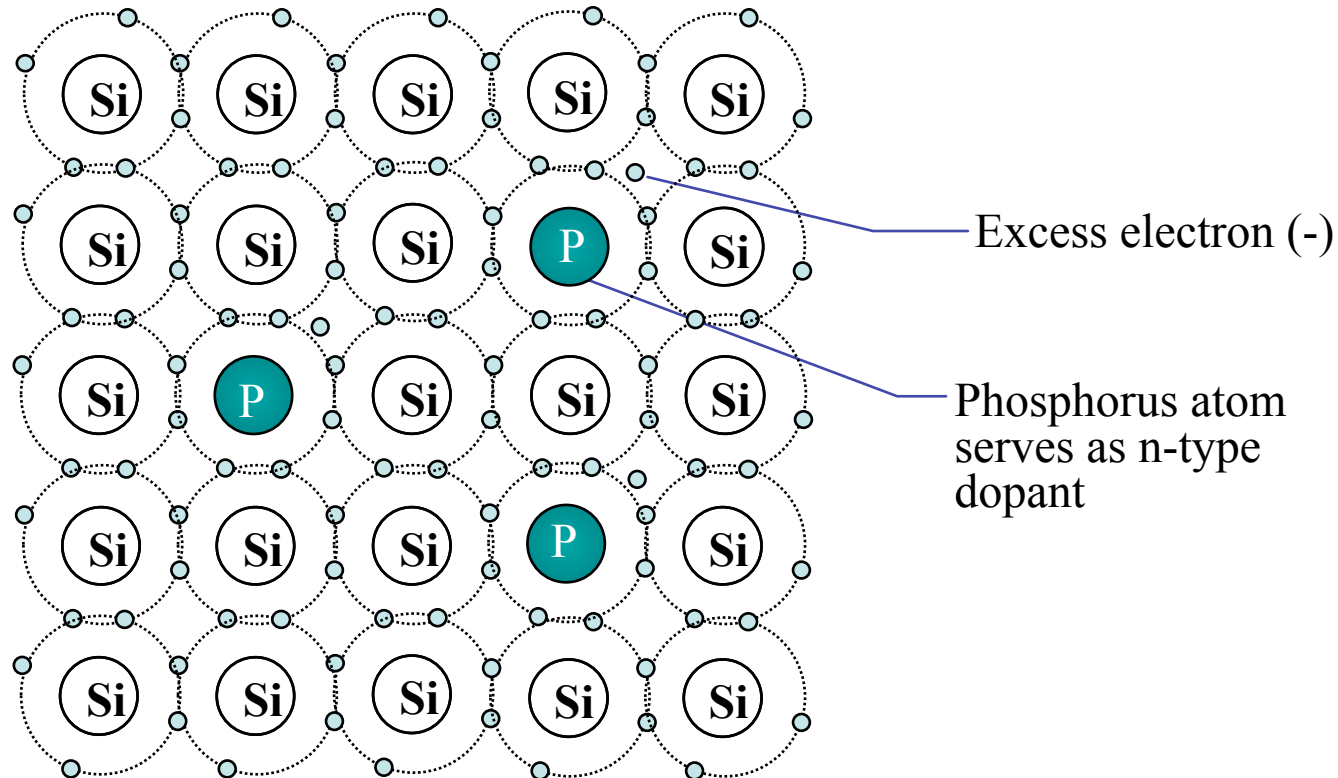Electrons in N-Type Silicon with Phosphorus Dopant



Donor atoms provide excess electrons to form n-type silicon.

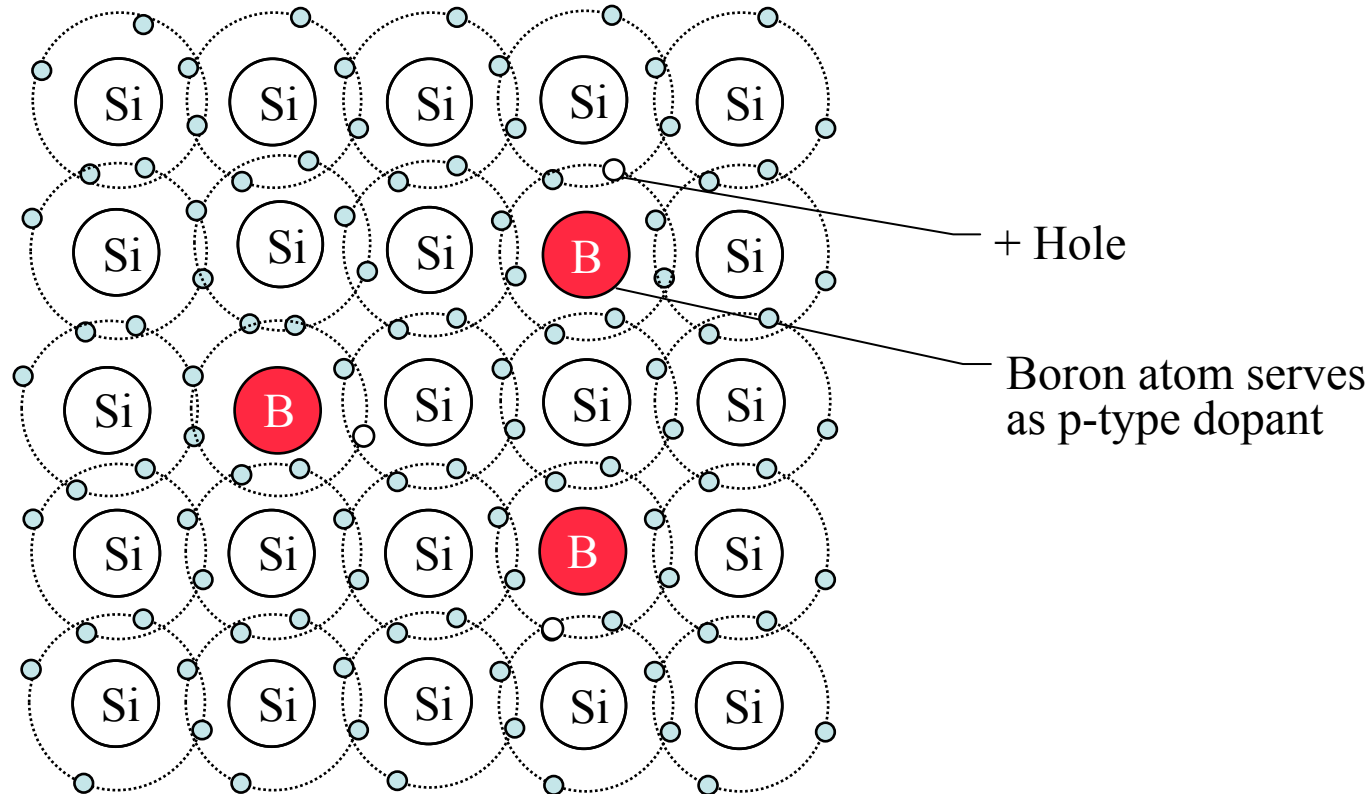Holes in p-Type Silicon with Boron Dopant




Acceptor atoms provide a deficiency of electrons to form p-type silicon.


Silicon Dopants

Acceptor Impurities	Semiconductor	Donor Impurities
Group III (p-type)	Group IV	Group V (n-type)
<u>Boron 5</u> <i>Aluminum 13</i> Gallium 31 Indium 49	Carbon 6 <u>Silicon 14</u> Germanium 32	<i>Nitrogen 7</i> <u>Phosphorus 15</u> <u>Arsenic 33</u> Antimony 51


Conduction in n and p-Type Silicon

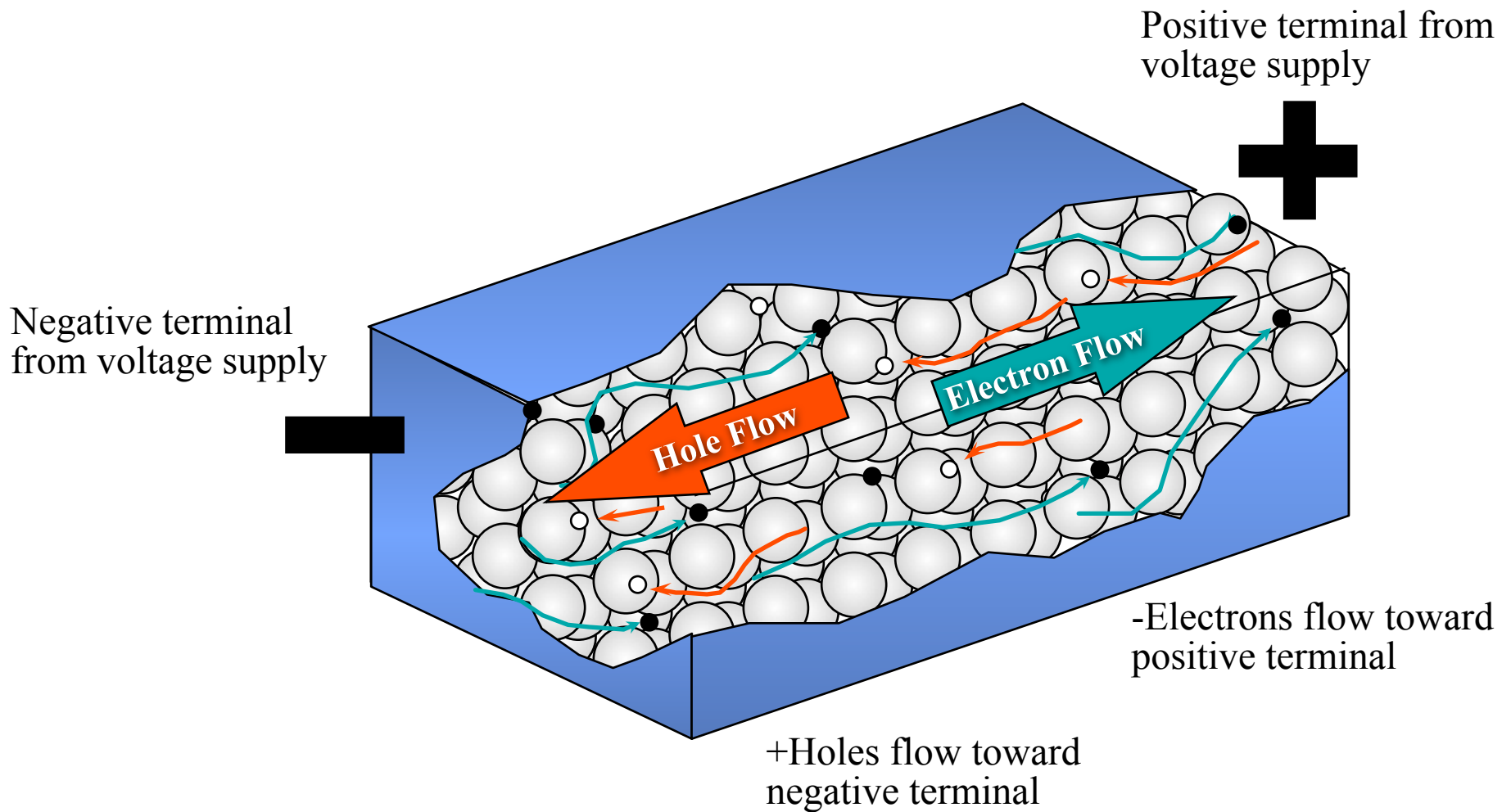

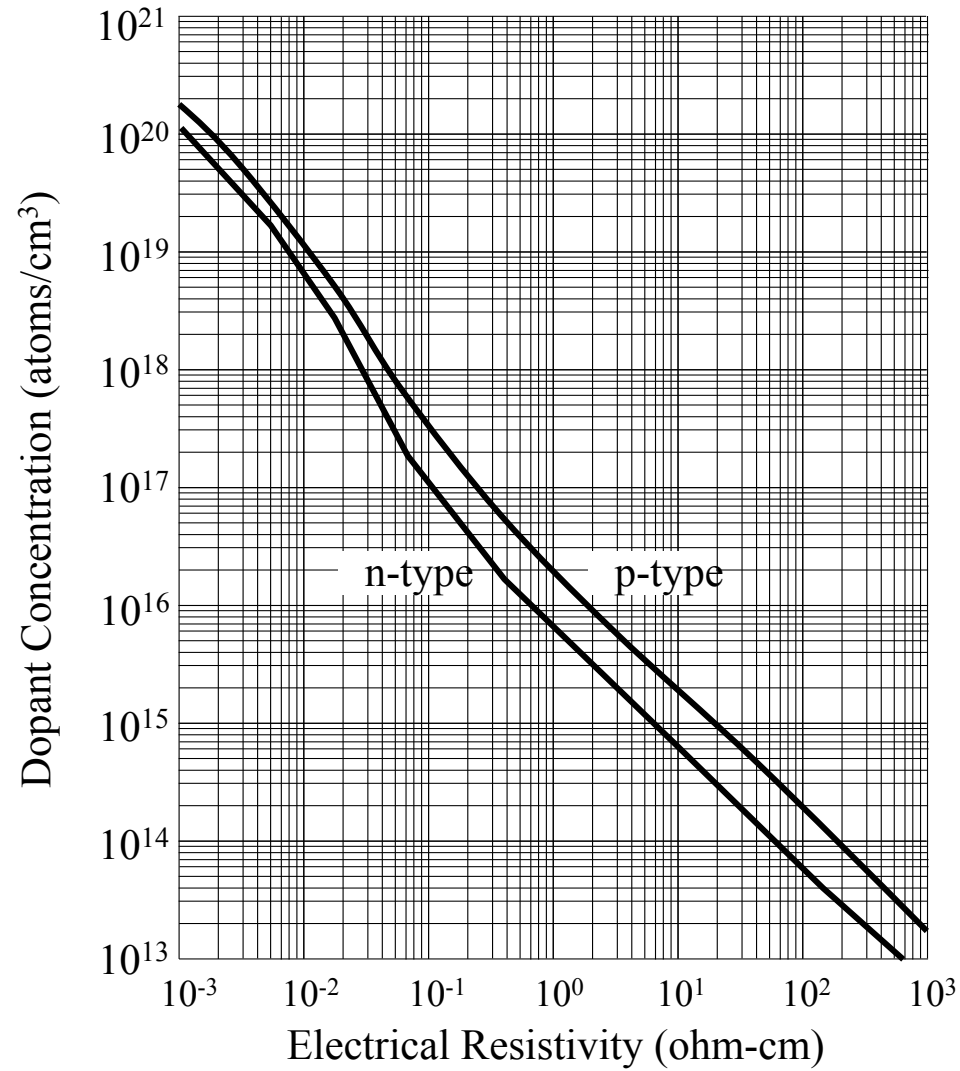
Silicon Resistivity Versus Dopant Concentration



n- and p-Type Silicon

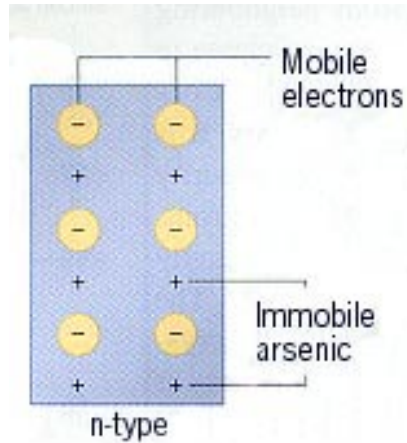

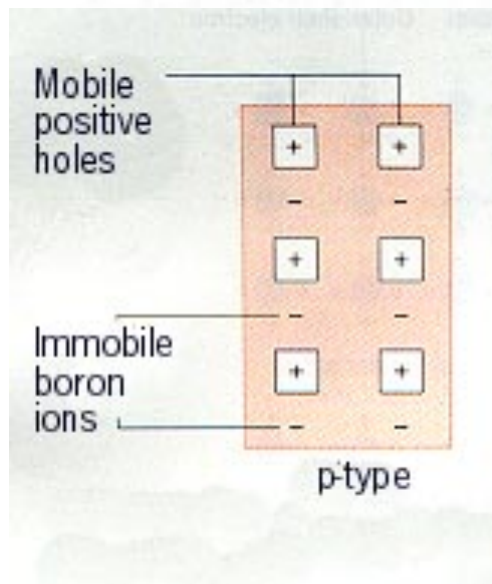The dominant charge carrier in n-type Si is the electron.



The dominant charge carrier in p-type Si is the hole

Important Facts:


Not shown are the silicon atoms, which are present in vastly greater numbers than either arsenic or boron.

Typical doping concentrations are 10^{16} arsenic or boron atoms per cm^3 .


The concentration of silicon atoms is about 10^{22} atoms per cm^3 .

For every "dopant" atom, there are about a million silicon atoms.

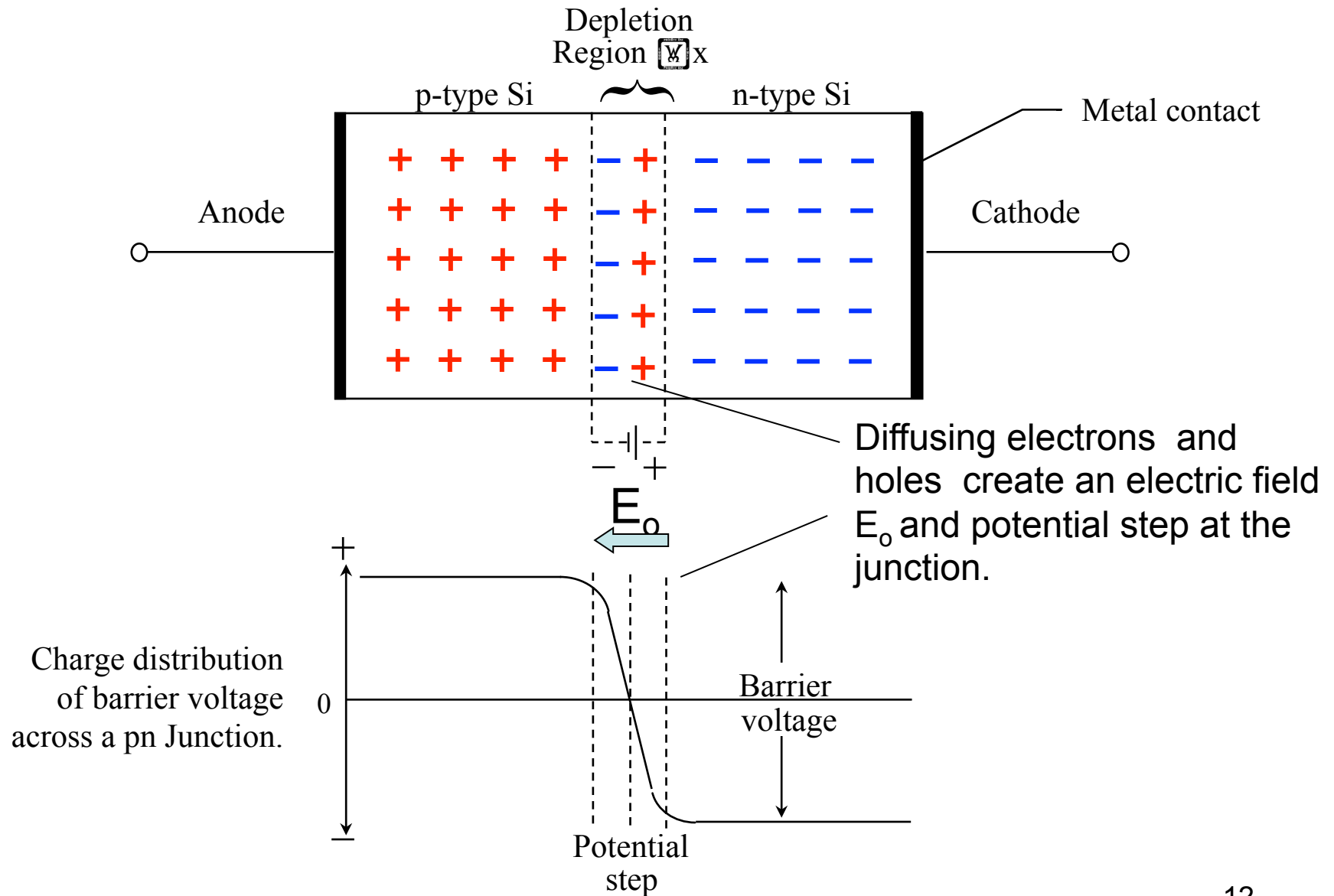Open-Circuit Condition of a p-n Junction Diode




Forward-Biased PN Junction Diode

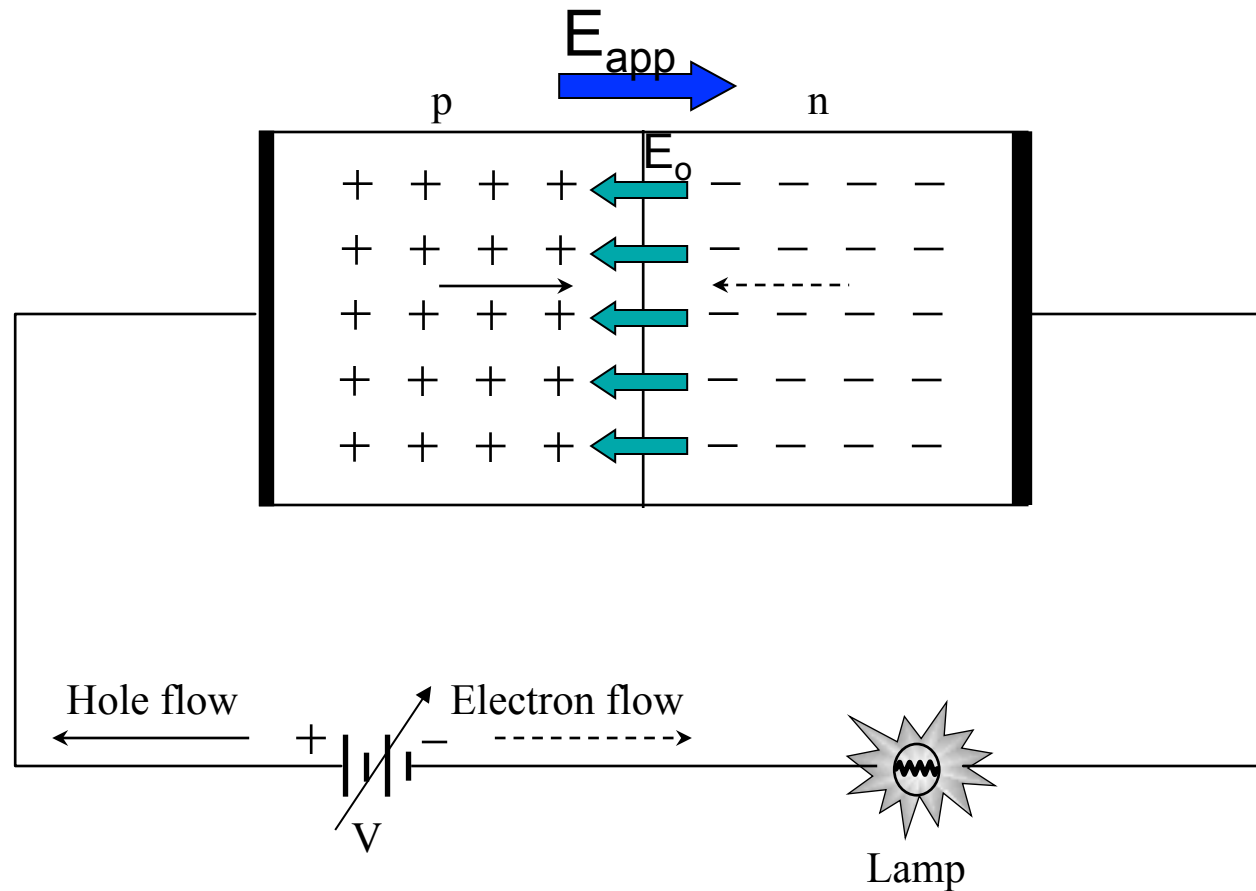


In **forward bias** the applied E-field cancels internal electric field and charges begin flowing across the junction when $E_{app} > E_o$ or $V_{app} > \sim 0.6V$.

Reverse-Biased PN Junction Diode

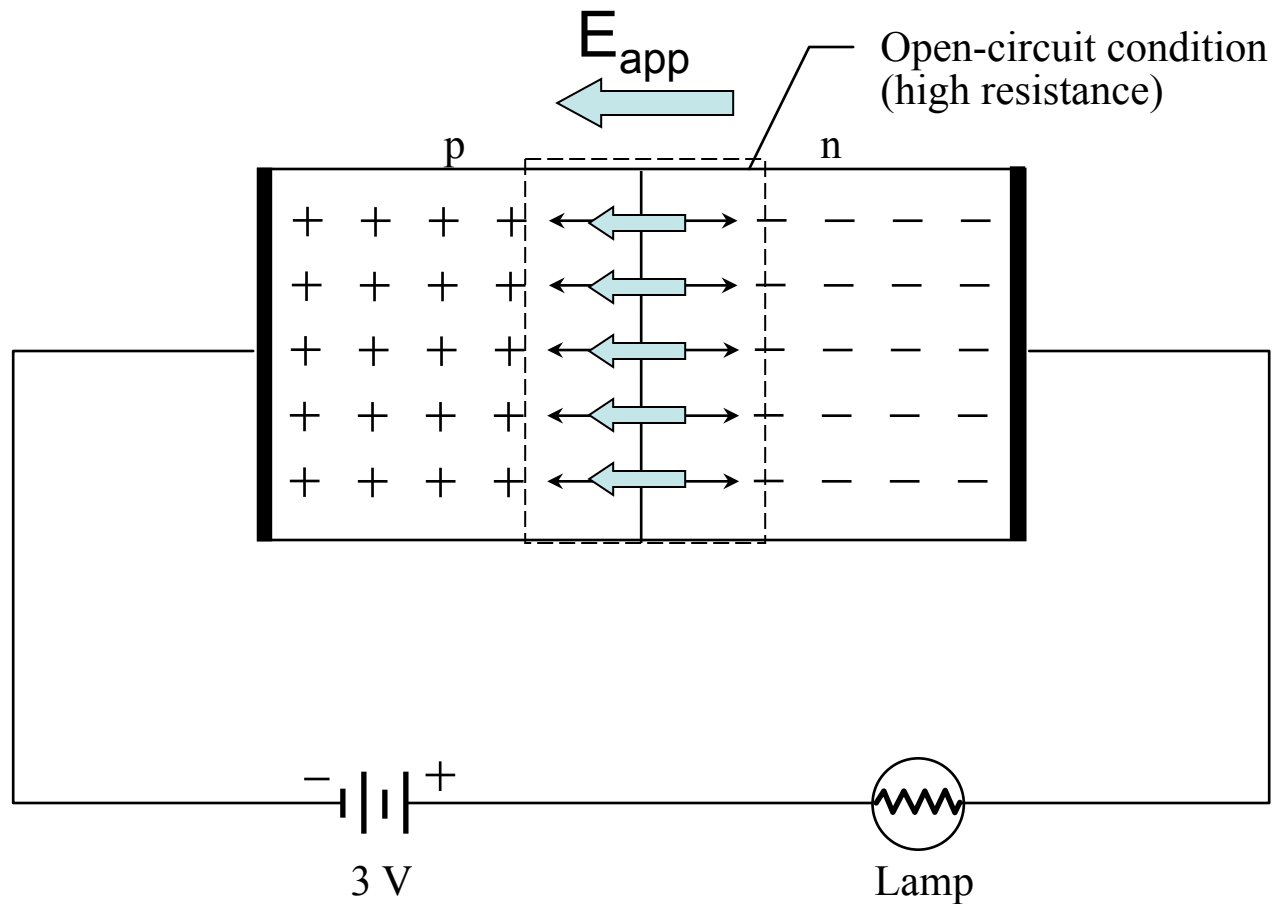

In the **reverse bias** the external E-field increases the size of the depletion zone until all charge carriers are near the contacts - **fully depleted**.

I-V Characteristic Curve

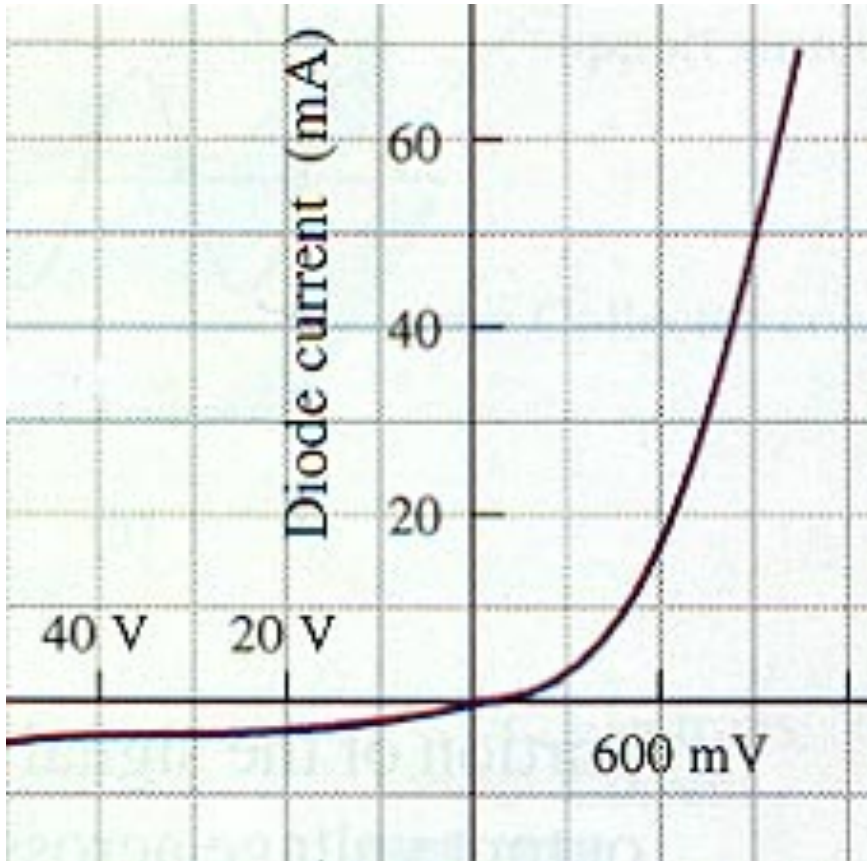

Reverse current exaggerated; typical reverse saturation current: $I_S \sim 10^{-(6-12)} \text{A}$.

This is the "characteristic" curve of a pn junction diode. It shows the slow, then abrupt, rise of current as the voltage is raised.

Under reverse bias, even very large voltages will cause only very small currents, essentially *constant* reverse bias currents.

Shockley Diode Law (Ideal)


$$I = I_S(e^{+eV_D/kT} - 1) \sim I_S e^{+eV_D/kT}$$

I_S = reverse bias saturation current

V_D = diode voltage

$kT = 0.025 \text{eV}$ at 300°K

Turn-On Voltage

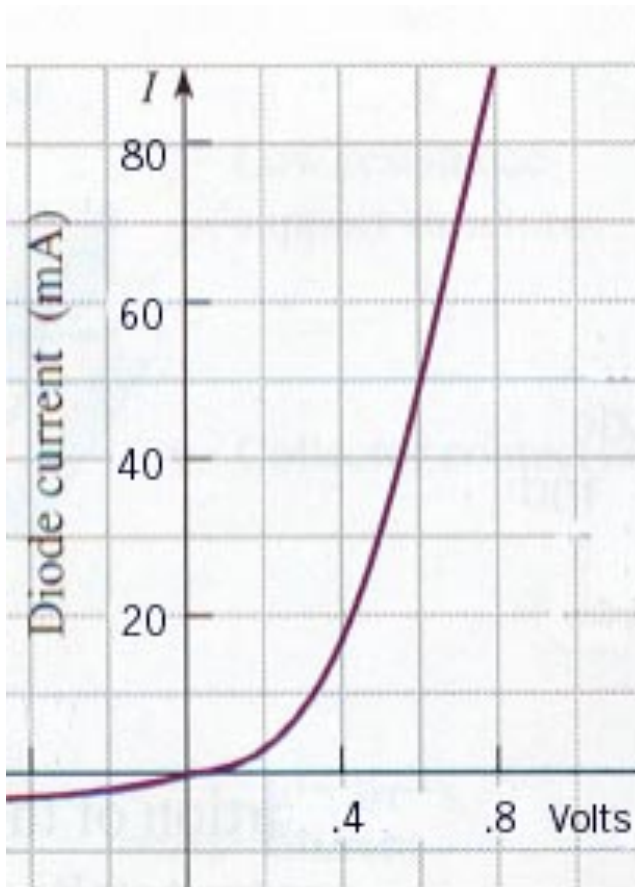


A pn junction diode "turns on" at about 0.6 V, but that varies according to the doping concentration, diode type.

Notice the sharp rise in current near the turn-on voltage. This behavior will be exploited later in the construction of the transistor amplifier.

Use the Shockley Equation to determine the forward diode current $V_D = 1\text{ V}$ $T = 300^\circ\text{ K}$ and $I_s = 10\text{ pA}$.

$$I = 10\text{ pA} \exp(1\text{ eV} / 0.025\text{ eV}) = 2.4\text{ e9 A} !!$$

Solving Diode Equation by Iteration

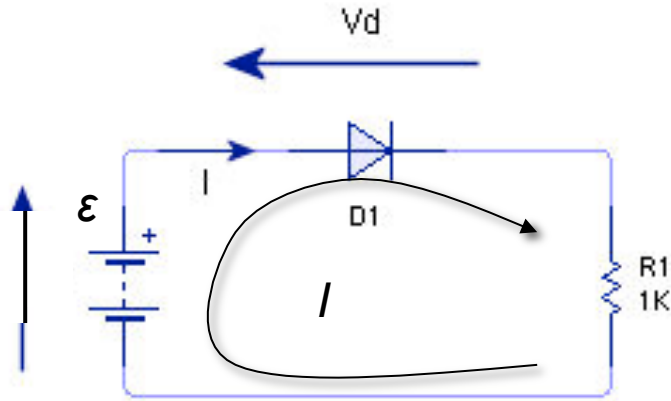


$$\varepsilon - V_d - IR = 0 \quad \text{Kirchhoff's law}$$

$$I = \frac{\varepsilon - V_d}{R} = I_s \left(e^{V_d/nkT} - 1 \right) \quad n \equiv \text{diode realty factor } n \sim 1.5$$

$$\frac{eV_d}{nkT} = \ln \left(\frac{I}{I_s} + 1 \right)$$

$$V_d = \left(\frac{n}{e} \right) kT \ln \left(\frac{\varepsilon - V_d}{I_s R} + 1 \right) \quad \text{Solve by iteration}$$

DIODE EQ. ITERATIVE SOLUTION

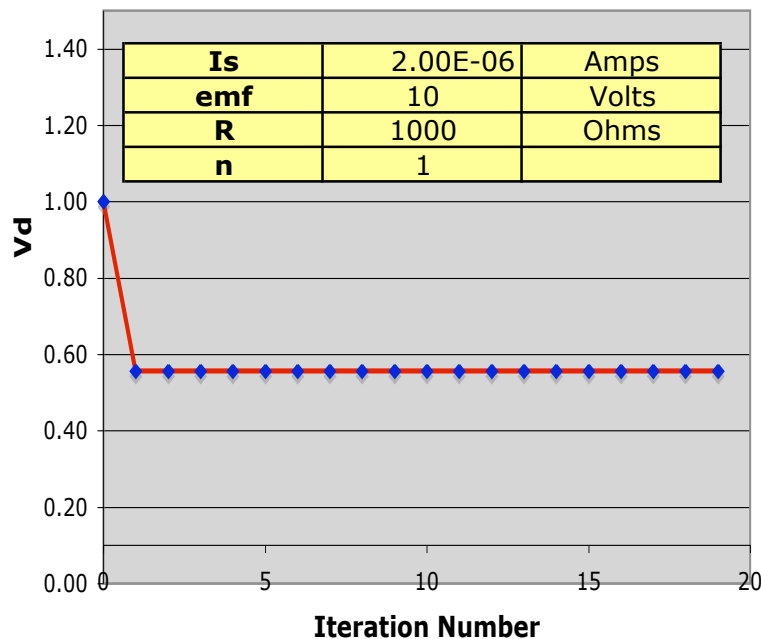

$$V_d^{(1)} = \left(\frac{n}{e} \right) kT \ln \left(\frac{\varepsilon - V_d^{(0)}}{I_s R} + 1 \right)$$

$$V_d^{(2)} = \left(\frac{n}{e} \right) kT \ln \left(\frac{\varepsilon - V_d^{(1)}}{I_s R} + 1 \right)$$

.


Stop when $V_d^{(N+1)} \sim V_d^{(N)}$

http://en.wikipedia.org/wiki/Diode_modelling#Shockley_diode_model

A PN Junction Diode and Its Symbol




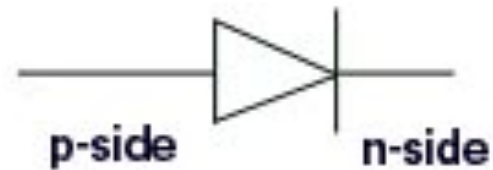Black band corresponds to the "point" in the diode symbol on the right.





It points as "point" is spelled, with "p" first, and "n" later.

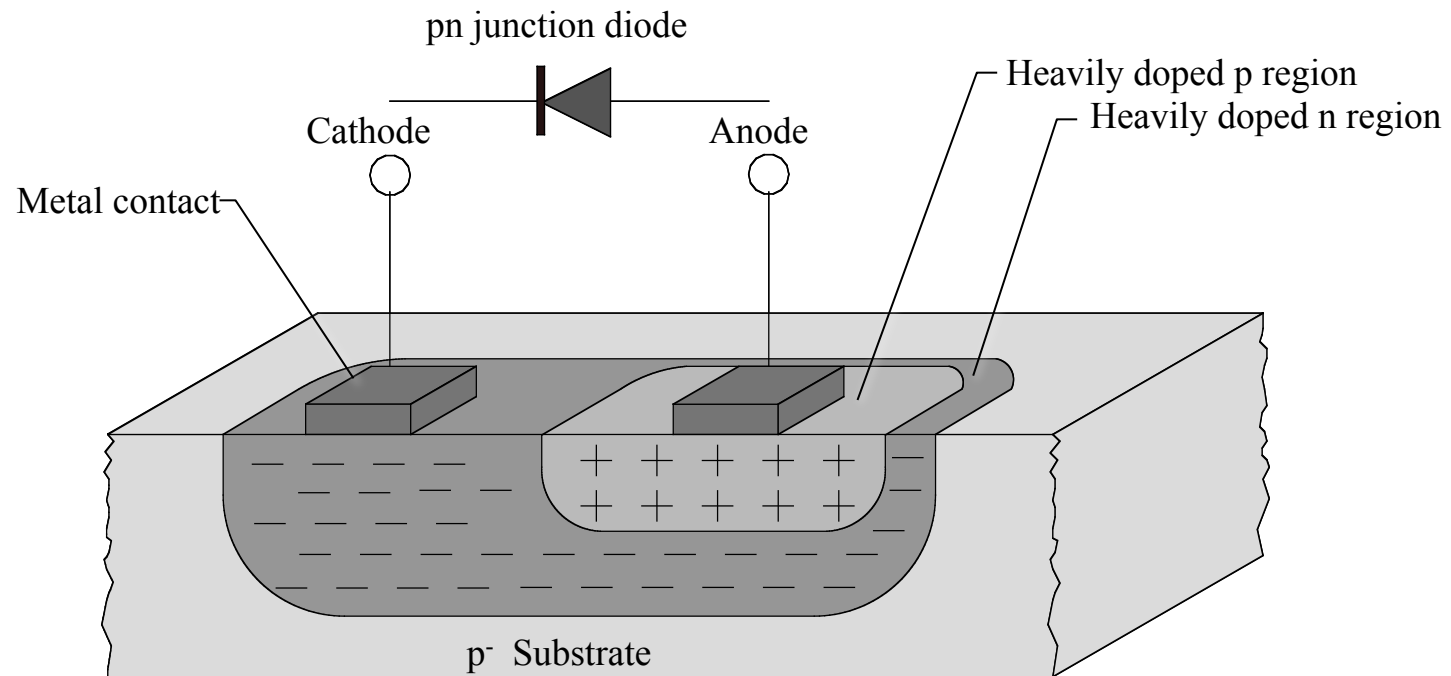Basic Symbol and Structure of the pn Junction Diode



Light Emitting Diodes

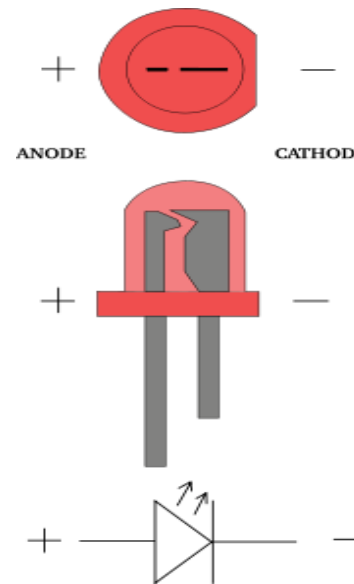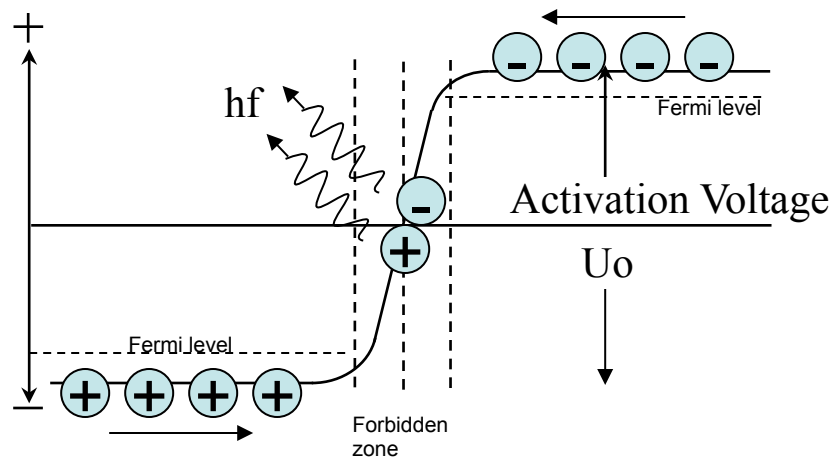As electrons and holes pass thru the forward biased junction, some annihilate and release $hf = eU_0$ of activation energy in to light.




Activation Energy

Color	Potential Difference (Vf)
Infrared	1.6 V
Red	1.8 V to 2.1 V
Orange	2.2 V
Yellow	2.4 V
Green	2.6 V
Blue	3.0 V to 3.5 V
White	3.0 V to 3.5 V
Ultraviolet	3.5 V

$$E = hc/\lambda = 1240 \text{ eV-nm} / \lambda(\text{nm})$$

Red light of 650nm would correspond to $U_0 = 1240/650 \text{ eV} = 1.9 \text{ eV}$


Simple Diode Circuit

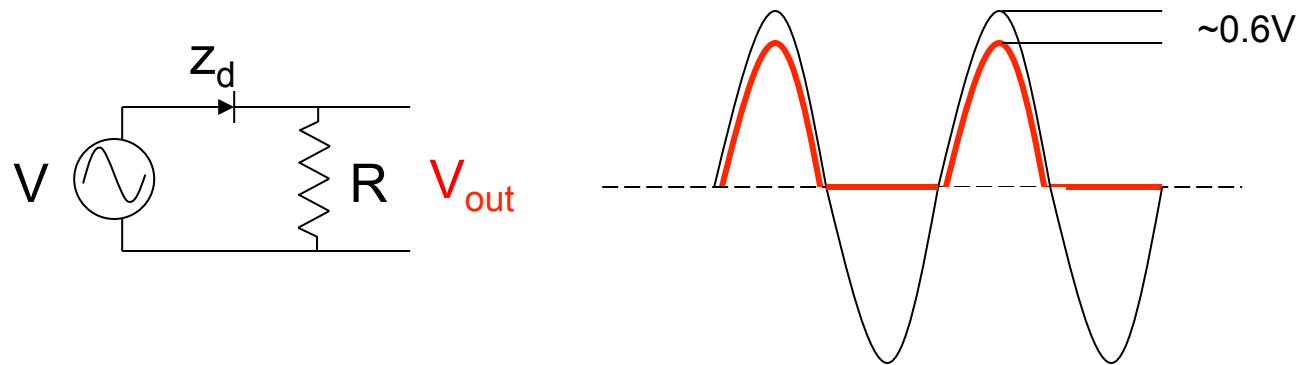


$$V_{diode} \approx 0.6V$$

$$V > V_{diode} \quad z_d = r \quad \text{and} \quad V_{OUT} = \left(\frac{R}{r+R}\right)V = \left(\frac{1}{1+r/R}\right)V \approx (1-r/R)V \approx V - V_{diode}$$
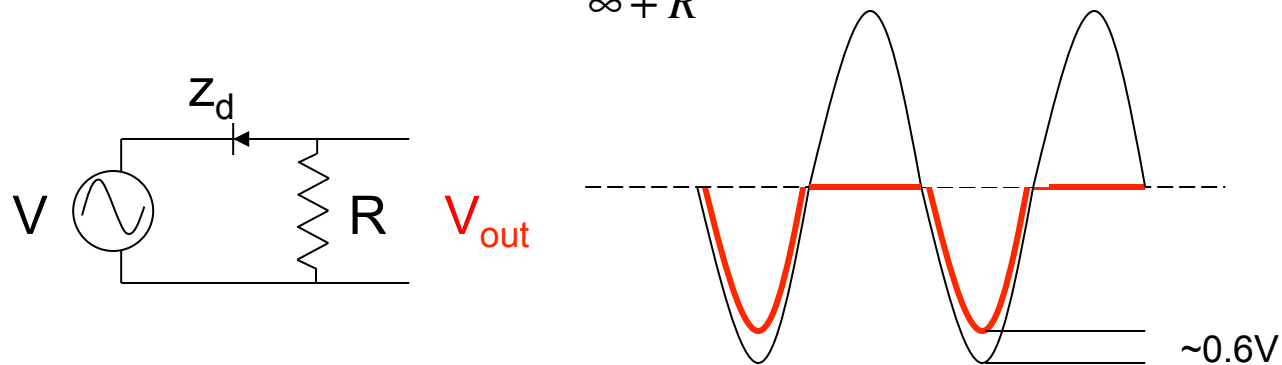
$$V < V_{diode} \quad z_d = \infty \quad \text{and} \quad V_{OUT} = \left(\frac{R}{\infty+R}\right)V = 0$$



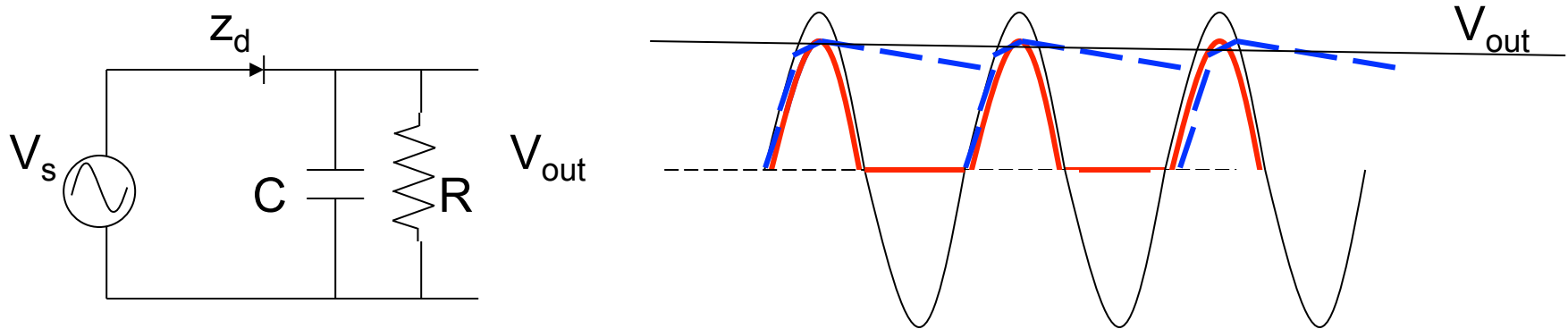Half Wave Rectifier - AC-to-DC Conversion



AC - DC Converter

Capacitor charges to peak voltage $V_{OUT} \sim V_s - 0.6V$

Voltage decays on down-cycle $V_{OUT} = V_s e^{-t/RC}$


$$V_{OUT}(t) = V_s (1 - t / RC + \dots) \quad t / RC \ll 1$$

$$\Delta V = V_{OUT}(t) - V_s = \frac{V_s}{R} \frac{t}{C} = \frac{i}{f C} \quad \text{ripple voltage}$$

$$r = \Delta V / V_{OUT} \quad \text{ripple factor}$$


$V_{OUT} \cong V_s - 0.6V$ We have produced a DC voltage from AC input.

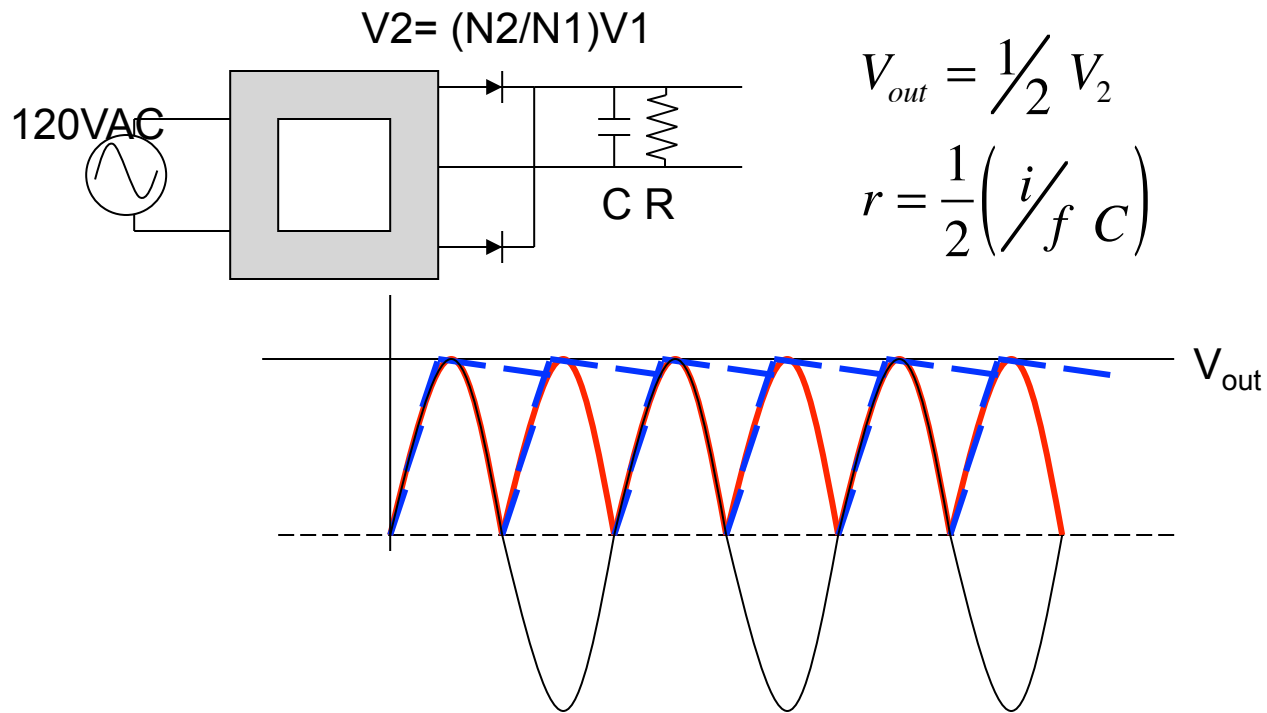Full Wave Rectifier - AC-to-DC Conversion



- In a Full Wave Rectifier two diodes act to rectify both positive and negative cycles.
- A transformer is generally used to isolate the 120VAC (20A) from the secondary.
- Less power wasted and a reduced ripple factor:

Cockroft -Walton Voltage Multipliers

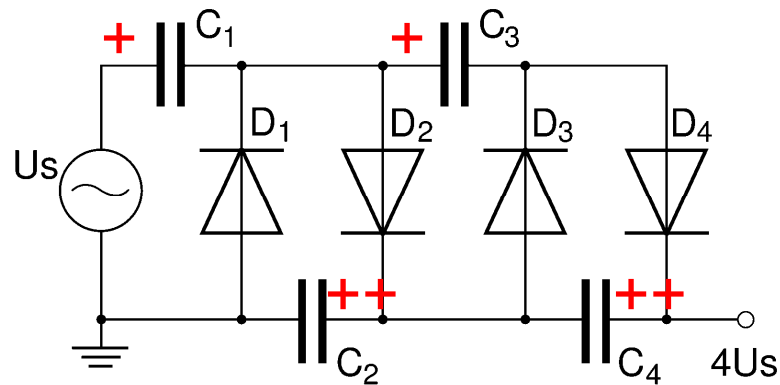


4-stage Multiplier

1. On the positive halfcycle C_1, C_2, C, C_4 charge to $+U_s$ thru D_2 and D_4 . D_1 and D_3 are blocking.
2. On the negative halfcycle C_1, C_3 , charge to $-U_s$, but C_2 and C_4 can not discharge.
3. On the 2nd cycle C_1, C_2, C, C_4 charge again to $+U_s$ thru D_2 and D_4 . and C_2 and C_4 coming each chargeing to $2 U_s$.
4. The total potential difference across the output C_2+C_4 is $V_{out} = +4U_s$.
5. Practically speaking $V_{out} < +4U_{rms}$.
6. You can hear your digital camera charge up the capacitor banks for the flash. The cockroft walton concept can only supply a short burst of charge and must be modified for high DC current use.




<http://www.blazelabs.com/e-exp15.asp>

Voltage Doubler Circuit

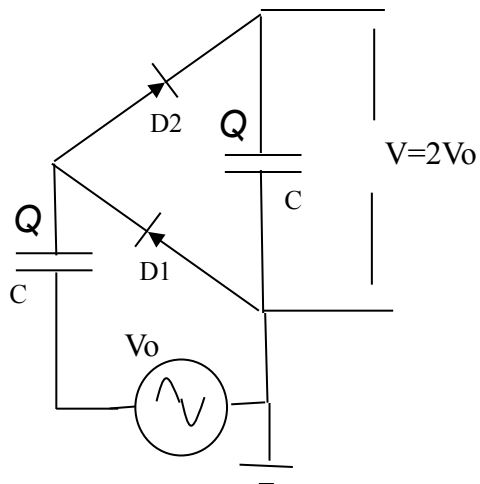


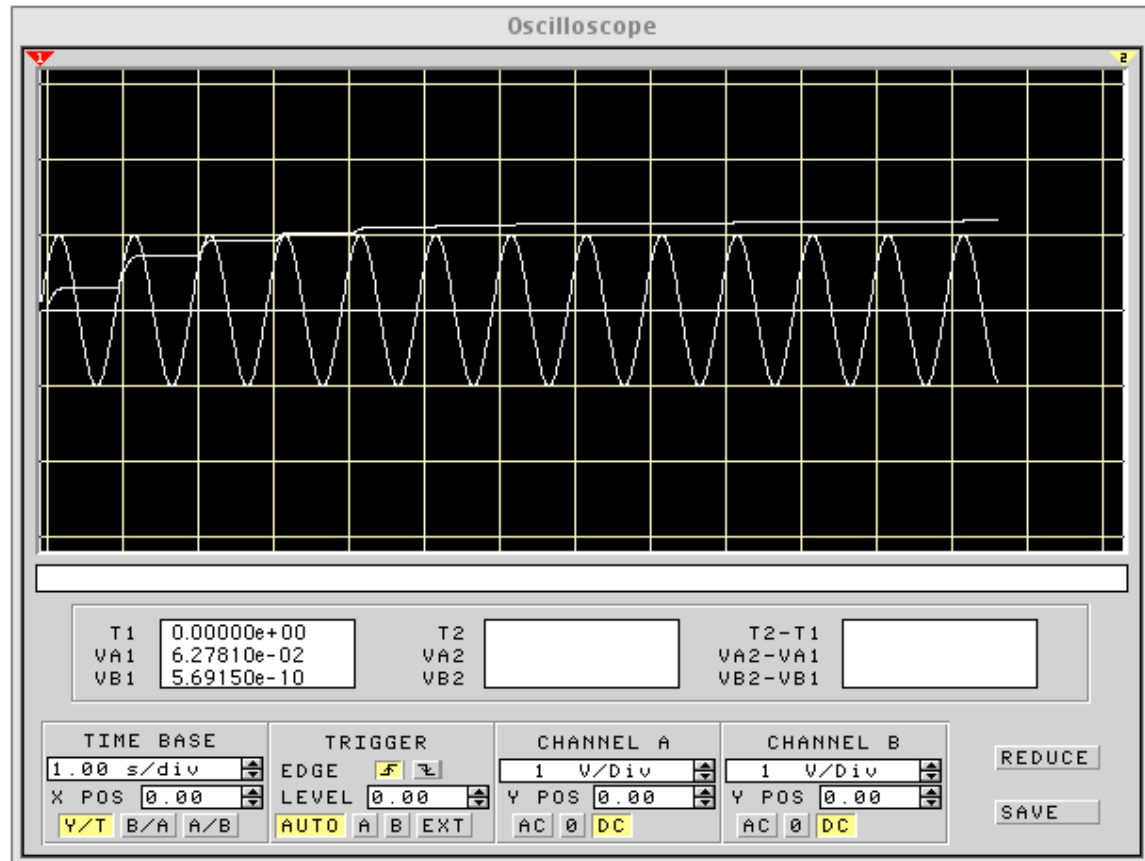
- Capacitors are charged to Q by $V_o \sin(\omega t)$ after a few cycles.
- Charge can not leak off due to diodes. T
- Total Voltage sum is $V=2V_o$ (doubler)!



Zener Diode / Voltage regulator

- A Zener works in reverse bias mode. It is designed to break down at the precise voltage called $V_{Zener} \sim 10-100V$ eg.
- Point *a* in the circuit is fixed to the Zener voltage when $V_{in} > V_z$.
- The Zener diode is used for tight DC voltage regulation.

Zener breakdown
Voltage $\sim -V_Z$

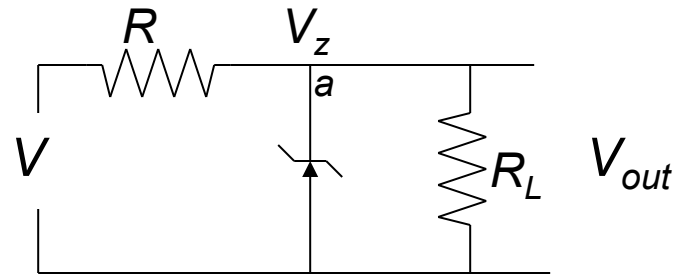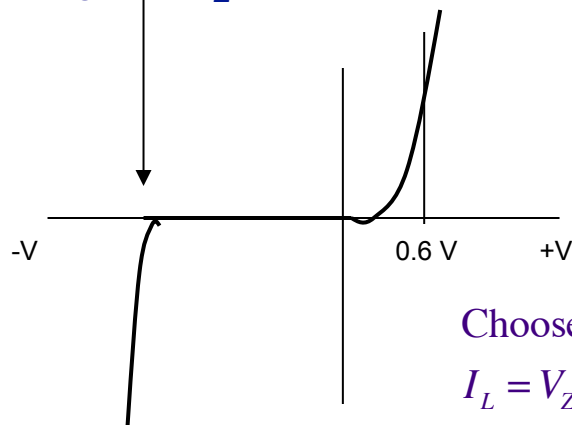

Choose R to limit the current thru the Zener diode ($I_{Zmax} \approx 50ma$)

$$I_L = V_Z / R_L$$

$$I = (V - V_Z) / R$$


$$I_Z = I - I_L < I_{Zmax}$$

$$(V - V_Z) / R - V_Z / R_L < I_{Zmax}$$

$$(V - V_Z) / R < I_{Zmax} + V_Z / R_L$$

$$R > \frac{(V - V_Z)R_L}{I_{Zmax}R_L + V_Z} > \frac{(10V - 5V)1000\Omega}{0.005A \cdot 1000\Omega + 5V} = 91\Omega$$


Input/Output Protection with Diodes

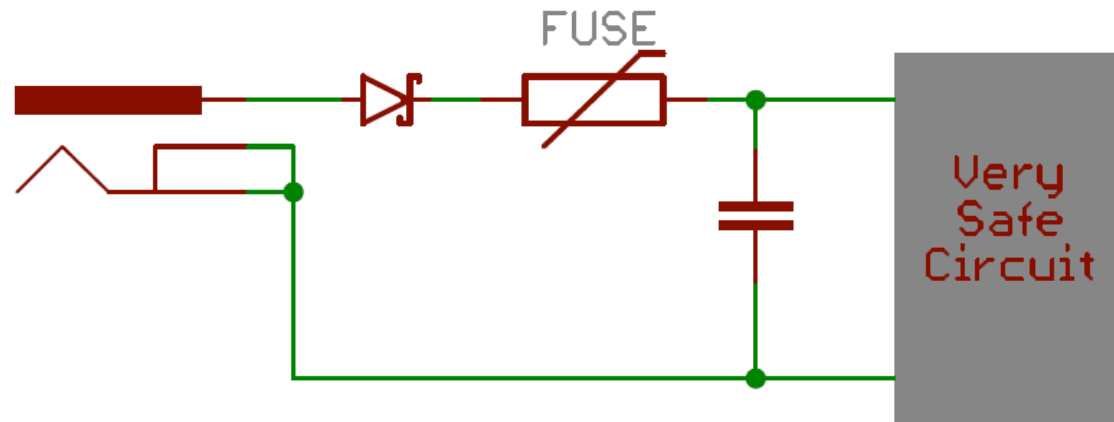

A diode placed in series with the positive side of the power supply is called a reverse protection diode. It ensures that current can only flow in the positive direction, and the power supply only applies a positive voltage to your circuit.

Input/Output Protection with Diodes

- The 470Ω resistor in series with the LED limits the forward bias current flowing through the LED typically $I_{limit} < 20\text{ma}$.
- $9V - 470 I - 0.6V = 0$ so $I = 8.4V/470\Omega = 18\text{ma}$ (safe).
- $I_d = 0$ in most cases where point a is maintained with a positive voltage.
- If someone attached the battery in the reverse directions the LED would blow out w/o the protection diode. The diode allows the **current** to bypass the LED!

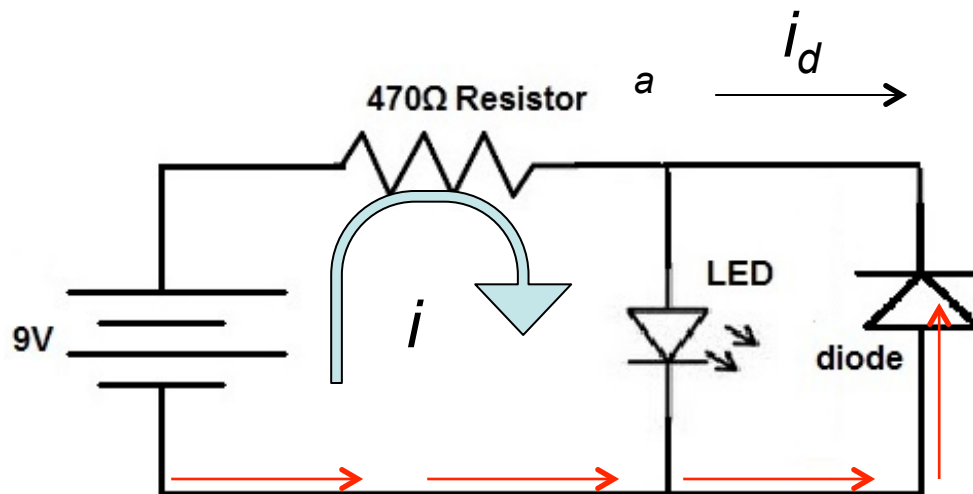

Load Protection with Diodes

- Consider a circuit with a power supply and an inductive load (e.g. motor) on it. From the instant the switch is **closed**, the inductive load will accumulate stored energy. When the switch is **opened** this energy will generate a high reverse voltage and arc across the contacts of the switch. This could damage the switch, load and other circuit components.
- A power diode placed across the inductive load will provide a path for the release of energy stored in the inductor while the inductive load voltage drops to zero.

