
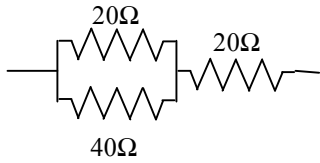


Phys 321 HW-0 Resistance and Circuits

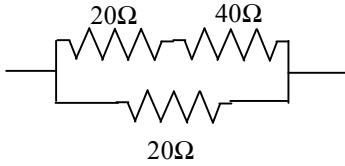1- Determine the net resistance of these networks.



$R_{tot} = \text{_____ } \Omega$




$R_{tot} = \text{_____ } \Omega$

What is the net current through resistor R2?

$i_1 = \text{_____}$


$i_2 = \text{_____}$

$I_{R2} = \text{_____}$

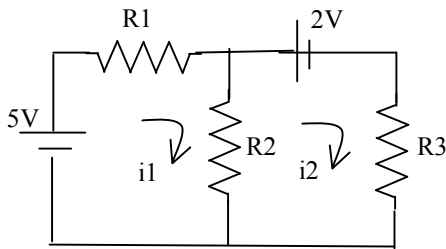


Then $I_{R1} = i_1$ $I_{R2} = i_1 - i_2$ $I_{R3} = i_3$

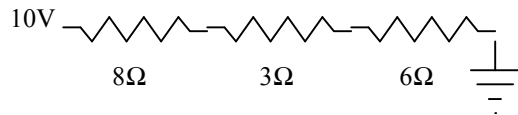3- What is the voltage drop across the 8Ω resistor?



$V_8 = \text{_____ } V$

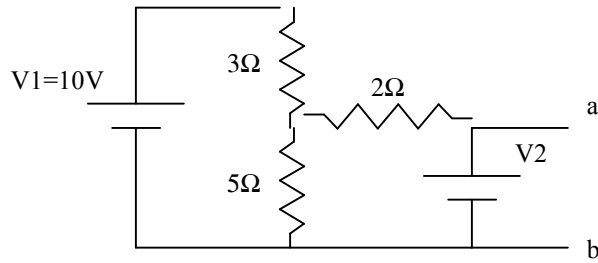- 4- Use Thevenin's Theorem to determine the effective voltage and resistance of the circuit between points a b with V2 removed.



- 5- Use Thevenin's Theorem to determine the effective voltage and resistance of the circuit between points at a b with R3 removed. $R1=100\Omega$, $R2=1000\Omega$, $R3=99\Omega$, $R4=1000\Omega$, $R5=10\Omega$.

