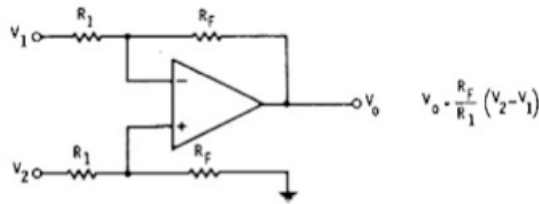


## Homework Chapter 9 (Please attach this sheet to your HW solutions.)

#1- Derive the Vout for the Difference Amplifier from Op Amp first principles.



(F) Differential-input amp.

$$V_1 - iR_1 = V_- \text{ or } i = (V_1 - V_-)/R_1$$

$$V_- = iR_F + V_{out} \text{ or } i = (V_- - V_{out})/R_F$$

$$(V_1 - V_-)/R_1 = (V_- - V_{out})/R_F$$


$$V_- = (V_1 R_F + V_{out} R_1)/(R_1 + R_F)$$

$$V_+ = V_- = V_2 R_F/(R_1 + R_F) = (V_1 R_F + V_{out} R_1)/(R_1 + R_F)$$

$$(V_1 R_F + V_{out} R_1) = [V_2 R_F/(R_1 + R_F)] (R_1 + R_F)$$

$$V_o = \frac{R_F}{R_1} (V_2 - V_1)$$
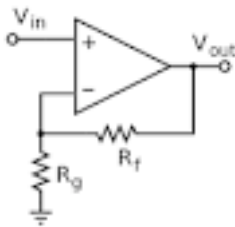
#2 - With  $R_F=100k\Omega$  and  $R_g=10k\Omega$  determine  $V_{out}$  as a function of  $V_{in}$ . Also evaluate the input impedance of the circuit.



Non-Inverting Amp

$$V_{out} = V_{in}(1 + R_F/R_g) = 11 V_{in}$$

$R_{in} \sim \text{HIGH}$

#3- An amplifier has a common mode rejection ratio of  $cmrr=60\text{db}$  and a gain of  $A_v=150$ . If a differential signal of  $2\text{mV}$  is applied to the input along with an unwanted common mode noise of  $10\text{mV}$ , what is the amplitude of the signal and noise at the output?

$$60\text{db} = 10^{-3}$$

$$A_v = 150 \text{ for true signal } \rightarrow$$

$$A_{cmrr} = A_v/80\text{db} = 150 \times 10^{-3} \rightarrow$$


$$V_{out} = 300 \pm 3\text{mV}$$

$$V_{\text{signal}} = 2\text{mV} \times 150 = \mathbf{300\text{mV}}$$

$$V_{\text{noise}} = (10+10)\text{mV} \times 150 \times 10^{-3} = \mathbf{3.0\text{mV}}$$

~
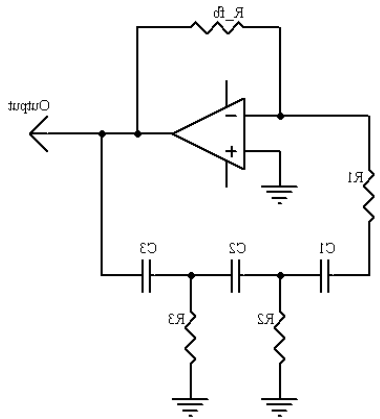
#4- What is the frequency of the phase shift oscillator shown below. Given  $R_1=R_2=R_3=1k\Omega$  and  $C_1=C_2=C_3=10\text{pf}$ . Also give  $R_{fb}$ .



$$f = 1/2\pi RC\sqrt{6} = 6.5\text{MHz}$$

$$R_{fb} \sim 30R = 30\text{ k}\Omega$$

