

Chapter-8 Homework

#1- Design a common-emitter amplifier with output impedance $10\text{K}\Omega$ and having a gain of 100 using a transistor of $\beta=200$ and a 24V power supply. Sketch the amplifier and give R_1 , R_2 , R_C , R_E .

$$V_{CC}=+24\text{V}$$

$$\text{Output impedance} = R_C = 10\text{K}\Omega$$

Choose $V_C = V_{CC}/2$ so the amplifier has $\pm 12\text{V}$ swing

$$I_C = (24 - V_C)/R_C = 12/10\text{K} = 1.2\text{mA}$$

$$\text{For a gain} = -100 \text{ choose } R_C/R_E = 100 \text{ or } R_E = 100\Omega$$

Determine the base voltage for biasing R_1 and R_2 -

$$V_E = I_E R_E \sim I_C R_E = (1.2\text{mA})(100\Omega) = 0.12\text{V}$$

$$V_B = V_E + 0.6\text{V} = 0.72\text{V}$$

Choose $R_2 = 10 R_E$ satisfying $\beta R_E \gg (1/R_1 + 1/R_2)^{-1}$.

This limits the bias current through the base. We want the input signal current to dominate the base bias current!

$$R_2 \sim (1/10)\beta R_E = 2\text{K}\Omega$$

$$I_2 = V_B/R_2 = 0.72\text{V}/2000\Omega = 0.36\text{mA}$$

$$I_B = I_C/\beta = 1.2\text{mA}/200 \sim 0.006\text{mA}$$

$$I_1 = I_B + I_2 = 0.37\text{mA}$$

$$R_1 = (V_{CC} - V_B) / I_1 = (24 - 0.72)/0.37 = 63\text{K}\Omega$$

Also $V_B = 0.6\text{V} + 0.12\text{V} = 0.72\text{V}$
where 0.6V is transistor turn-on and 0.12V is 1/100 of $(V_{CC}/2)$ the null output voltage

$$V_B = [R_2/(R_1 + R_2)] \times 24\text{V} \text{ voltage divider theorem}$$
$$0.72\text{V} = [2000/(R_1 + 2000)] \times 24\text{V}$$
$$R_2 = 65\text{K}\Omega \sim 63\text{K}\Omega$$

#2- Design an emitter-follower with input impedance of $1\text{M}\Omega$ using a $\beta=500$ transistor. If a 300Ω signal generator is driving the circuit, what is the output impedance?

$$V_{CC} = 12\text{V}$$

$$R_E = R_{in} / \beta = 1\text{e}6 / 500 = 2\text{K}\Omega$$

$$R_{out} = R_{source} / \beta = 300/500 = 0.6\Omega$$

#3- An amplifier has an input impedance $Z_{IN} = 10\text{K}\Omega$ and output impedance $Z_{OUT} = 100\Omega$. The input signal is sent through a $C = 470\mu\text{F}$ input capacitor. The stray capacitance in the leads is $C_S = 10\text{pF}$. Determine the high and low cutoff frequency of the open amplifier circuit.

$$f_{LO} = 1/2\pi R_{in} C_{in} = 1/(6.28)(10\text{K})(470\text{e-}6) = 0.034\text{Hz}$$

$$f_{HI} = 1/2\pi R_{out} C_{out} = 1/(6.28)(100)(10\text{pf}) = 160\text{MHz}$$