

## THE TRANSFORMER EXERCISE

Through Lenz's Law we can introduce some of the basic formalism for the transformer. The magnetic flux  $\Phi = \Phi_M$  and emf  $\varepsilon$  through a circuit or coil ( $N$  turns) is given by

$$\varepsilon = -\frac{d\Phi}{dt} \quad \text{and} \quad \Phi_M = N B A$$

The inductance  $L$  of the circuit is defined by  $L = \frac{d\Phi}{dI}$ . The emf can now be written as


$$\varepsilon = -\frac{d\Phi}{dI} \frac{dI}{dt} = -L \frac{dI}{dt}$$

Consider a simple coil of  $N_1$  turns on the primary and  $N_2$  turns on the secondary. Assume the coils each have length  $\ell$  and cross sectional area  $A$ . The steel laminations of the transformer have permeability  $\kappa_M$  ( $\kappa \sim 5000 \mu_0$  for Iron). We can write

$$B = \kappa_M \frac{N I}{\ell} \quad \text{and} \quad \Phi = \kappa_M \frac{N^2 I}{\ell} \cdot A$$

$$L_{1,2} = \frac{d\Phi}{dI} = \kappa_M \frac{N_{1,2}^2}{\ell} \cdot A$$

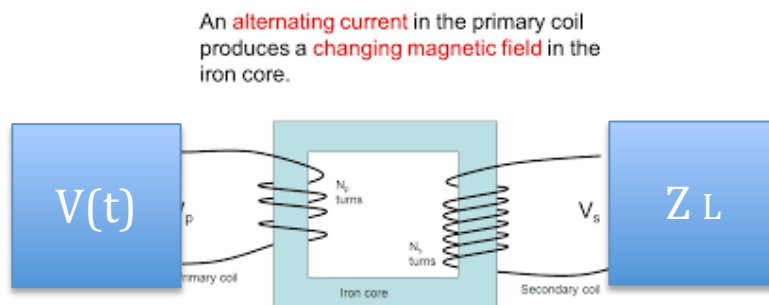Since the coils are strongly coupled together there is a strong mutual inductance between the primary and secondary coils  $M_{12} = M_{21} = M \approx k \sqrt{L_1 \cdot L_2}$  where coupling strength  $k$  varies from 0-1;  $k \sim 0.95$  for a well designed transformer.



Assume  $V_p(t) = V_1 e^{i\omega t}$  and a load  $Z_L$  is attached to the secondary. Let  $I_1$  and  $I_2$  be clockwise currents in the primary and secondary coils. We can write Kirchoff's:

$$\varepsilon_1 = \overbrace{(i\omega L_1)}^{Z_{L1}} I_1 + \overbrace{(i\omega M)}^{Z_M} I_2$$

$$0 = \overbrace{(i\omega L_2)}^{Z_{L2}} I_2 + \overbrace{(i\omega M)}^{Z_M} I_1 + Z_L I_2$$

$$\begin{aligned} \varepsilon_1 &= (i\omega L_1) I_1 + (i\omega M) I_2 \rightarrow & \varepsilon_1 &= (i\omega L_1) I_1 + (i\omega M) I_2 \\ 0 &= (i\omega L_2) I_2 + (i\omega M) I_1 + Z_L I_2 \rightarrow & 0 &= (i\omega L_2 + Z_L) I_2 + i\omega M I_1 \end{aligned}$$

$$I_1 = \frac{-(i\omega L_2 + Z_L)}{i\omega M} I_2$$

$$\varepsilon_1 = \left( (i\omega L_1) \frac{-(i\omega L_2 + Z_L)}{i\omega M} + (i\omega M) \right) I_2$$

$$\varepsilon_1 = \left( \frac{(i\omega L_1)(i\omega L_2 + Z_L) - \omega^2 M^2}{-i\omega M} \right) I_2$$

$$I_2 = \frac{-i\omega M}{(i\omega L_1)(i\omega L_2 + Z_L) - \omega^2 M^2} \varepsilon_1 \quad \text{and} \quad |I_2| = \sqrt{I_2 I_2^*}$$

$$I_1 = \frac{(i\omega L_2 + Z_L)}{((i\omega L_1)(i\omega L_2 + Z_L) - \omega^2 M^2)} \varepsilon_1 \quad \text{and} \quad |I_1| = \sqrt{I_1 I_1^*}$$

Exercises:

- 1) Find expressions for  $|I_1|$  and  $|I_2|$ .
- 2) If  $L_1 = L_2 = 1 \text{ mH}$  and  $Z_L = 50 \Omega$ , what angular frequency  $\omega$  would  $|I_2|$  be maximum. Let  $k=1$ ?
- 3) Show that  $|I_2|/|I_1| = N_1 / N_2$  with  $Z_L = 0$  and  $L_1 = L_2$ .