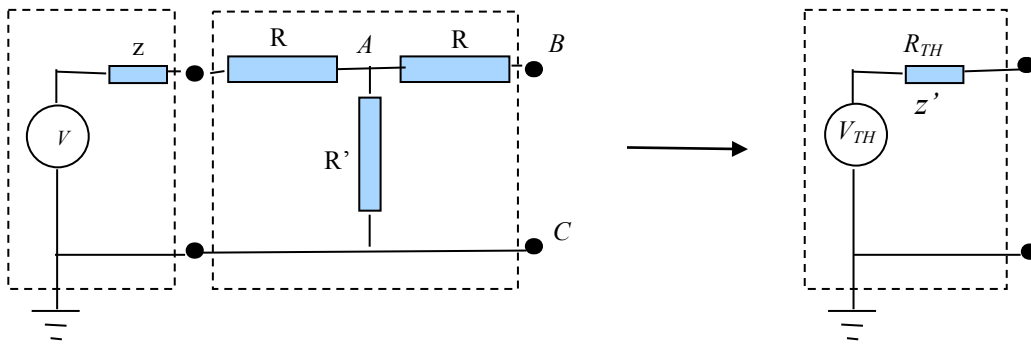


Tee Attenuators

When using a simple voltage divider we can attenuate the input signal strength but will have difficulty in keeping the input(source impedance) and output impedance the same ($z=z'$). A tee or pi attenuator will allow us to do this.

I. Tee Attenuator



Use Thevenin's Approach

$$V_{TH} = V_{BC} = V_A + \overbrace{\widehat{V_{AB}}}^{=0 \text{ no current}} = V_{AC} = \overbrace{\frac{R'}{z+R+R'}}^{\text{Voltage Divider}} V$$

$$R_{TH} = \left(\frac{1}{z+R} + \frac{1}{R'} \right)^{-1} + R = \frac{(z+R)R'}{(z+R)+R'} + R$$

$$= (z+R) \left(\frac{V_{BC}}{V} \right) + R = z'$$

Given α and z' we have two equations and two unknowns R, R' to solve:

1) Attenuation of the Tee Attenuator $\alpha = \frac{V_{BC}}{V} = \frac{R'}{z+R+R'}$

2) Output Impedance of the Tee Attenuator $z' = R_{TH} = (z+R) \left(\frac{V_{BC}}{V} \right) + R$

Example:

Let $\alpha = V_{BC}/V = 0.1$ attenuation level,

$z' = z = 50\Omega$ output impedance matching input impedance

$$R = \frac{1-\alpha}{1+\alpha} z = \frac{0.9}{1.1} 50\Omega = 41\Omega$$

$$R' = \frac{\alpha(z+R)}{1-\alpha} = 10.1\Omega$$