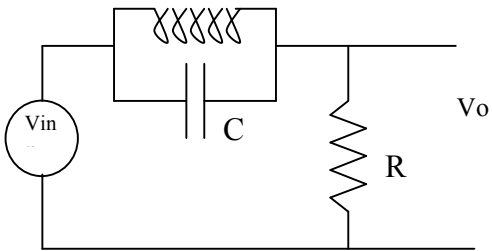


Chapter3 - AC Filter Homework

Answer these on a separate sheet(s). Number your problems. Show your work. Attach the problem sheet to your answers.

1) Derive and sketch the frequency dependence of the gain for a high pass filter in terms of R and C .

2) Find the gain as a function of frequency for the following circuit. Is there a resonance in the circuit? If so, at what frequency?



3) - 6db in power is what factor of gain? Show your derivation.

- 6db in voltage is what factor of gain? Show your derivation.

4) What is the Q value of the circuit in #2 if $R = 10\text{k}\Omega$, $C = 1\mu\text{F}$, $L = 1\text{mH}$.