Chapter - 1 Direct Current Circuits

- RESISTANCE
- KIRKOFFS LAW and LOOP-MESH METHOD
- VOLTAGE DIVIDER
- INTERNAL RESISTANCE and OUTPUT IMPEDANCE
- HOW TO MEASURE OUTPUT IMPEDANCE OF A
 DEVICE
- •THEVENIN's THEOREM

Resistivity

• ρ property of a material characterizing electron flow

• Σ=1/ρ conductivity

•Metal – Energy gap, Eg, between Valence and Conduction bands overlap.

•Semiconductor - small Energy gap between valence and conduction bands, of order 1 eV.

•Insulator – large Energy gap between valence and conduction bands, of order 10 eV.



Resistance

Materials have different resistivities ρ
R = ρ(L/a) = resistance (Ohms) L=length a = cross sectional area





Ohm's Law

• The Voltage drop across a circuit element R is proportional to the current flowing through it.

i =V/R or V = *i* R



• The constant of proportionality is the resistance R or impedance.

Series and Parallel Connections

• Resistances in series directly add.



• Resistances in parallel follow the inverse rule of addition.



Kirchoffs Circuit Laws (by Mesh Currents)

(1) Choose mesh currents to run CW in each circuit loop (convention).

(2) Add the battery emfs when in direction of mesh current, subtract when opposing mesh current.

(3) Write Kirkoff's law for each mesh

(4) Subtract the voltage drops (-iR) across resistor in the mesh, add (+iR) the adjacent mesh.

(5) Physical currents through components can be determined from i1 and i2.



Example



Find *I1*, *I2*, *I* ?

5V - 10 i1 + 10 i2 = 0 0 - 2 i2 - 10 i2 + 10 i1 = 01) 5V = 10 i1 - 10 i22) 0 = -10 i1 + 12 i2 5V = 0 + 2 i2 adding 1) + 2) --> i2 = 5/2 A i1 = (12/10)i2 = 3A i2 = 5/2 AI = i1 = 3A

Example from web!



2LOOP Graphical Solution

Rewrite equaions in terms of straight lines y = mx + b



Voltage Divider



A simple resistive voltage divider allows us to adjust the input voltage to a lower level.



$$Vout = \left(\frac{R2}{R1 + R2}\right) Vin$$

This high voltage probe uses a voltage divider to allow us to measure a large voltage by dropping it to a lower range.

Voltage Divider



Voltage drop on ith resistor is proportional to ratio of Ri to Rtot! $Vi = \{ Ri/Rtot \} V$

 $V1 = R1/Rtot \times V$

 $V2 = R2/Rtot \times V$

Example



•What is the voltage drop across the 5 Ω resistor? Ans: V_{5 Ω} = (5/10) 5V = 2.5V

Current Division

Current will take the path of least resistance, dividing Itself by inverse proportion with i = i1 + i2



$$i1 = \frac{V}{r1} = \frac{i r}{r1} = \frac{r_{tot}}{r1}i$$
$$i2 = \frac{V}{r2} = \frac{i r}{r2} = \frac{r_{tot}}{r2}i$$

Power Dissipated by a Circuit Element



$$P = I V$$

$$P = d/dt U \quad U = qV$$

$$P = d/dt qV$$

$$P = dq/dt V = I V$$

•The power dissipated by a circuit element is given by P=IV,

I = the current passing through the element.

$$V = voltage drop across the element.$$

•Light bulbs (nonOhmic) Resistors(Ohmic)

How long does a 9volt last under 1ma load? Let U = 20kJ V = 9V I = 1mA P = dU / dt $dt = \frac{1}{IV} dU \rightarrow t = \frac{1}{9mW} 20kJ = 2.2e6s = 620h$ 9V 20kJ

Internal Resistance and Output Impedance

- Every Source of Emf has some small internal resistance.
- A signal generator has an internal resistance related to its output Impedance r or z. (z~50 Ohm).
- A voltage divider circuit can be used to measure r and z.
 Adjust R until V_{out}=1/2 V ! Then R = internal resistance !



Input Impedance of Voltmeter and Ammeter

• All input devices has some small internal resistance to the current flowing into it. (Impedance to ground or negative terminal)

- A voltmeter has a **high input impedance** to limit the current flowing in to the measuring device.
- An ammeter wants to divert all the current into it and therefore has a very **low input impedance**.



Input and Output Impedance

• Consider an I/O circuit to be an element which transforms an input voltage waveform to and output voltage waveform.



- The input voltage source $V_{\rm IN}$ sees an effective input impedance $Z_{\rm IN}$ wrt to the input current $I_{\rm IN}=V_{\rm IN}/Zi_{\rm IN}$.

- The output current ${\bf I}_{OUT}$ is driven through an effective series resistance Zout with $V_{OUT}{=}{\bf I}_{OUT}Z_{OUT}$
- All I/O devices can be characterized by an input and output impedance.

Thevenin's Theorem(1)

Consider a complex circuit of which we are dealing with a small part.

1) to calculate the current through (or voltage across) a component in any circuit.

2) or develop a constant voltage equivalent circuit which may be used to simplify the analysis of a complex circuit



Thevenin's Theorem(2)

Any network as observed from two terminals is equivalent to a source of emf and impedance in series, connected to the two terminals.



(1) The element to be studied is removed from the circuit.

(2) V_{TH} is computed or measured from knowledge of the circuit

(3) All voltage sources are shorted and all current sources are opened=circuited.

(4) The equivalent resistance R_{TH} of the circuit is calculated or measured.

(5) The series connection of R_{TH} and V_{TH} are made and the element to be studied is reinserted into the circuit

Thevenin's Theorem(2)

Voltage Divider with Load



What is the current through the load? $V = 50V_{\star}$ R1= 100Ohm, R2=100Ohm RL=50Ohm.

IL = _____0.25A

Vth = 50V (100Ohm/200Ohm) = 25V Rth = 50 Ohm Rtot = Rth + RL = 50Ohm + 50Ohm= 100Ohm

Thevenin Circuit

- (1) Remove load R_L (grey component)
- (2) $V_{TH} = Vab = V R2/(R1+R2)$.
- (3) With battery shorted find Rab.
 - RTH = Rab = R1 R2/(R1+R2) parallel
- (4) Replace Load in to series connection of V_{TH} and R_{TH}.



Thevenin Equivalent Circuit

http://esdstudent.gcal.ac.uk/Thevenin3.htm

2 Port Network (extra)

A two port network is a linear mathematical model that can be used to analyse a circuit and other systems, if the input and output voltages and currents can be isolated. This linear model can be generalized to other flows (I) and potentials (V).



$$V1 = z_{11} I1 + z_{12} I2$$
$$V2 = z_{21} I1 + z_{22} I2$$

z's are the open circuit impedance parameters and can be evaluated zero current or no load conditions.

$$z_{11} = \frac{V1}{I1}_{I2=0}$$
 $z_{12} = \frac{V1}{I2}_{I1=0}$ $z_{21} = \frac{V2}{I1}_{I2=0}$ $z_{22} = \frac{V2}{I2}_{I1=0}$

2 Port Network (extra)

Consider the simple circuit. Given V1,V2, r1,r2,r3, find the z paramaters for the network?



2 Port Network (example)



1) With side-2 open $z_{11} = V1/I1 = 1 + 1 = 2\Omega$ $z_{11} = 2\Omega$ 2) $z_{21} = V2/I1$ where $V2 = I_{1\Omega}1\Omega = I1$ $z_{21} = 1\Omega$ 3) With side-1 open $z_{22} = 1 + 1 = 2\Omega$ $z_{22} = 2\Omega$ 4) $z_{12} = V1/I2$ where $V1 = I_{1\Omega}1\Omega = I2$ $z_{12} = 1\Omega$

For simple RLC neworks $z_{12} = z_{21}$. These are call **reciprocal networks**. Excitation of the input and output produce the veverable response in a reciprocal network.

2 Port Network (example)



1) With side-2 open circuited $z_{11} = V_1/I_1 = 50 \parallel (125+75) = 40 \Omega$ $z_{11} = 40 \Omega$ 2) $z21 = V_2/I_1$ where $V_2 = 75 I_{75}$ $I_{75} = (\frac{50}{50+125+75})I_1 = 0.2 I_1$ by current division $z_{21} = 75 \times 0.2 I_1/I_1 = 15 \Omega$ 3) With side-1 open circuited $z_{22} = V_1/I_1 = 75 \parallel (125+50) = 52.2 \Omega$ 4) $z12 = V_1/I_2$ where $V_1 = 50 I_{50}$ $I_{50} = (\frac{75}{50+125+75})I_2 = 0.3 I_2$ by current division $z_{21} = 50 \times 0.3 I_1/I_1 = 15 \Omega$