

2-7 QUESTIONS AND PROBLEMS

1. Calculate the effective capacitance of the circuit shown in Figure A.

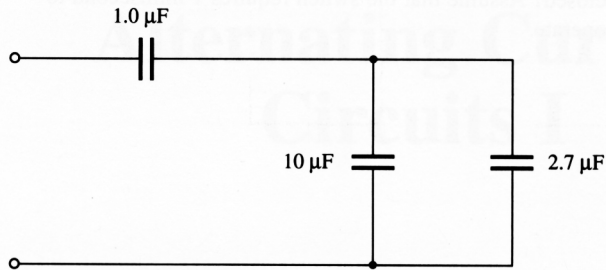


FIGURE A Circuit for problem 1.

2. Calculate the effective capacitance of the circuit shown in Figure B.

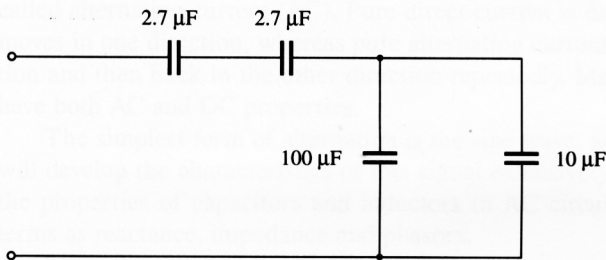


FIGURE B Circuit for problem 2.

3. Sketch v_{out} vs. time for the circuit shown in Figure C after the switch is closed.

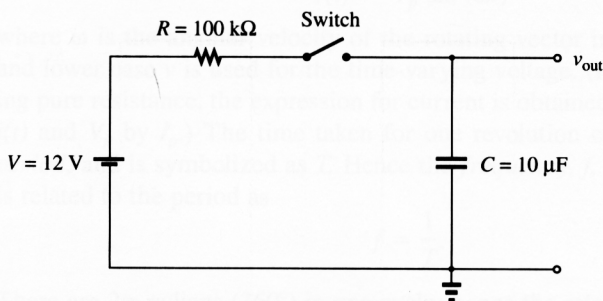


FIGURE C Circuit for problems 3, 4 and 5.

4. Given that the tolerance for the resistor is $\pm 5\%$ and that for the capacitor is -20% to $+80\%$, what would be the minimum and maximum values of v_{out} you would expect from the circuit of Figure C after a time of 1.0 second?

5. An RC circuit is needed with a time constant of 1.000 second. Explain why the circuit shown in Figure C is a poor circuit if the capacitor is electrolytic.

6. A designer wishes to replace the circuit shown in Figure D with an RC circuit that has the same voltage vs. time characteristics. Design an acceptable RC circuit.

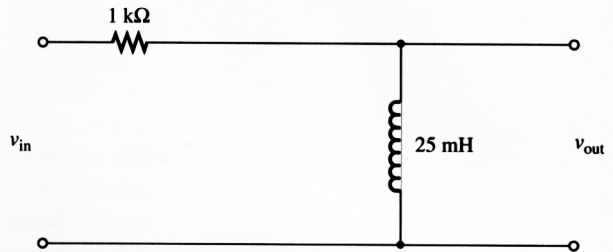


FIGURE D Circuit for problem 6.

7. In the circuit shown in Figure E, describe the current that flows from the battery to point A after the switch is closed. In what direction does it flow and what is its value?

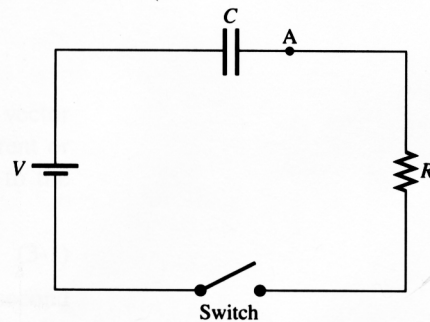


FIGURE E Circuit for problem 7.

8. A timing circuit may use the RC charging time to control a subsequent stage, as in Figure F. With $R = 1 \text{ M}\Omega$, what value of C is needed so that v_c equals 70 V at 10.0 seconds after the switch closes?

9. If the subsequent stage referred to in problem 8 has an effective resistance to ground of $10 \text{ k}\Omega$, how long after the