

PHYS 212, Honors Section – Review Material

Chapter 28: Direct-Current Circuits

- **Emf:** For a battery or other power source, the amount of amount of work done per unit charge to force a current through the circuit,

$$\mathcal{E} = dW/dq .$$

- **Internal resistance:** All batteries have a small internal resistance r , which can be treated as in series with the battery itself; This implies that the actual terminal voltage V is related to the battery emf \mathcal{E} by

$$V = \mathcal{E} - Ir .$$

- **Potential differences:** Finding the potential difference V across an emf device or a resistor with a current I flowing through it, and across a capacitor with a charge Q on it, including the sign of V .
- **Resistors in series:** The resistance equivalent to R_1, R_2, \dots in series is

$$R_{\text{eq}} = R_1 + R_2 + \dots$$

- **Resistors in parallel:** The resistance equivalent to R_1, R_2, \dots in parallel is obtained from

$$R_{\text{eq}}^{-1} = R_1^{-1} + R_2^{-1} + \dots$$

- **Kirchhoff's laws:** Statement and use of the loop rule and the junction rule.
- **RC circuits:** The time constant is $\tau = RC$; What happens to the charge across a capacitor and the current through a resistor when the capacitor is being charged or discharged.
Charging the capacitor: The voltage varies in time according to

$$V(t) = V_0 (1 - e^{-t/RC}) ; \text{ similarly, for the charge, } q(t) = Q (1 - e^{-t/RC}) .$$

Discharging the capacitor: The voltage varies in time according to

$$V(t) = V_0 e^{-t/RC} .$$

Note: You are not required to know the topics and equations inside square brackets.