

## Prelab for PHYS222

### Kirchhoff Laws

Name \_\_\_\_\_

Section \_\_\_\_\_

1. Looking at Figure 20-1, how many different loops are in this circuit? Be mindful that you cannot cross a path more than one time (in a single loop). Show the loops on a diagram below.

2. What is Kirchhoff's Current Law? It is a restatement of what fundamental law?

3. What is Kirchhoff's Voltage Law?

4. Simplify the following relationships using the given resistance and voltage values. ***You do not have to solve these equations.*** You simply need to put them in a form where you can enter the appropriate terms in a simultaneous equation solving program or calculator.

You are thus solving two equations (with two unknown variables,  $I_1$  &  $I_2$  -See Lab theory section.)  
You will need equations with the forms  $AI_1 + BI_2 = C$  and  $DI_1 + EI_2 = F$ . Show all work.

$$E_1 - I_1 R_1 - I_1 R_2 + I_2 R_2 - I_1 R_3 = 0 \quad ; \quad -E_2 - I_2 R_4 - I_2 R_5 - I_2 R_2 + I_1 R_2 = 0$$

$R_1 = 22 \text{ ohms}$ ;  $R_2 = 18 \text{ ohms}$ ;  $R_3 = 15 \text{ ohms}$ ;  $R_4 = 10 \text{ ohms}$ ;  $R_5 = 12 \text{ ohms}$

$E_1 = 9.51 \text{ V}$  and  $E_2 = 9.52 \text{ V}$