

Name: \_\_\_\_\_ Section: \_\_\_\_\_ Date: \_\_\_\_\_


## Worksheet - Exp 17: Kirchoff's Laws for Circuits

**Objective:** This experiment applies Kirchoff's laws for circuits to a two-loop circuit to determine the currents and voltage differences around each loop.




**Theory:** The two basic laws that are most useful in analyzing circuits are Kirchoff's laws for current and voltage.

- *Kirchoff's Current Law* (The Junction Rule) states that at any junction of a circuit, the sum of currents entering the junction equals the sum of currents leaving the junction. This follows from the principle of charge conservation.  $\Sigma I_{in} = \Sigma I_{out}$
- *Kirchoff's Voltage Law* (The Loop Rule) states that around any closed loop in a circuit, the algebraic sum of all potential differences is equal to zero.  $\Sigma V_i = 0$

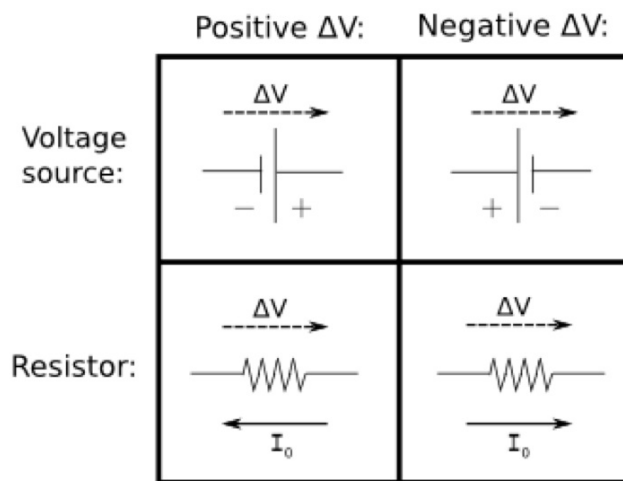
The following sign convention is observed when adding together potential differences:



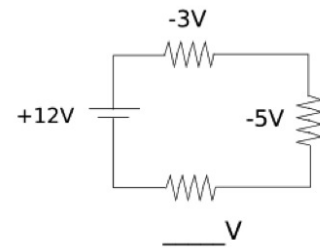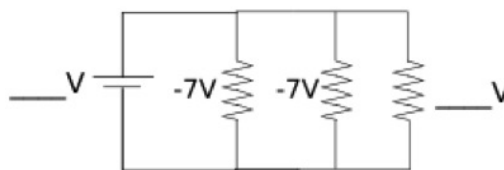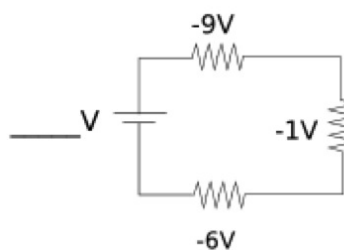1. Use Kirchoff's Voltage Law to find the missing voltage differences in the following circuits. For these circuits, current flows clockwise and potential difference is measured clockwise. (4 pts)



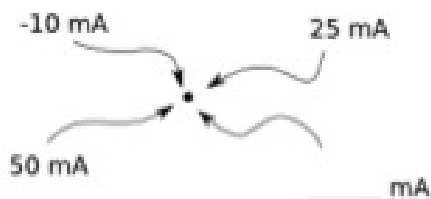2. Below are two nodes in different circuits. Each has four currents flowing either in or out of it. For each, use Kirchoff's Current Law to fill in the value of the missing current. [Note each sign (+/-) and direction] (4 pts)



**Procedure:****Part 1: Loop Method - Calculations**


3. Determine the nominal resistance and tolerance of each resistor by reading its color code. They should have the following approximate resistances: (5 pts)

$$R_1 = 10 \, \Omega \quad R_2 = 12 \, \Omega \quad R_3 = 15 \, \Omega$$

$$R_4 = 18 \, \Omega \quad R_5 = 22 \, \Omega$$

4. Measure the resistance of each resistor using an ohmmeter. (5 pts)
5. Measure  $\epsilon$  of the two batteries using a voltmeter. They should be at least 1.1V.
6. Construct the circuit shown. Do not connect the ammeter.
7. Using your knowledge of the loop and junction rules, write three equations relating currents in the circuit. (12 pts)

|       | Nominal | Measured |
|-------|---------|----------|
| $R_1$ |         |          |
| $R_2$ |         |          |
| $R_3$ |         |          |
| $R_4$ |         |          |
| $R_5$ |         |          |

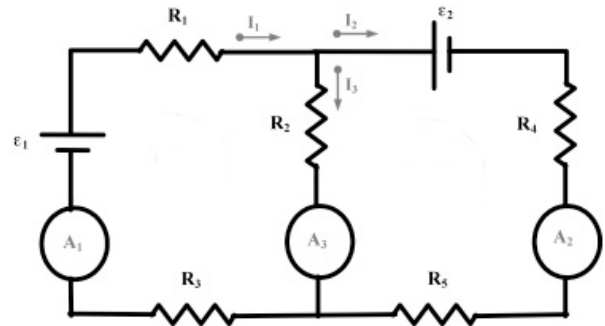

| <u>Color</u>            | <u>Number</u> | <u>Multiplier</u> |
|-------------------------|---------------|-------------------|
| Black                   | 0             | $10^0$            |
| Brown                   | 1             | $10^1$            |
| Red                     | 2             | $10^2$            |
| Orange                  | 3             | $10^3$            |
| Yellow                  | 4             | $10^4$            |
| Green                   | 5             | $10^5$            |
| Blue                    | 6             | $10^6$            |
| Violet                  | 7             | $10^7$            |
| Grey                    | 8             | $10^8$            |
| White                   | 9             | $10^9$            |
| <b><u>Tolerance</u></b> |               |                   |
| Gold                    | 5%            |                   |
| Silver                  | 10%           |                   |
| (No Band)               | 20%           |                   |

8. Record these equations on the last page. You must solve them by hand, but may use a calculator to verify.

### Part 2: Current & Voltage Laws Applied

- Connect the batteries to the circuit.
- Measure the current in each of the three branches of the circuit. Refer to the image to the right for proper ammeter connection technique. Disconnect the batteries and turn off the DMM after measurement. (6 pts)

| Current     | Theoretical | Measured | %Diff. |
|-------------|-------------|----------|--------|
| $I_1 (A_1)$ |             |          |        |
| $I_2 (A_2)$ |             |          |        |
| $I_3 (A_3)$ |             |          |        |



- Compare the measured values of current with the calculated values. If they are not approximately equal, check your calculations or retest the circuit. (6 pts)
- Reconnect the batteries and measure the electric potential across each element of the circuit. Record your answers in the table.  $V_1$  is the voltage across  $R_1$ , and so on. Sign and direction are crucial; measure based on the hypothetical directions of current you chose at the beginning. Refer to the diagram in the prelab material and follow your TAs guidance. (14 pts)
- Do the currents measured verify Kirchhoff's Current Law? How? If not, what could have caused the discrepancy? (10 pts)

|                 |  |
|-----------------|--|
| Left Loop:      |  |
| $\epsilon_1$    |  |
| $V_1$           |  |
| $V_2$           |  |
| $V_3$           |  |
| $\Sigma V$      |  |
| Right Loop:     |  |
| $\epsilon_2$    |  |
| $V_4$           |  |
| $V_5$           |  |
| $V_2$           |  |
| $\Sigma V$      |  |
| Perimeter Loop: |  |
| $\epsilon_1$    |  |
| $V_1$           |  |
| $\epsilon_2$    |  |
| $V_4$           |  |
| $V_5$           |  |
| $V_3$           |  |
| $\Sigma V$      |  |

- Do the voltages measured verify Kirchhoff's Voltage Law? How? Explain possible causes for any non-zero loop sums. (10 pts)

Record the equations from step 7 here. Solve them by hand. (24 pts)