

Name: \_\_\_\_\_ Section: \_\_\_\_\_ Date: \_\_\_\_\_

## Datasheet - Exp 16: Series and Parallel Circuits

### PROCEDURE

#### Part 1: Series Circuit

Record all data in tables on next page.

Recall that ( $i = 1, 2, \dots, n$ )

1. Measure each  $R_i$ , then construct a series circuit (Fig. 16.4) with 100- $\Omega$ , 200- $\Omega$ , and 300- $\Omega$  resistors and ammeter (200 mA DCA); **do not connect the power supply yet.**

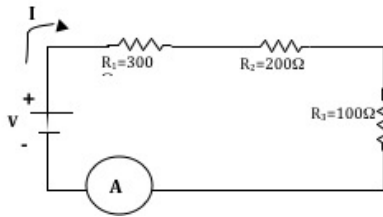


Fig. 16.4

2. Draw the schematic using measured  $R_i$  Values.
3. Calculate  $R_{eq}$  for the circuit.
4. Measure  $R_{eq}$  by plugging an ohmmeter in place of the power supply.
5. Remove the ohmmeter and connect the unplugged power supply and a voltmeter (DCV) to your circuit.

#### Get instructor approval of your circuit

6. Always be sure the power supply is turned off before you plug it into an outlet. Plug in the power supply, and set the voltage to 1.00 V. Measure the current and voltage.
7. Record the current (A) and the voltage (V) as you increase the voltage in 1.0 V increments up to 4.0 V.
8. Leave the voltage at 4.0 V; disconnect the voltmeter from the power supply. Maintaining the same orientation of the leads (if clockwise, black follows red), measure  $V_i$ , the voltage drop across each resistor.
9. Add these potential differences ( $\sum_{i=1} V_i$ ).
10. Does  $\sum_{i=1} V_i$  equal  $-4.0$  V? If not, ask your TA for guidance.

#### Part 2: Parallel Circuit

11. Repeat Part 1, Step 1 - Step 8, for the parallel circuit (Fig. 16.5).

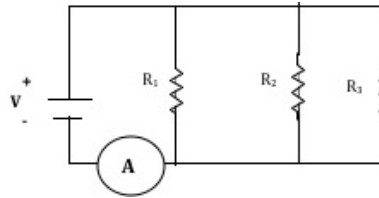


Fig. 16.5

Things to consider when writing your report:

Does  $V_2 = V_1 + V_A$ , or does  $V_2 = V_1 = V_3$ ? Are each of these values negative or positive?! Yes, it matters!

Does  $V = |V_1 + V_A|$ ?

#### Part 3: Combination Circuit

12. Repeat Part 1, Step 1 - Step 8, for the combination circuit (Fig. 16.6).

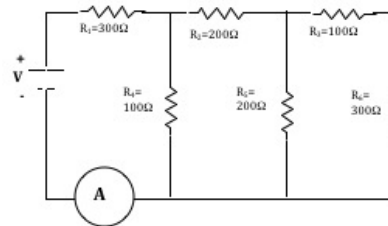


Fig. 16.6

#### Part 4: Graphing

13. Graph  $I$  vs.  $V$  for each of the first three circuits (Part 1, Part 2, and Part 3).

**Resistors:**

$R_i$	Measured
$R_1$	
$R_2$	
$R_3$	
$R_4$	
$R_5$	
$R_6$	
$R_A$	

**Measured Data:**

	$I_{Part1}$	$V_{Part1}$	$I_{Part2}$	$V_{Part2}$	$I_{Part3}$	$V_{Part3}$
<b>1.0 V</b>						
<b>2.0 V</b>						
<b>3.0 V</b>						
<b>4.0 V</b>						

**Circuit Data:**

	Part 1	Part 2	Part 3
<b>Calc <math>R_{eq}</math></b>			
<b>Meas <math>R_{eq}</math></b>			
<b>Graph <math>R_{eq}</math></b>			
$V_A$			
$V_1$			
$V_2$			
$V_3$			
$V_4$	X	X	
$V_5$	X	X	
$V_6$	X	X	

**Questions**

1. Why should the voltage drops (electric potential differences) across the resistors connected in parallel be the same? Were your values equal?
2. Calculate the equivalent resistance of each of the first three circuits you constructed for this experiment using your measured values. Show each step in this process (math and schematic). Remember to include  $R_A$  in your calculations.
3. Calculate the equivalent resistance of each circuit using the slope from your graphs.
4. Calculate Percent error for Measured  $R_{eq}$  compared to Calculated  $R_{eq}$ , and for Graph  $R_{eq}$  compared to Calculated  $R_{eq}$ . Use these in your discussion of data.