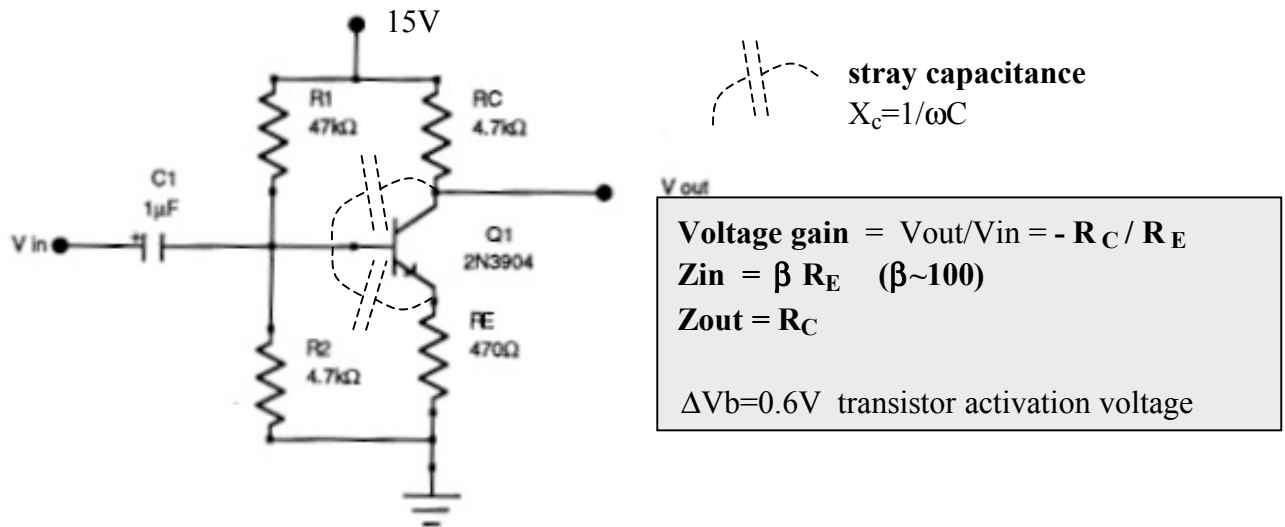


## Designing a the Common Emitter Amplifier -Handout

The transistor can be used as a voltage amplifier.  $R_1$ ,  $R_2$ ,  $R_C$ ,  $R_E$ , must be selected based on design criteria: Input impedance, Output Impedance, Gain.



1. The input signal is AC coupled to the amplifier. The input capacitor blocks the DC. There is stray capacitance in the circuit which we ignore at low frequency.
2. First select the output impedance.  $R_C = 4700\Omega$ .
3. Then choose the voltage drop across  $V_C$  to be half the supply voltage  $V_C = 15V/2 = 7.5V$ . This allows the AC input signal to swing full range of  $\pm 7.5V$
4. Calculate the nominal current thru  $I_C = (15V - V_C) / R_C = 7.5 / 4.7K = 1.6mA$
5. Choose  $R_E = R_C/10 = 470\Omega$  for a gain of 10!  $Z_{in} = \beta R_E$
6. To set the base voltage divider note that  $V_E = I_E R_E \sim I_C R_E = (1.6mA)(470\Omega) = 0.75V$
7. We have that  $V_B = V_E + \Delta V_b = 0.75V + 0.6V = 1.35V$
8. To limit the power supply current through the base choose  $R_2 < Z_{in} \sim (1/10) \beta R_E$   
**Let  $R_2 = (\beta / 10) R_E = 10 R_E = 4700 \Omega$  (rule of thumb!)**
9. Then  $R_1$  can be calculated by considering the current and voltage drop on  $R_1$ .  
 $I_2 = V_B / R_2 = 1.35V / 4700 \Omega = 0.29mA$  and  $I_B = I_C / \beta = 0.016A$   
 $I_1 = I_2 + I_B = 0.31mA$   
 $R_1 = (15V - V_B) / I_1 = (15.0 - 1.35)V / 0.31e-3A = \sim 46 k\Omega$  (Use 47 kΩ)

## Chapter-8 Homework

#1- Design a common-emitter amplifier with output impedance  $10\text{K}\Omega$  and a gain of 100 using a transistor of  $\beta=200$  and a 24V power supply.

