

## Notes on Kirchhoff's Laws uncertainty calculations

### The uncertainty of Metex DMM

DC voltmeter (all ranges)  $\pm 0.5\%$  of rdg + 1 dgt  $\Rightarrow \pm (1/2 \text{ percent of reading} + \text{one digit})$

DC ammeter (200 mA setting)  $\pm 1.2\%$  of rdg + 1 dgt  $\Rightarrow \pm (1.2 \text{ percent of reading} + \text{one digit})$

### Voltage uncertainty calculations

Sample data table for measured potentials (with calculated DMM uncertainties)

Loop1 Potentials $V \pm \delta V$ (V)	Loop2 Potentials $V \pm \delta V$ (V)	Loop3 Potentials $V \pm \delta V$ (V)
$V_{fa} - 1.548 \pm 0.009$	$V_{bc} - \pm$	$V_{fa} - 1.548 \pm$
$V_{ab} - -0.342 \pm 0.003$	$V_{cd} - \pm$	$V_{ab} - -0.3432$
$V_{be} - -0.712 \pm 0.005$	$V_{de} - \pm$	$V_{bc} - -1.568$
$V_{ef} - -0.490 \pm 0.003V$	$V_{eb} - \pm$	$V_{cd} - 0.384$
$\sum V_{loop} \pm \delta V_{loop} \quad 0.004 \pm \text{below}^*$	$\sum V_{loop} \pm \delta V_{loop}$	$V_{de} \quad 0.467$
XXXXXXXXXXXXXXXXXXXXXX	XXXXXXXXXXXXXXXXXXXXXX	$V_{ef} \quad -0.490$
XXXXXXXXXXXXXXXXXXXXXX	XXXXXXXXXXXXXXXXXXXXXX	$\sum V_{loop} \pm \delta V_{loop}$

#### Loop 1 uncertainties (How to Do)

$$\delta V_{fa} = \pm [1.548 \times 0.005 + 0.001]V = \pm [0.00774 + 0.001]V = \pm 0.00874V = \pm \mathbf{0.009V}$$

$$\delta V_{ab} = \pm [0.342 \times 0.005 + 0.001]V = \pm [0.00171 + 0.001]V = \pm 0.00271V = \pm \mathbf{0.003V}$$

$$\delta V_{be} = \pm [0.712 \times 0.005 + 0.001]V = \pm [0.00356 + 0.001]V = \pm 0.00456V = \pm \mathbf{0.005V}$$

$$\delta V_{ef} = \pm [0.490 \times 0.005 + 0.001]V = \pm [0.00245 + 0.001]V = \pm 0.00345V = \pm \mathbf{0.003V}$$

**Uncertainties are of a sum (i.e., Kirchhoff's Voltage law) are to be added in quadrature**

$$\delta V_{loop1} = \pm \sqrt{(0.009)^2 + (0.003)^2 + (0.005)^2 + (0.003)^2}V = \pm 0.0114V = \pm 0.01V$$

This uncertainty and the ones above should be added to data table (with correct significant figures) you turn in with lab report

\* Thus we see for final loop one sum plus uncertainty  $\sum V_{loop1} \pm \delta V_{loop1} = 0.00 \pm 0.01V$

**Similar calculations should be done for loop 2 (which would also cover loop 3). To save you work you can use loop 1 values in loops 2 and 3 as long as you match similar values. Therefore only 4 calculations needed.**

## Notes on Kirchhoff's Laws uncertainty calculations

### Current uncertainties calculations

**Sample data for current values** (without DMM uncertainties)

Measured-(DMM) <i>Current</i> ± $\delta$ <i>Current</i> (A)	Calculated (A)	% Difference
I <sub>1</sub> <b>0.0306</b> ± value calculated below	0.0329	
I <sub>2</sub> <b>0.0195</b> ± value calculated below	0.0217	
I <sub>3</sub> <b>0.0496</b> ± value calculated below	0.0547	

**Uncertainty calculation for current:** See DMM ammeter (200mA) uncertainty above:

$$\delta I_1 = \pm[0.0306 \times 0.012 + 0.0001]A = \pm[0.000367 + 0.0001]A = \pm[0.000467]A = \pm 0.0005A$$

$$\delta I_2 = \pm[0.0195 \times 0.012 + 0.0001]A = \pm[0.000234 + 0.0001]A = \pm[0.000334]A = \pm 0.0003A$$

$$\delta I_3 = \pm[0.0496 \times 0.012 + 0.0001]A = \pm[0.000595 + 0.0001]A = \pm[0.000695]A = \pm 0.0007A$$

**These uncertainties should be added to data table (like above) that you turn in with lab report**

Since Kirchhoff's current law states that the amount of current going into a junction is the same as the current out of a junction you are interested in whether

$$I_1 \pm \delta I_1 + I_2 \pm \delta I_2 = I_3 \pm \delta I_3$$

Using currents and uncertainty values from data above we see (adding uncertainties in quadrature)

$$0.0306 \pm 0.0005A + 0.0195 \pm 0.0003A = [0.0306 + 0.0195] \pm \sqrt{(0.0005)^2 + (0.0003)^2} A$$

$$I_1 \pm \delta I_1 + I_2 \pm \delta I_2 = 0.0501 \pm 0.00058A = 0.0501 \pm 0.0006A$$

$$\rightarrow 0.0495A < I_1 + I_2 < 0.0507A$$

**The measured value for I<sub>3</sub> was 0.0496 ± 0.0007A.**

$$\rightarrow 0.0489A < I_3 < 0.0503A$$

Is  $I_1 \pm \delta I_1 + I_2 \pm \delta I_2$  equal to  $I_3 \pm \delta I_3$  when uncertainty is considered? Yes since results overlap.

**Comments on results. The data sheet that you fill out are not the results.** Your results are taken from the data sheets (and the uncertainties determined) and should answer the following questions:

- 1) Are the sum the voltages around any closed loop equal to zero (when uncertainty is considered)
- 2) Are the sum of the currents going into a junction the same as the current coming out of a junction (when uncertainty is considered).

**If you give only the data sheet as your results you will be penalized!!!!**